

assume the same graph for each

here will get $Y_a = Y^T$

$$v_b^T i_b = 0 \quad v_b^{aT} i_b^a = 0$$

$$v_b^{aT} i_b^a - v_b^T i_b = 0 \quad \text{or the same}$$

$$v_{b_1}^a i_{b_1}^a + v_{b_2}^a i_{b_2}^a + v_b^{aT} i_b^a - v_b^T i_b = 0$$

$$v_{b_1}^a i_{b_1}^a - v_b^T i_b = 0$$

EE 610
10/26/10 ⇒ 10/27/10

$d = \text{differential}$


$$\begin{aligned}
 & \hat{V}_2^a i_{b_2} - \hat{V}_1^a i_{b_1} + \hat{V}_b^{aT} Y_{b \times b} \hat{V}_b - \hat{V}_b^T Y_{b \times b}^a \hat{V}_b^a = 0 \\
 & = \underbrace{\left(\hat{V}_b^{aT} Y_{b \times b}^a \hat{V}_b^a \right)^T}_{\hat{V}_b^{aT} Y_{b \times b}^a} = \hat{V}_b^{aT} Y_{b \times b}^a \hat{V}_b^a
 \end{aligned}$$

$$\begin{aligned}
 & \left(d \hat{V}_2^a \right) i_{b_2} + \hat{V}_2^a d i_{b_2} - \left(d \hat{V}_1^a \right) i_{b_1} - \hat{V}_1^a d i_{b_1} \\
 & + d \hat{V}_b^{aT} Y_{b \times b}^a \hat{V}_b^a + \hat{V}_b^{aT} d Y_{b \times b}^a \hat{V}_b^a + \hat{V}_b^{aT} Y_{b \times b}^a d \hat{V}_b^a \\
 & - d \hat{V}_b^T Y_{b \times b}^a \hat{V}_b^a - \hat{V}_b^T d Y_{b \times b}^a \hat{V}_b^a - \hat{V}_b^T Y_{b \times b}^a d \hat{V}_b^a = 0
 \end{aligned}$$

\hat{V}_b^{aT} doesn't make changes in adjoint current

$$\hat{V}_2^a \cdot d i_{b_2} = \hat{V}_b^{aT} d Y_{b \times b}^a \hat{V}_b^a$$

Example.

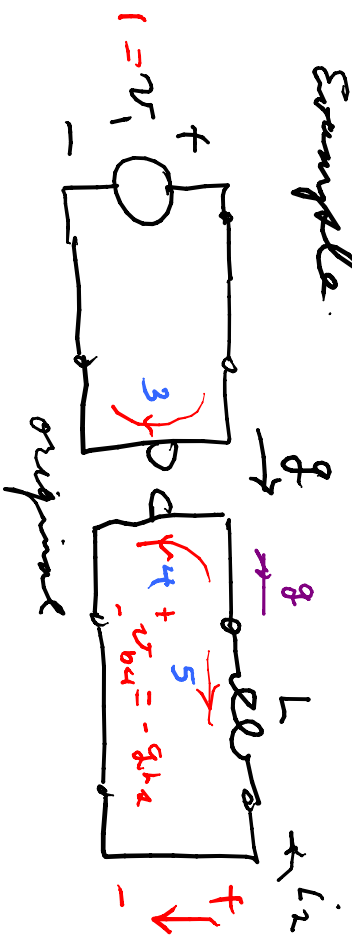


$$T(\alpha) = \frac{i_2}{v_1}$$

derive $\frac{\partial T(\alpha)}{\partial g}$

$$Y_{6 \times 6} = \begin{bmatrix} 0 & g & 0 \\ -g & 0 & 0 \\ 0 & 0 & \frac{1}{L} \end{bmatrix}$$
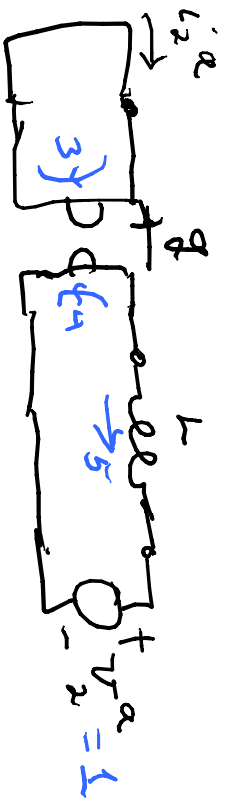
$$Y_{4 \times 6} = \begin{bmatrix} 0 & -g & 0 & 0 & 0 & 0 \\ 0 & g & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1/\alpha & 0 \end{bmatrix}$$



$$\frac{\partial Y_{6 \times 6}}{\partial g} = \begin{bmatrix} 0 & 1 & 0 \\ -1 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix}, \quad \frac{\partial Y_{4 \times 6}}{\partial g} \vec{v}_b = \begin{bmatrix} v_3 & v_4 & v_5 \\ v_3 & v_4 & v_5 \\ -1 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} v_3 \\ v_4 \\ v_5 \end{bmatrix}$$

$$\frac{\partial i_2}{\partial g} = \frac{\partial v_2}{\partial g} = v_3 \alpha v_4 - v_4 \alpha v_3 = v_1 = 1$$

∴ solve the 2 circuits:
(used in chap 9
section 3)

$$\frac{di_{o2}}{dq} = v_{b3}^{-\alpha} v_{b4} \rightarrow v_{b4}^{-\alpha} v_{b3}$$

$$= v_{b3}^{-\alpha} (-g_{kA}) - v_{b4}^{-\alpha} \cdot 1 = \frac{di_{o2}}{dq} = -1$$

from the circuit $i_{o2} = g$, $-\frac{di_{o2}}{dq} = 1$


Some adjoints

$$\sum_{r=1}^{\infty} y = \frac{1}{R} = Y^{\alpha}$$

$$\frac{1}{I} C_A = Y = Y^{\alpha}$$


$$h_1 \sum_{k=1}^M \left\{ F_{k2} \right\}$$

is its own adjoint

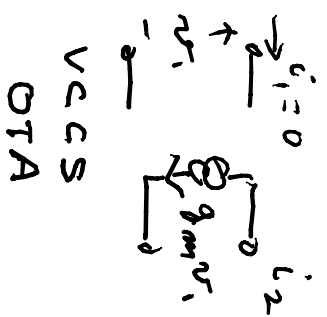


VCCS
OTA
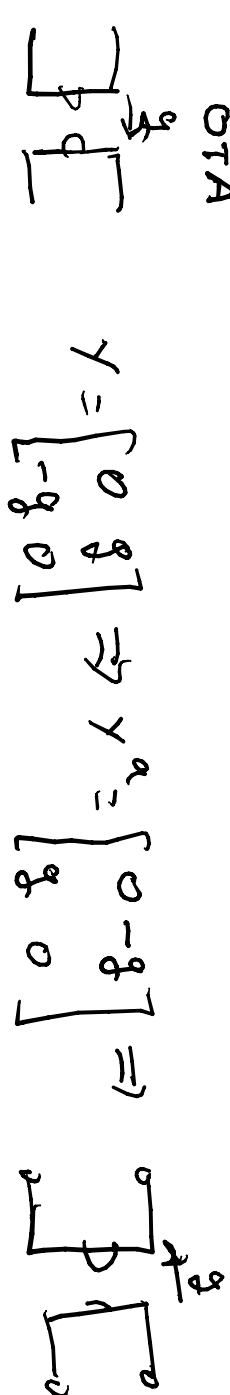
$$Y = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix} \Rightarrow Y^a = Y^T = \begin{bmatrix} 0 & g_m \\ 0 & 0 \end{bmatrix}$$


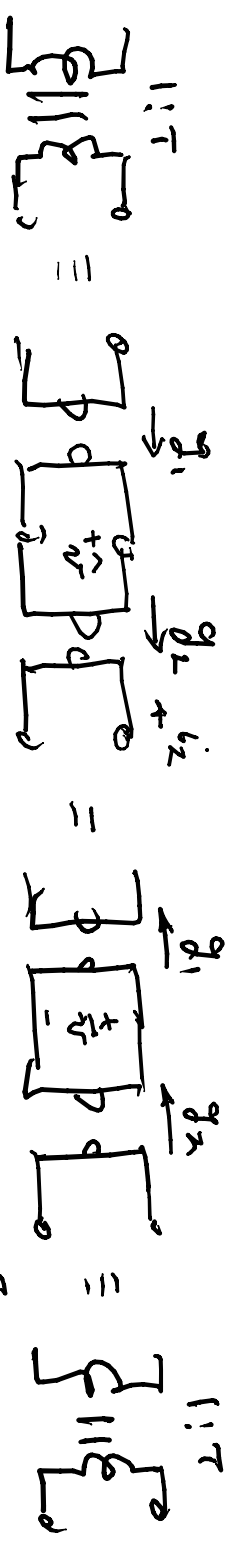
$$Y = \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix} \Rightarrow Y^a = \begin{bmatrix} 0 & -g \\ g & 0 \end{bmatrix} \Rightarrow$$



adjoint

$$i_1 + T i_2 = 0$$

$$i_1 = g_1 v_1, i_2 = -g_2 v_2$$

$$\frac{i_1}{i_2} = -\frac{g_1}{g_2} \Rightarrow i_1 + \frac{g_1}{g_2} i_2 = 0$$

$$i_1 = -g_1 v_1, i_2 = +g_2 v_2$$

$$i_1 + g_1 i_2 = 0$$

look at symmetrizing a symmetric constant Y

$$Y = \begin{bmatrix} 2 & 3 & 4 \\ 3 & 5 & -1 \\ 4 & -1 & 6 \end{bmatrix}; \quad \Delta = 2 \begin{vmatrix} 5 & -1 \\ -1 & 6 \end{vmatrix} + 4 \begin{vmatrix} 3 & 4 \\ -1 & 6 \end{vmatrix} + 4 \begin{vmatrix} 3 & 4 \\ 5 & -1 \end{vmatrix}$$

$$= 2 \times 29 - 3 \times 14 + 4(-23) < 0$$

$\therefore Y$ is not PR

$$T Y T^T;$$

$$\underbrace{\begin{bmatrix} 1 & 0 & 0 \\ -3/2 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}}_{T_1} \underbrace{\begin{bmatrix} 2 & 3 & 4 \\ 3 & 5 & -1 \\ 4 & -1 & 6 \end{bmatrix}}_Y \underbrace{\begin{bmatrix} 1 & -3/2 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}}_{T_1^T}$$

use T_1 to add $-\frac{y_{21}}{y_{11}}$ to 2nd row
(& same for columns by T_1^T)

$$= \begin{bmatrix} 2 & 3 & 4 \\ 0 & 1/2 & -7 \\ 4 & -1 & 6 \end{bmatrix} \begin{bmatrix} 1 & -3/2 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} = \begin{bmatrix} 2 & 0 & 4 \\ 0 & 1/2 & -7 \\ 4 & -7 & 6 \end{bmatrix}$$

use T_2
for makes
(3,1) entry 0

$$\underbrace{\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ -2 & 0 & 1 \end{bmatrix}}_{T_2} \begin{bmatrix} 2 & 0 & 4 \\ 0 & 1/2 & -7 \\ 4 & -7 & 6 \end{bmatrix} \begin{bmatrix} 1 & 0 & -2 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 2 & 0 & 4 \\ 0 & 1/2 & -7 \\ 0 & -7 & -2 \end{bmatrix} = \begin{bmatrix} 1 & 0 & -2 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 2 & 0 & 0 \\ 0 & 1/2 & -7 \\ 0 & -7 & -2 \end{bmatrix}$$

use T_3

$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 7/1/2 & 1 \end{bmatrix} \begin{bmatrix} 2 & 0 & 0 \\ 0 & 1/2 & -7 \\ 0 & -7 & -2 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 1/4 \\ 0 & 0 & 1 \end{bmatrix}$$

\Rightarrow (3,3) entry
 $= -14 \times 2 - 2 = -100$

$$= \begin{bmatrix} 2 & 0 & 0 \\ 0 & 1/2 & -7 \\ 0 & 0 & -100 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 7/2 \\ 0 & 0 & 1 \end{bmatrix} = \begin{bmatrix} 2 & 0 & 0 \\ 0 & 1/2 & 0 \\ 0 & 0 & -100 \end{bmatrix}$$

$$= (T_3 T_2 T_1) Y (T_3^T T_2^T T_1^T)$$

