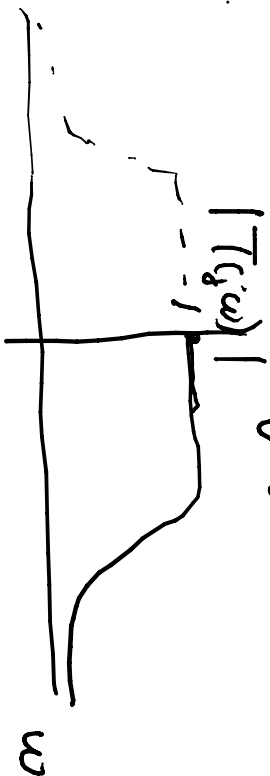


Maximize flat $T(s)$, low pass

EE610
11/02/10



$$T(s) = \frac{K}{s^m + a_{m-1}s^{m-1} + \dots + a_0}$$

normalize to

$$T(s) = \frac{1}{s^m + a_{m-1}s^{m-1} + \dots + a_1s + 1}$$

$$|T(j\omega)|^2 = \frac{1}{D(j\omega)D(-j\omega)} = \frac{1}{D(s)}$$

$$\frac{d|T(j\omega)|^2}{d\omega} = 2|T(j\omega)| \frac{d|T(j\omega)|}{d\omega}$$

$$g(\omega), \quad \frac{d|g(\omega)|}{d\omega} = \frac{dg}{d\omega} \cdot \frac{-1}{g(\omega)^2}$$

∴ look at $\frac{1}{|T(\omega)|^2}$ & its derivatives:

$$\frac{1}{|T(\omega)|^2} = 1 + k_2 \omega^2 + \dots + k_{2m} \omega^{2m}$$

↑ coefficients are the derivatives & for maximally flat $T(\omega)$ we set all the coefficients ~~residuals~~ to zero

$$|T(\omega)|^2 = \frac{1}{\omega^{2m} + 1} = T(\omega)T(-j\omega)$$

analytically continue by $\omega = s/j$

$$T(a)T(-a) = \frac{1}{(-1)^m a^{2m+1}} \quad \text{order of } a^{2m} = (-1) / (-1)^m = (-1)^{m+1}$$

$$= \begin{cases} +1 & \text{if } m \text{ odd} \\ -1 & \text{if } m \text{ even} \end{cases}$$

$$\therefore a^{2m} = \begin{cases} e^{j(0+2k\pi)} & m = \text{odd} \\ e^{j(\pi+2k\pi)} & m = \text{even} \end{cases}$$


$$\therefore a^{2m} = \begin{cases} e^{j(\frac{2k\pi}{2m})} & m \text{ odd} \\ e^{j(\frac{\pi+2k\pi}{2m})} & m \text{ even} \end{cases} \quad k=0, 1, 2, \dots, 2m-1$$

$$\text{Rk: } m=1 = \text{odd} \quad e^{j0} = 1, \quad e^{j\frac{2\pi}{2}} = e^{j\pi} = -1 \Rightarrow \text{poles at } \pm 1$$



$$\therefore T(a) = \frac{1}{a - (-1)} = \frac{1}{a+1}$$

$\text{Rk: } m=2 = \text{even}, \quad e^{j\pi/4}, e^{j3\pi/4}, e^{j5\pi/4}, e^{j7\pi/4}, e^{j9\pi/4} = e^{j\pi/4}$
 $k=0, \quad k=1, \quad k=2, \quad k=3, \quad k=4 \equiv 0 \pmod 4$

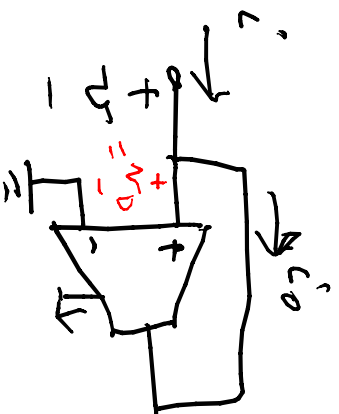
$\therefore T(a) = \frac{1}{(a - a_1)(a - a_1^*)} = \frac{1}{a^2 + \sqrt{2}a + 1}$ (Butterworth)



Kohärenz)

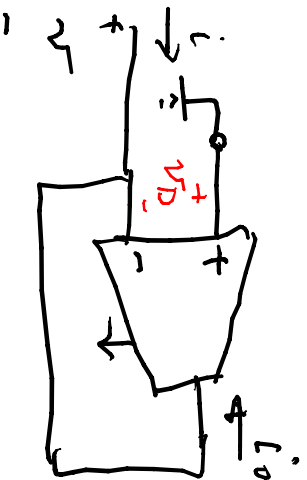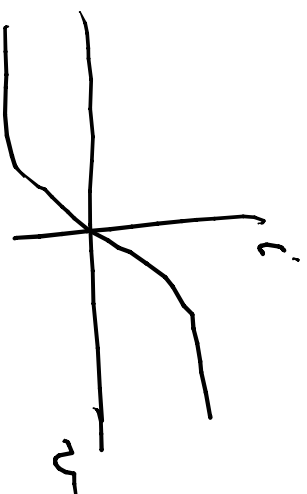


$$u_D = u$$


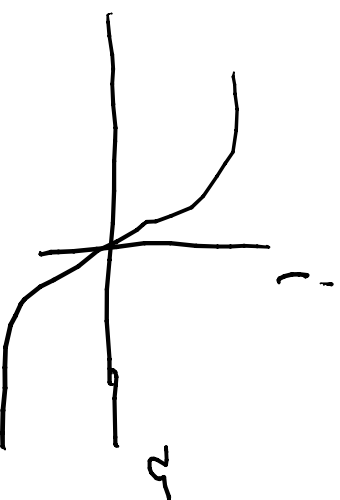


(a negative remater)


Das geht kaputt

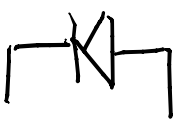


\Rightarrow

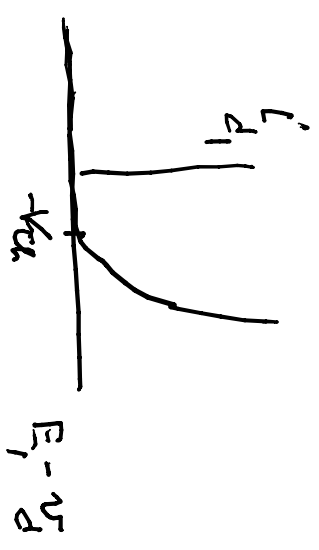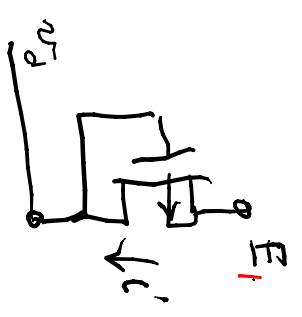



gives hysterisis
if $E_1 < E_2$

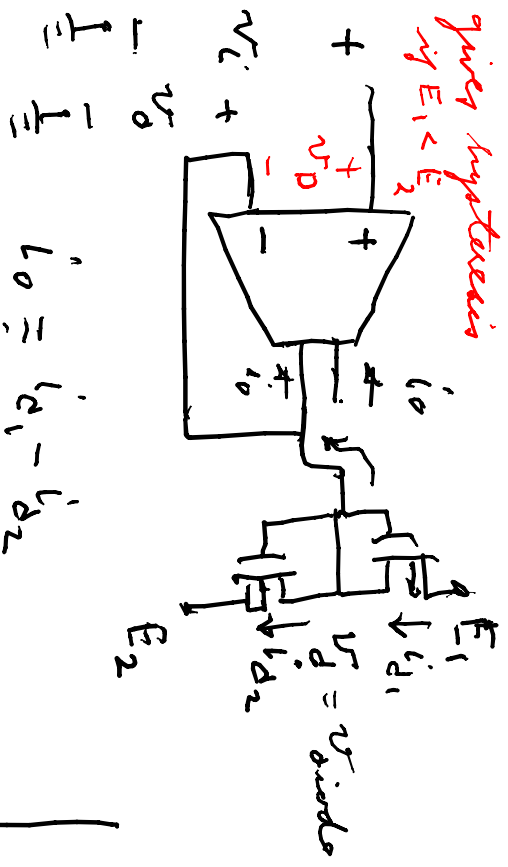


$I_0 = I_{d1} - I_{d2}$

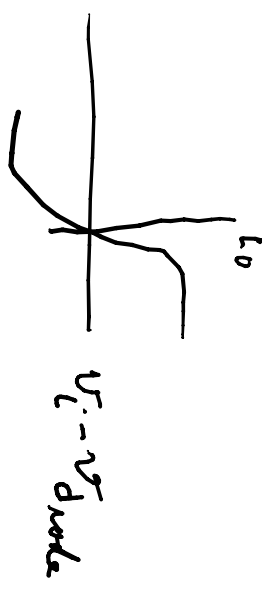


for the diode conformation

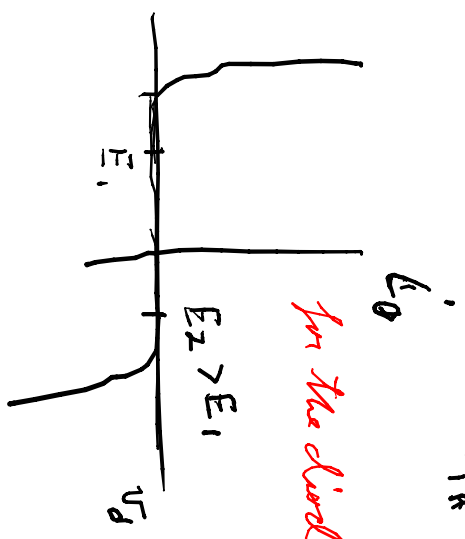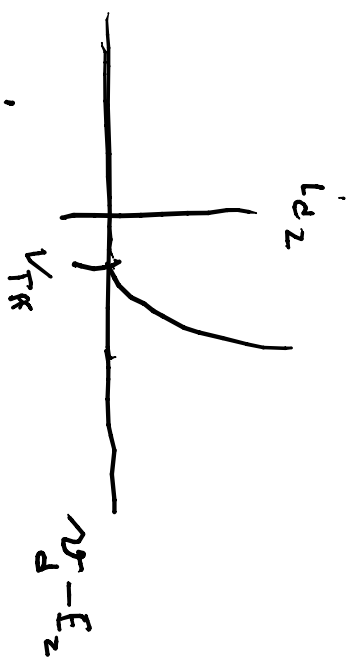

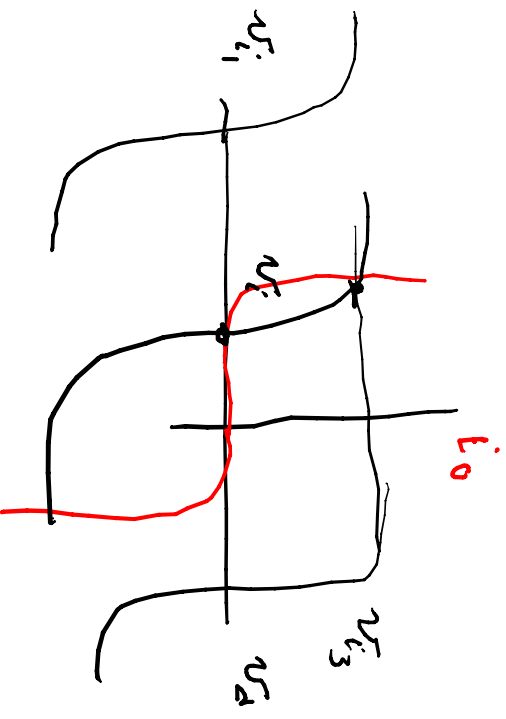

Not interest points

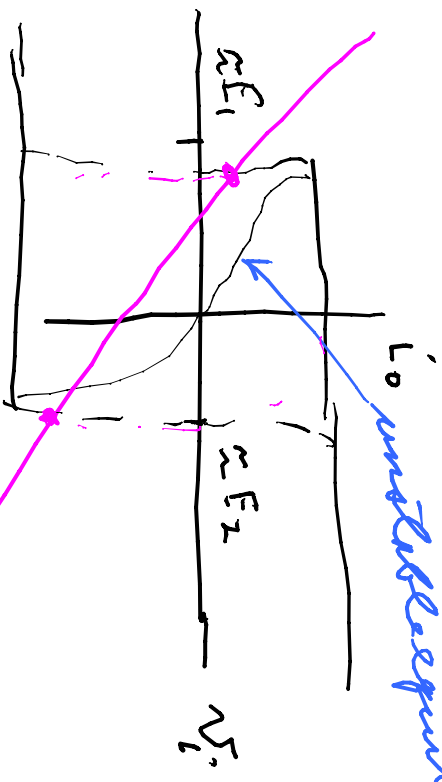


L_0 multiple equilibrium


parallel load line for an oscillator

this circuit gives "strong" hysteresis

Making the OTA, via differential pairs

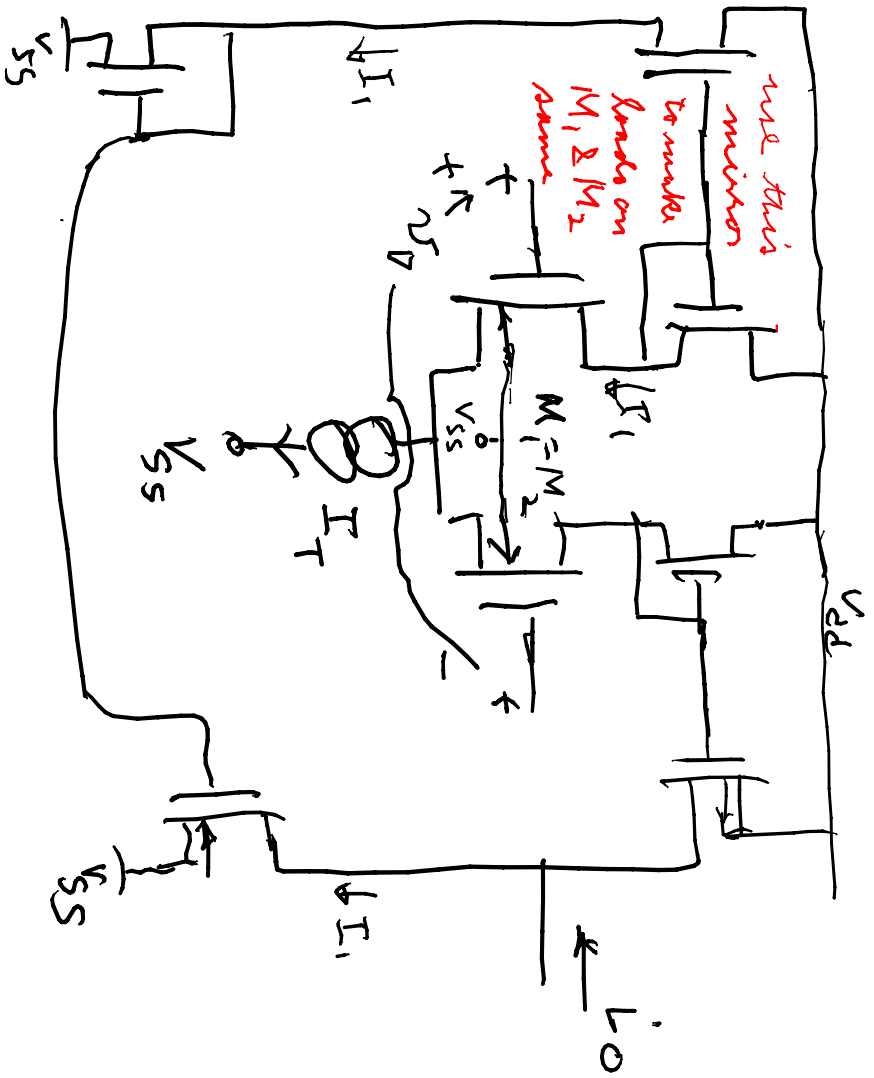

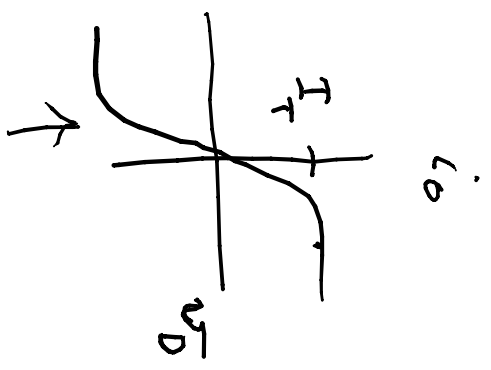Since M_1 & M_2 have same V_{GS} their threshold voltages are the same & cancel in obtaining I_0



$I_{\text{tank}} \left(\frac{v_D}{V_T} \right)$


if sub-threshold
(by I_T in nano-Amps)

Current source

Tsukuri, et al, CMOS FET

Complementary current-mode

(IEEE, WT 11-5.1-5.4, 1998)

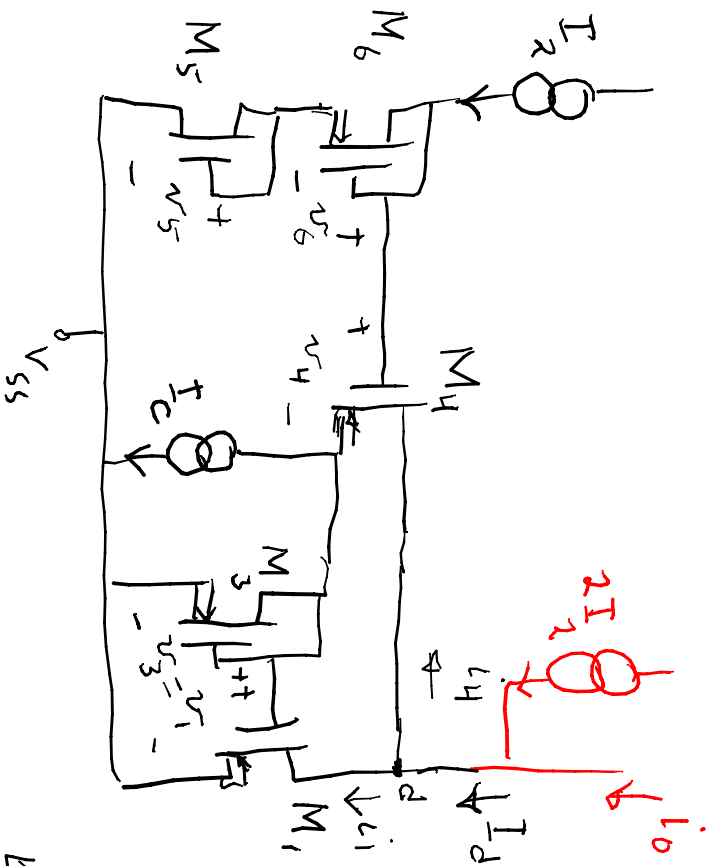

will give a square
 $out = I_D - 2I_r = (\frac{1}{8}I_r) I_c = output / 8I_r$

all NMOS transistors identical & in saturation

$$i_D = \beta (V_{GS} - V_{th})^2$$

$$\Rightarrow V_{GS} = V_{th} + \sqrt{i_D / \beta}$$

key equation: $v_i = V_{GS_i}$, $i=1, \dots, 6$

$$v_5 + v_6 = v_4 + v_1$$

$$\Downarrow v_4 = I_D - I_1 = I_c + I_1$$

$$\sqrt{I_2} + \sqrt{I_2} = \sqrt{(I_D - I_1) + I_1}$$

Answering $4I_2 = I_D - i_1 + 2\sqrt{(I_D - i_1)i_1 + i_1^2} \Rightarrow 4I_2 - I_D = 2\sqrt{(I_D - i_1)i_1}$

Answering again: $16I_2^2 + I_D^2 = 8I_2I_D = 4(I_D - i_1)i_1$ but $I_D - i_1 = I_c + i_1 = i_4$
 $\Rightarrow 2i_1 = I_D - I_c$

$$= 4(I_D - \frac{I_D - I_c}{2})(\frac{I_D - I_c}{2})$$


$$= (I_D + I_c)(I_D - I_c)$$

$$= I_D^2 - I_c^2$$

cancel I_D^2 : $8I_2I_D = 16I_2^2 + I_c^2$

$$\Rightarrow I_D = \frac{1}{8I_2} \cdot I_c^2 + 2I_2$$

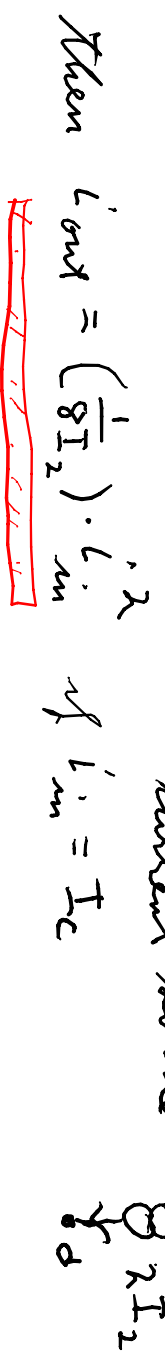\therefore if let $i_{out} = i_0 = I_D - 2I_2$ by inserting at node the current source



If we $I_1 - 2I_2$ as input and an output where I_C is
can also get $I_{out} = \sqrt{8I_2}$. Lin

If the transistors work in subthreshold $I_3 = I_0 e^{V_{GS}/V_T}$

Then $V_6 + V_5 = V_4 + V_1$ is $2\ln I_2 = \ln i_4 + \ln i_1$

$$\Rightarrow I_2^2 = i_1 i_4$$

and can restructure to get the square or $\sqrt{\quad}$.