
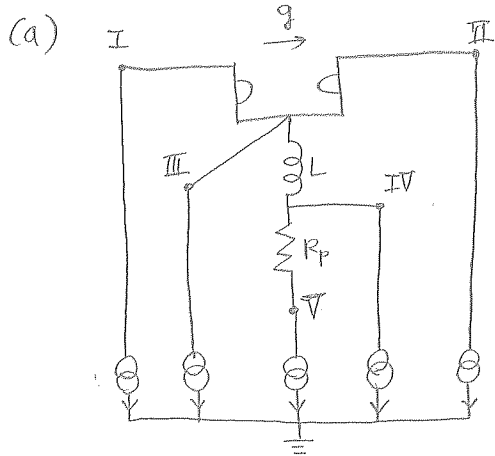



3

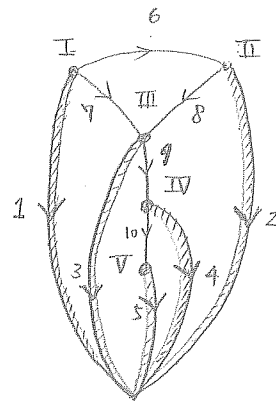

graph and tree \Rightarrow



① Cut set matrix and tie set matrix:

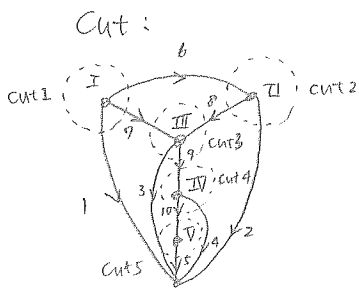

$$\underline{C} = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 1 & 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & -1 & 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & -1 & -1 & 1 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & -1 & 1 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & -1 \end{bmatrix} \underline{i}$$

\underline{C} : Cut set matrix

$$\Rightarrow \text{tie set matrix } \underline{T} = \begin{bmatrix} -1 & 1 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ -1 & 0 & 1 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & -1 & 1 & 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix}$$

② $\underline{A} \underline{v} = \underline{B} \underline{i}$:

$$\begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \\ v_7 \\ v_8 \\ v_9 \\ v_{10} \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \\ i_7 \\ i_8 \\ i_9 \\ i_{10} \end{bmatrix}$$

Use $\left[\underline{A} \cdot \underline{C}^T \mid -\underline{B} \cdot \underline{T}^T \right] \begin{bmatrix} \underline{v} \\ \underline{i} \end{bmatrix} = -\underline{B} \underline{j} \Rightarrow$

$$\begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & -1 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & -1 & -1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & -1 & 1 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & -1 \\ 0 & 0 & 0 & 0 & 0 & 0 & -1 & 0 & 0 & 0 & 0 \\ 0 & g & -g & 0 & 0 & 0 & 0 & -1 & 0 & 0 & 0 \\ -g & 0 & g & 0 & 0 & 0 & 0 & 0 & -1 & 0 & 0 \\ 0 & 0 & \frac{1}{sL} & \frac{1}{sL} & 0 & 0 & 0 & 0 & 0 & -1 & 0 \\ 0 & 0 & \frac{1}{R_p} & \frac{1}{R_p} & 0 & 0 & 0 & 0 & 0 & 0 & -1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ i_6 \\ i_7 \\ i_8 \\ i_9 \\ i_{10} \end{bmatrix} = \begin{bmatrix} -i_1 \\ -i_2 \\ -i_3 \\ -i_4 \\ -i_5 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\Rightarrow \hat{u}_6 = 0 \Rightarrow \hat{u}_7 = -\hat{u}_1, \quad \hat{u}_8 = -\hat{u}_2 \Rightarrow \hat{u}_9 + \hat{u}_{10} + \hat{u}_{11} = -\hat{u}_3, \quad -\hat{u}_9 + \hat{u}_{10} = -\hat{u}_4, \quad \hat{u}_{10} = \hat{u}_5$$

$$\text{let } v_5 = 0 \Rightarrow \frac{1}{R_p} v_4 = \hat{u}_6, \quad \frac{1}{sL} (v_3 - v_4) = -\hat{u}_1 - \hat{u}_2 - \hat{u}_3, \quad g(-v_1 + v_3) = -\hat{u}_2$$

$$g(v_2 - v_3) = -\hat{u}_1$$

③ the semistate equations:

$$(1) \text{ input current into port 1: } I_1 = -\hat{u}_1 = g(v_2 - v_3) = g\left(v_2 - v_1 + \frac{\hat{u}_2}{g}\right)$$

$$(2) \text{ input current into port 2: } I_2 = -\hat{u}_2: \quad \frac{1}{sL} (v_3 - v_4) = -\hat{u}_1 - \hat{u}_2 - \hat{u}_3$$

$$\Rightarrow \frac{1}{sL} \left[v_1 - \frac{\hat{u}_2}{g} - R_p(-\hat{u}_1 - \hat{u}_2 - \hat{u}_3 - \hat{u}_4) \right] = -\hat{u}_1 - \hat{u}_2 - \hat{u}_3$$

$$\text{choose } \hat{u}_3 = \hat{u}_4 = 0 \Rightarrow \frac{1}{sL} \left(v_1 - \frac{\hat{u}_2}{g} \right) = \left(1 + \frac{R_p}{sL} \right) (-\hat{u}_1 - \hat{u}_2)$$

$$\because v_5 = 0 \quad \therefore \text{The voltage at port 1: } V_1 = v_1$$

$$\text{The voltage at port 2: } V_2 = v_2$$

$$\Rightarrow \begin{cases} V_1 = \frac{1}{g} I_2 + sL(I_1 + I_2) + R_p(I_1 + I_2) \\ V_2 = +V_1 + \frac{1}{g} I_1 + \frac{1}{g} I_2 = \frac{1}{g} I_1 + sL(I_1 + I_2) + R_p(I_1 + I_2) \end{cases}$$

⇒ The semistate equations:

$$\begin{cases} V_1 = \frac{1}{g} I_2 + R_p(I_1 + I_2) + sL(I_1 + I_2) \\ V_2 = \frac{1}{g} I_1 + R_p(I_1 + I_2) + sL(I_1 + I_2) \end{cases}$$

$$\text{or in the matrix form: } \vec{V} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}, \quad \vec{I} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = s \begin{bmatrix} L & L \\ L & L \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} + \begin{bmatrix} +R_p & +R_p - \frac{1}{g} \\ +R_p + \frac{1}{g} & +R_p \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

(b) The two port impedance matrix:

$$\because \vec{V} = \underline{\underline{Z}} \vec{I}, \quad \text{the semistate equation: } \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} R_p + sL & R_p + sL - \frac{1}{g} \\ R_p + sL + \frac{1}{g} & R_p + sL \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\underline{\underline{Z}} = \begin{bmatrix} R_p + sL & \frac{1}{g} + R_p + sL \\ \frac{1}{g} + R_p + sL & R_p + sL \end{bmatrix}$$

Note the result is the same as # 1.