

## PSet 4 #1. L-R properties

Using the partial fraction expansion for the first Foster reactance function derive the partial fraction expansion of the impedance  $z(s)$  for a passive inductor - resistor circuit. From that, give properties of the poles and zeros of  $z(s)$  and  $y(s)$  and the even part zeros of  $z(s)$ . Relate the even part zeros of  $z(s)$  to those of  $y(s)$ .

The first Foster function can be written as:

$$F_1(s) = K \frac{(s+\sigma_1)(s+\sigma_3)\cdots(s+\sigma_m)}{(s+\sigma_2)(s+\sigma_4)\cdots(s+\sigma_n)}$$

where  $0 \leq \sigma_1 < \sigma_2 < \sigma_3 \cdots$  and  $m = n \pm 1$ .

The partial fraction expansion is therefore given as:

$$F_1(s) = K_1 + \frac{K_2s}{s+\sigma_2} + \frac{K_4s}{s+\sigma_4} + \cdots + \frac{K_ns}{s+\sigma_n}$$

This is in the form of a inductor - resistor network circuit since each term  $\frac{Ks}{s+\sigma}$  can be considered an inductor-resistor pair in parallel:  $z(s) = \frac{RLs}{R+Ls}$

$$z(s) = K \frac{(s+\sigma_1)(s+\sigma_3)\cdots(s+\sigma_m)}{(s+\sigma_2)(s+\sigma_4)\cdots(s+\sigma_n)}$$

Therefore, by looking at the partial fraction expansion of  $z(s)$ , we see that there are alternating poles and zeros at  $s = -\sigma_1, -\sigma_3, \dots, -\sigma_m$  (zeros) and  $s = -\sigma_2, -\sigma_4, \dots, -\sigma_n$  (poles).

$$y(s) = \frac{1}{z(s)} = \frac{1}{K} \frac{(s+\sigma_2)(s+\sigma_4)\cdots(s+\sigma_n)}{(s+\sigma_1)(s+\sigma_3)\cdots(s+\sigma_m)}$$

Looking at the partial fraction expansion of  $y(s)$ , we see that there are alternating poles and zeros at  $s = -\sigma_1, -\sigma_3, \dots, -\sigma_m$  (poles) and  $s = -\sigma_2, -\sigma_4, \dots, -\sigma_n$  (zeros).

To find the even part of the zeros of  $z(s)$  we look at the admittance,  $y(s)$  and use the formula  $f_e(x) = \frac{1}{2}[f(x) + f(-x)]$ :

$$y_e(s) = \frac{1}{2} \left[ \frac{1}{K_\infty} + \frac{K_1s}{s+\sigma_1} + \frac{K_3s}{s+\sigma_3} + \cdots + \frac{K_ms}{s+\sigma_m} + \frac{1}{K_\infty} + \frac{K_1s}{s-\sigma_1} + \frac{K_3s}{s-\sigma_3} + \cdots + \frac{K_ms}{s-\sigma_m} \right]$$

This simplifies down to:

$$y_e(s) = \frac{1}{K_\infty} + \frac{K_1s^2}{s^2-\sigma_1^2} + \frac{K_3s^2}{s^2-\sigma_3^2} + \cdots + \frac{K_ms^2}{s^2-\sigma_m^2}$$

As you can see, the even part of  $y(s)$  gives matching poles at  $\pm\sigma_m$  which means that the even part of  $z(s)$  has zeros at  $\pm\sigma_m$ . Similarly for  $y(s)$ , the even part will have zeros at  $\pm\sigma_n$ .