


ENEE 303H Final Exam – Fall 2011 Take Home

150 points, open book, open notes. Good luck! Your signature certifies that the work is your own [due by the end of the scheduled final time in Room AVW 1364 with notebook]

1. (50 points)

The following is possibly a new kind of inverter having its input at the bulks (called body in the text; structure on p. 233, model on p. 324). Assume that the transistors are completely complementary along with $|V_{TO}|=0.1$, $V_{dd}=-V_{ss}=0.2$, $|γ|=0.4$, $KP=10E-5$, $λ=0$, $φ_f=0.6$, $W/L=10$

- Give the Q point NMOS drain current, I_{Dn} and small signal equivalent circuit and find the small signal DC voltage gain V_{out}/V_{in} .
- Assuming the bulk diodes satisfy the law of Figure 4.8, page 174 (that is, are turned off for $|V_{diode}| < 0.5$), give V_{out} over $-0.2 < V_{in} < 0.2$.
- Discuss if this is a good inverter for low power systems.

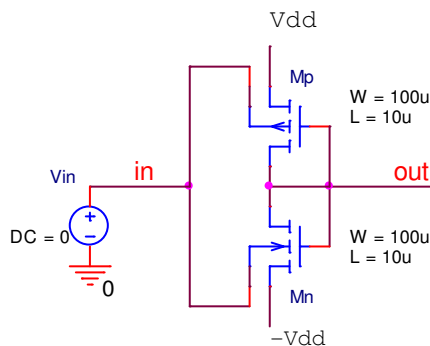


2. (50 points)

Use a 4007 PMOS transistor in the single ended Colpitts oscillator circuit of the next page (similar to that presented by Kyle Werner). Use equal capacitors $C1=C2=1\mu F$, L , and g_m to give $\omega_0=1\text{KHz}$, $R=10=-10\text{K}\Omega$ and $V_{dd}=5\text{V}$; ~~set I_{bias} at $100\mu\text{A}$~~ . That is find L , V_{bias} , I_{bias} , and g_m . Ignore transistor capacitors and the Early effect. You should find the new oscillation condition placed on g_m .

The 4007 Spice model parameters to be used are:
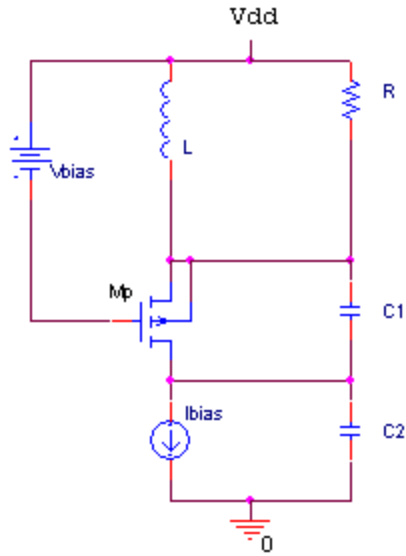
```
.model M4007N nmos(Level=1 Tox=300n KP=20.54u W=144u L=8u VTO= 1.3
+ LAMBDA=15m Cbd=4p Cbs=4p)
.model M4007P pmos(Level=1 Tox=300n KP=10.32u W=328u L=8u VTO=-1.5
+ LAMBDA=15m Cbd=8p Cbs=8p)
```



3. (50 points)

Use the following ideal model for the OTA (with also zero currents into the + & - leads) for which I_T and V_S are real and positive.

$$I_o = \begin{cases} I_T & \text{for } V_S \leq V_{id} \\ G_m V_{id} & \text{for } -V_S \leq V_{id} \leq V_S \\ -I_T & \text{for } V_{id} \leq -V_S \end{cases}$$

For the following circuit:

- Give the equation for the load curve of I_L versus V_o and graph the curve.
- Graph $-I_L$ on the OTA curve of I_o versus V_o when $V_i = 0$ for the two cases of $G_m < G = 1/R$ and $G_m > G = 1/R$
- The circuit has hysteresis for certain values of $G = 1/R$. Determine the range of those values.
- Graph V_o versus V_i to show the hysteresis for the values of R of part c) and give the hysteresis output values and input voltage jump point values. .

