


303H Fall 2011 – Midterm Exam Tu 11/01/11

Open book open notes but not open computers; 100 points total; if stuck go on to the next problem. Good luck

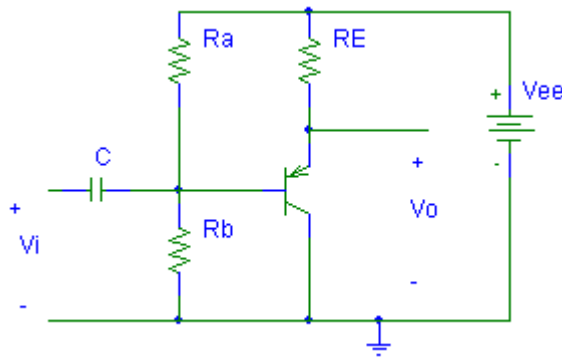1. (30 points, 15 min)

For this circuit, $\beta = 99$, $R_a = R_b = 1\text{Meg}$, $V_{ee} = 10$, $V_A = \infty$ and biased at $V_o = 8$

- Find the value of R_E and I_E .
- Give g_m , g_π and small signal open circuit voltage gain, $\frac{V_o(s)}{V_i(s)}$, for $C_\pi = 20\text{pFd.}$ (assume $C = \infty$)



2. (10 points, 5 min)


For the transfer function $\frac{V_o(s)}{V_i(s)} = \frac{s(s^2+4)}{(s+3)(s+5)}$ give the poles and zeros.

3. (30 points, 15 min)

For the following circuit assume identical transistors, with $\beta = \frac{K_P W}{2 L} = 10^{-4} \text{ A/V}^2$,

$V_{TO}=1\text{V}$, $LAMBDA=\lambda=0.01$ and $V_{dd}=10\text{V}$,

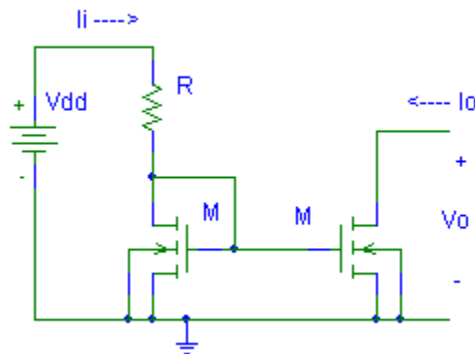- Find R for $V_{GS} = 4\text{V}$ and give the input current I_i .
- Give the output voltage, V_o , such that $I_o=I_i$.
- Find I_o if $V_o=7\text{V}$ and again if $V_o=2\text{V}$.



4. (30 points, 15 min)

For the following circuit the op-amp has zero input currents and gain k , $V_o = kV_d$.

- Assuming the gain k is finite (but independent of s), find the input admittance, $y = I/V$, in terms of C , $G_1=1/R_1$, $G_2=1/R_2$, and k .
- Let k become infinite and give y . Comment on the result.

