

1. (50 points, BJT curves)

Run simultaneous DC curves for the BJT 2N3904 & 2N3906 of IC versus VCE for the npn and VEC for the pnp with IB as a parameter to get curves of the type of Figure 6.19 of p. 375.

For this you can use one current source Iin for the base currents into two F components with their outputs being IB for the two transistors (note the negative sign on the pnp IB). And one voltage source Vbias for the collector – emitter voltages.

Submit these curves for $0V_{bias} \leq 5$ in 0.1V steps nested with $0 \leq I_{in} \leq 90\mu A$ in 30uA steps.

2. Download the bicmos12 set. [These can be found by downloading from the course web page the transistor files bicmos12.olb and bicmos12.lib (or for PSpice 8 the two equivalent files bicmos12.slb & bicmos12.lib). These files may already be installed but if not install them on the computers or folders from which you will run Spice]

3. (50 points, NMOS curves)

For just the mnmosis transistor of the bicmos12 set do a DC run ID versus $0 \leq V_{DS} \leq 5$ with $0 \leq V_{GS} \leq 5$ incremented in 1V steps.

Submit both your circuit and the resulting curves.