

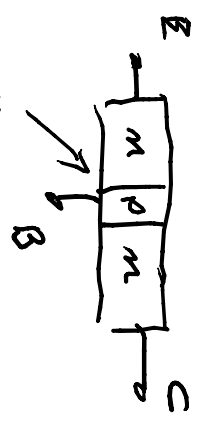
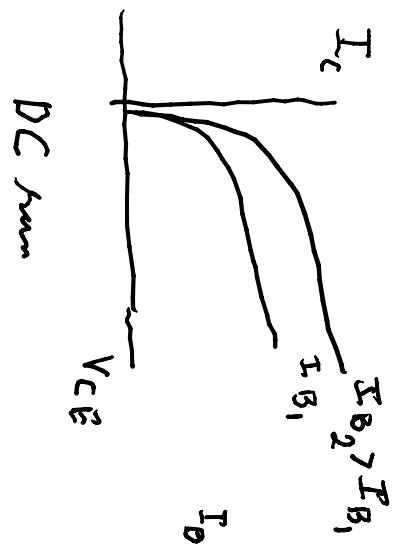
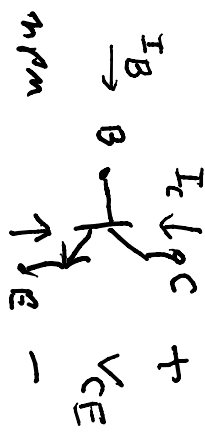
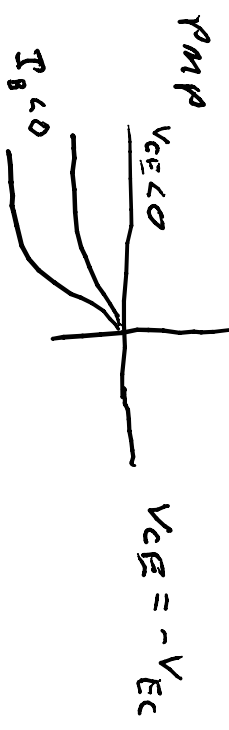


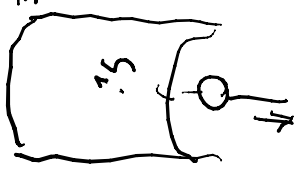
look at chapter 6 on BJT, p. 375 = npn curve



very thin

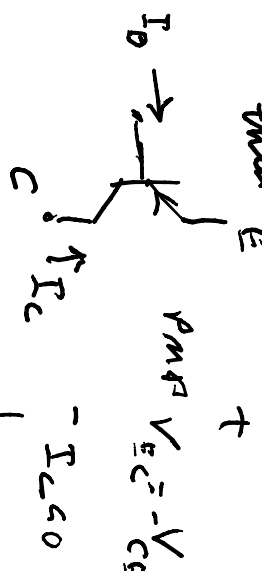

$V_{CE} = -V_{EC}$

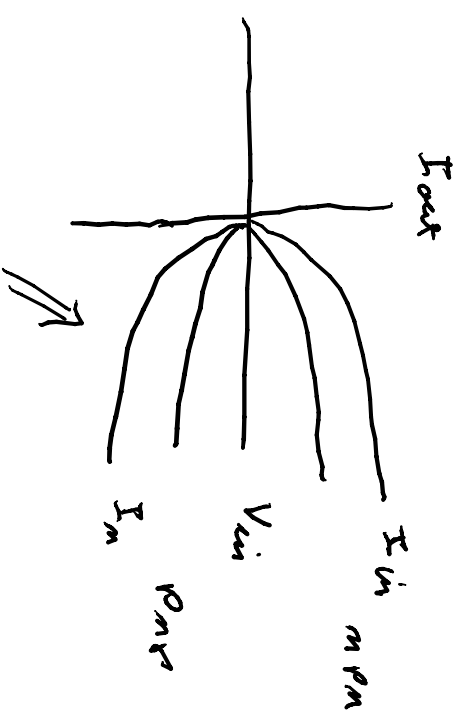


$F =$ current controlled current source




to get to PS in case of the m.p.m. see. and. reduce
load a project

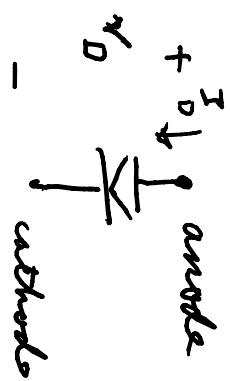Diodes P.150 = diode equation, actual stable diode



Power in = $V_D \times I_D$

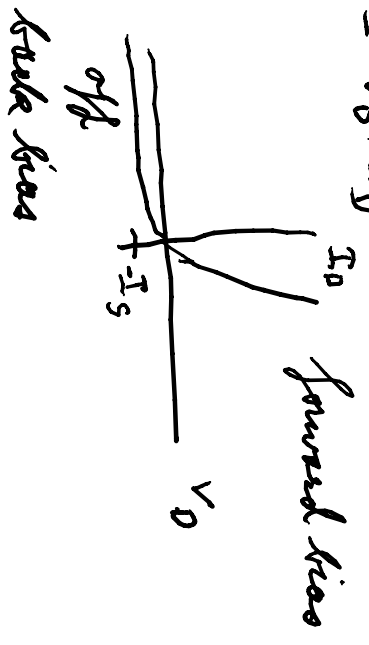Eq. (3.40) P.150 $V_D/V_T - 1$
 $I_D = I_S (e^{V_D/V_T} - 1)$




$V_T =$ thermal voltage = $\frac{kT}{181}$, $T =$ temperature

$K =$ Boltzmann's constant


$f =$ charge of an electron

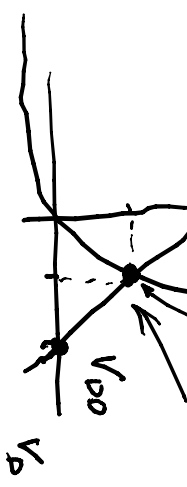P.180 \Rightarrow load lines
 $-I_Q = I_D$
 slope = $-G_L$



$Q =$ quiescent

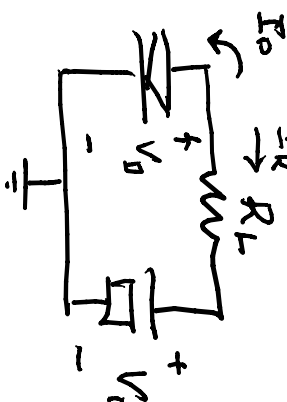$I_R = G_L (V_D - V_{DD}) \Rightarrow -I_R = -G_L V_D + G_L V_{DD}$



$I_R = -I_D$

$V_D = R_L I_R + V_{DD}$

$I_R = \frac{1}{R_L} (V_D - V_{DD})$
 $= -I_D$

$$I_D = I_S (e^{V_D / V_T} - 1) = -G_L (V_D - V_{DD})$$

Q point is $(V_D, I_D)_Q$ which solve this equation