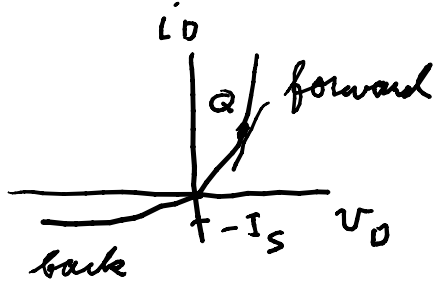


$i_D = \text{total}$, $I_D = \text{bias}$, $i_d = \text{signal}$

$i_D = I_S (e^{+v_D/V_T} - 1)$; $\left. \frac{\partial i_D}{\partial v_D} \right|_Q = \frac{I_S}{V_T} e^{v_D/V_T} = g_D$




Q
 $v_D = V_D$
= diode conductance




in forward region

$g_D = \frac{I_S}{V_T} e^{v_D/V_T} \approx \frac{I_D}{V_T}$, $V_T = \text{thermal voltage} = \frac{kT}{q}$





circuit for signal

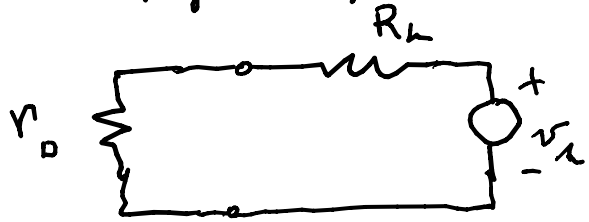

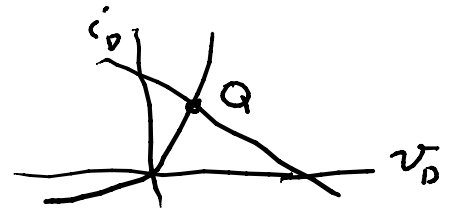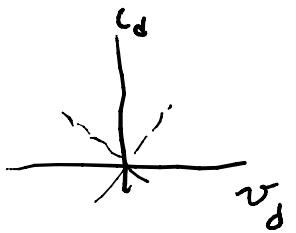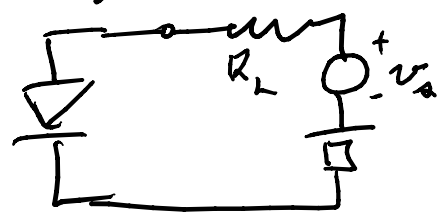full circuit $\approx 26 \text{ mV}$ @ room T



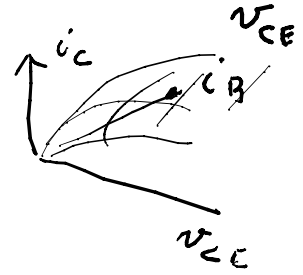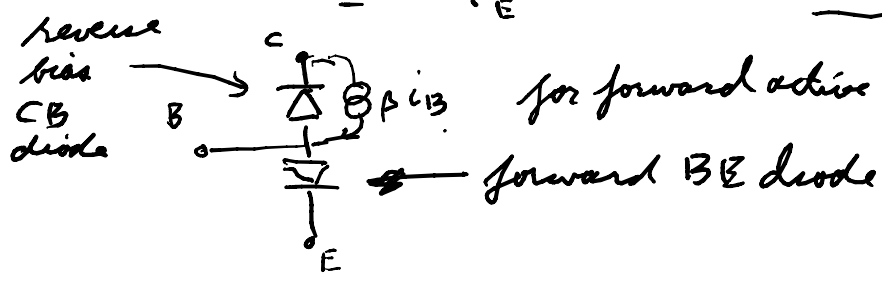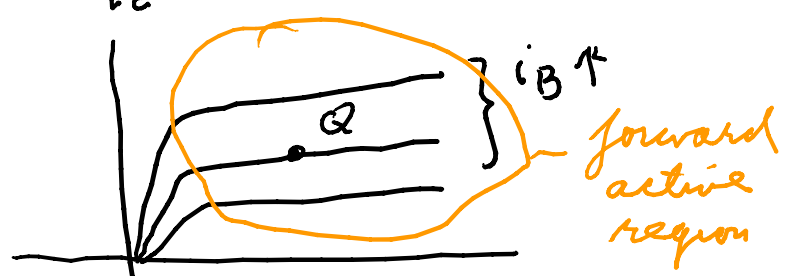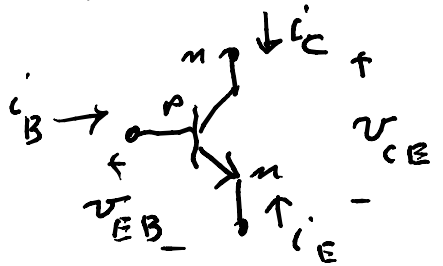Chapter 6 \Rightarrow BJT = bipolar junction transistor





$$i_c = f(v_{CE}, i_B) = f(v_{CE}, I_B) + \frac{\partial f}{\partial v_{CE}} \Big|_Q (v_{CE} - V_{CE}) + \frac{\partial f}{\partial i_B} \Big|_Q (i_B - I_B) + \frac{\partial^2}{\partial v_{CE} \partial i_B} \dots \text{high orders}$$

total bias Taylor series signals

$$i_c = I_C + g_0 v_{ce} + \frac{\partial i_c}{\partial i_B} \Big|_Q \cdot i_b + \dots \approx I_C + g_0 v_{ce} + \beta \cdot i_b$$

ignore

$$i_c = g_0 v_{ce} + \beta \cdot i_b$$

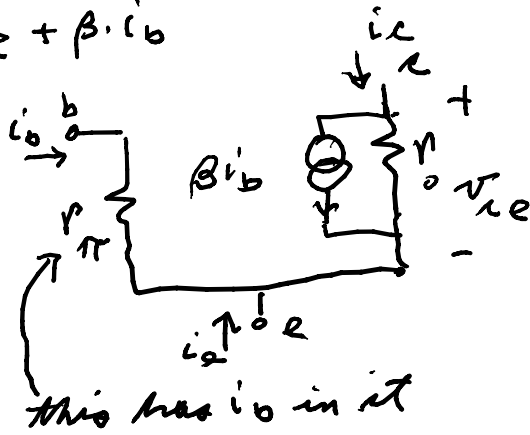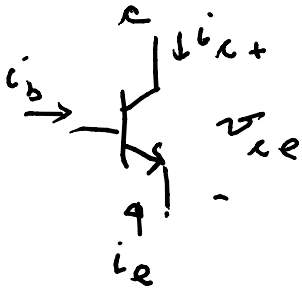

small signal equivalent circuit of an npn see p. 374 fig. 6.18

BE diode has emitter current i_E , use I_E
 $\frac{|I_E|}{V_T} = g_{D_{BE}}$

$$I_B + I_C + I_E = 0$$

$$I_B + \alpha(-I_E) + I_E = I_B + I_C + \frac{-I_C}{\alpha} = I_B + \left(\frac{\alpha-1}{\alpha}\right)I_C$$

$$\text{@ } Q, I_C = \beta I_B ; I_B + \left(\frac{\alpha-1}{\alpha}\right) \cdot \beta I_B = 0$$

$$I_B + (1-\alpha)I_E = 0 \Rightarrow I_E = \frac{1}{\alpha-1} I_B$$



$$\frac{|I_E|}{V_T} \cdot V_{BE} = \left(\frac{1}{1-\alpha} \cdot \frac{1}{V_T} \cdot I_B\right) V_{BE} = g_{\pi} \cdot V_{BE}$$


$$\Rightarrow g_{\pi} = \frac{I_B}{1-\alpha} \cdot \frac{1}{V_T} = \frac{\alpha}{1-\alpha} \cdot I_B \cdot \frac{1}{\alpha V_T}$$

$$I_C = \beta I_B = -\alpha I_E$$

$$\beta = \frac{\alpha}{1-\alpha}$$
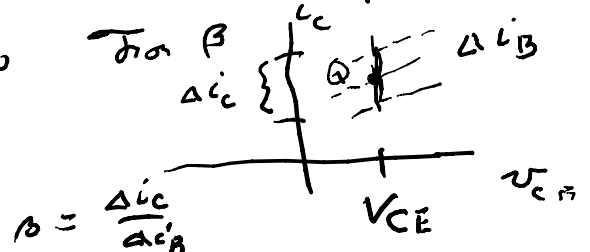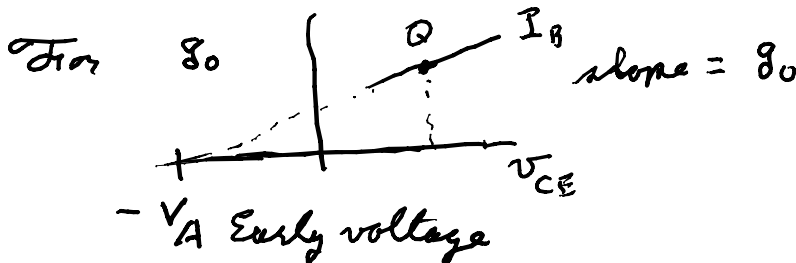
$$\approx \beta I_B \cdot \frac{1}{V_T} = \frac{I_C}{V_T} = g_{\pi}$$



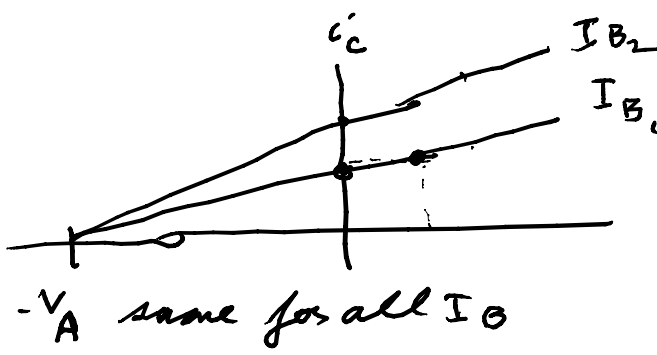

$$\left. \begin{array}{l} I_{B2} \\ I_{B1} \end{array} \right\} \text{slopes in forward active regions}$$

$$\text{slopes} \approx \frac{I_C}{V_A}$$

$$\text{''} \quad \frac{I_C}{V_A + V_{CE}}$$