
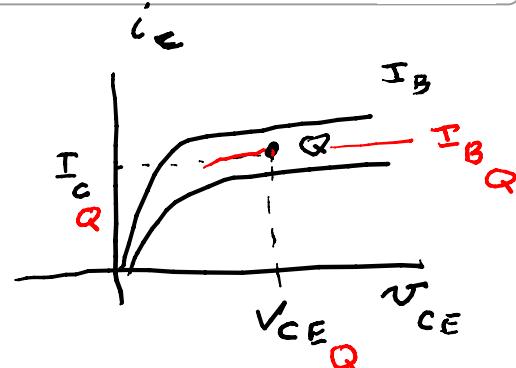


Biassing of BJT, npn


$$P_{402} \Rightarrow Q$$

$$V_{447}$$



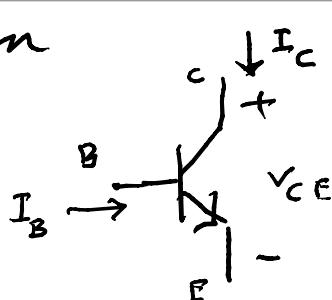


in forward active region


forward bias BE

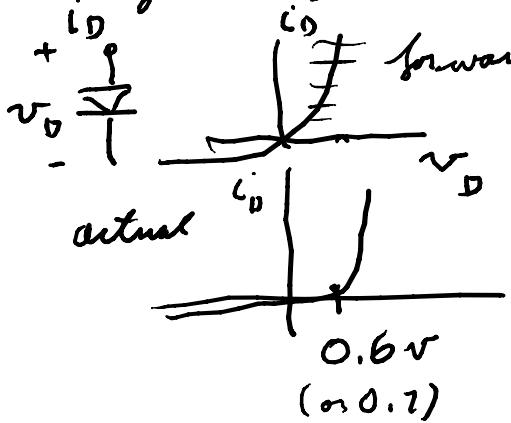

reverse bias CB

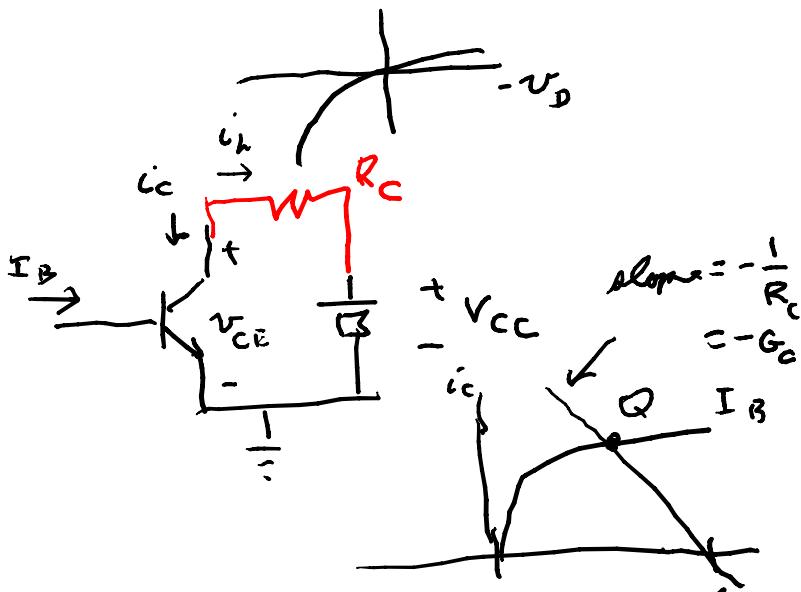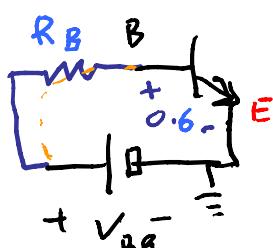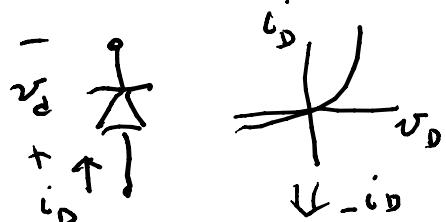

\Rightarrow

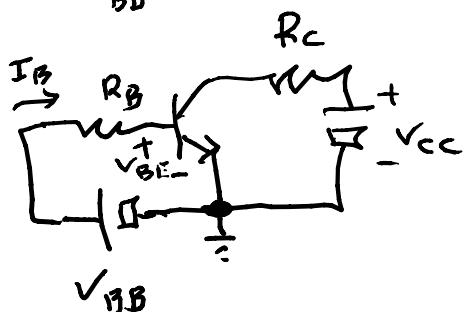

$$\Rightarrow 0 = -V_{BB} + R_B I_B + V_{BE} \quad \Rightarrow 0 = -V_{CC} + R_C I_C + V_{CE}$$


$\stackrel{0.6}{\parallel}$

$$\Rightarrow R_C = \frac{V_{CC} - V_{CEQ}}{I_C}$$


given V_{BB} & I_B at the Q point

$$\text{given } R_B = (V_{B13} - V_{BE}) / I_B$$

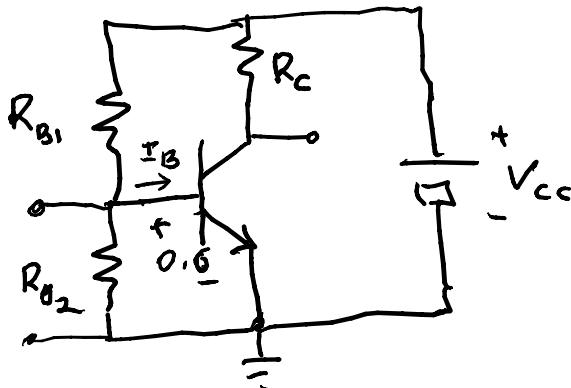To do with only one battery, given Q point



look at the base bias

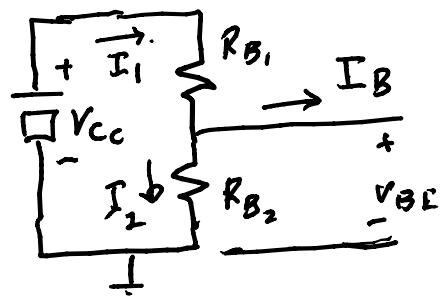

1) KCL: $I_1 = I_B + I_2$, $V_{BE} = R_{B2} I_2$, Ohm's law


2) $= I_B + \frac{V_{BE}}{R_{B2}}$

3) KVL: $0 = -V_{CC} + R_{B1} I_1 + V_{BE}$

4) $V_{CC} - V_{BE} = R_{B1} (I_B + V_{BE}/R_{B2}) = R_{B1} I_B + V_{BE} \cdot \frac{R_{B1}}{R_{B2}}$

Here have 1 eq. in 2 unknowns R_{B1} & R_{B2} so
since $V_{CC} - V_{BE}$ is limited, so have "constraints."
nice for PSpice PARAM part use.


small signal equivalent comes from

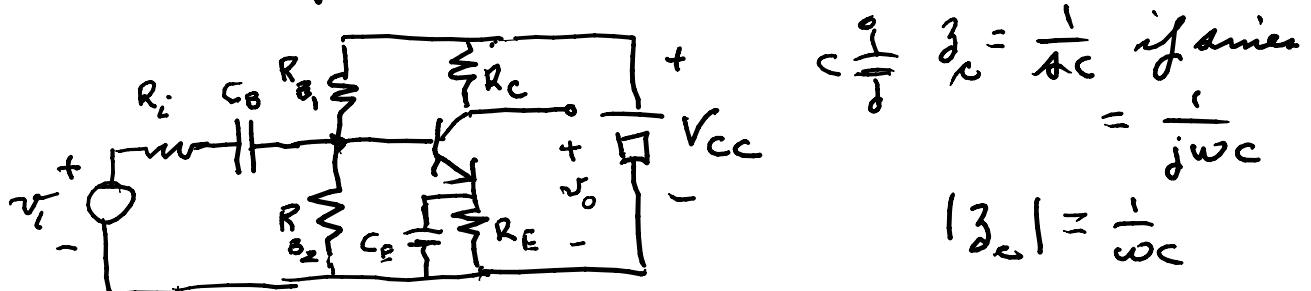

for C_B & C_E choose large so they
are shorts for signal frequencies
& R_{B1} & R_{B2} are large ($10\text{M}\Omega$ or so)

$$C \frac{d}{dt} \beta_c = \frac{1}{j\omega C} \text{ if since } \\ = \frac{1}{j\omega C} \\ |\beta_c| = \frac{1}{\omega C}$$

$\propto \frac{1}{\omega C}$

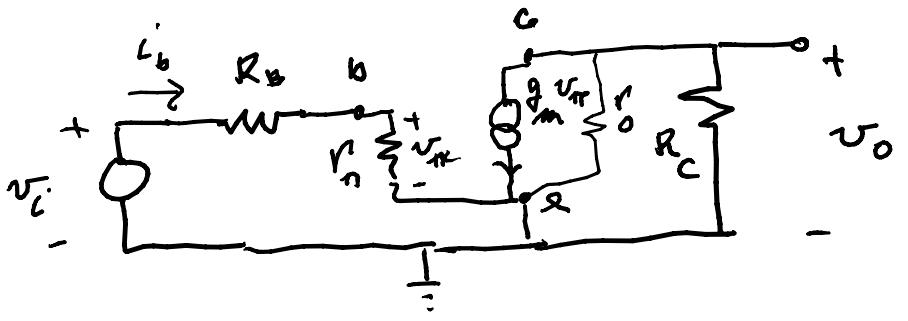

R. 410

$$g_m = \frac{I_C}{V_T}, V_T = \text{therm voltage}$$

$$g_o = \frac{I_C}{V_A} = \frac{1}{r_o}$$

$$g_{\pi} = \frac{g_m}{\beta} = \frac{1}{r_{\pi}}$$

gives gain $\frac{v_o}{v_i}$ for small signals

$$v_i = R_B i_b + r_{\pi} i_b = (R_B + r_{\pi}) i_b \Rightarrow i_b = \frac{v_i}{R_B + r_{\pi}}$$

$$v_{\pi} = r_{\pi} \cdot i_b = \frac{r_{\pi}}{R_B + r_{\pi}} \cdot v_i \Rightarrow g_m v_{\pi} = \frac{g_m r_{\pi}}{R_B + r_{\pi}} \cdot v_i$$

$$R_o = \text{"output"} = \frac{r_o R_c}{r_o + R_c}; \quad v_o = -(g_m v_{\pi}) \times \frac{r_o R_c}{r_o + R_c}$$

$$\frac{v_o}{v_i} = - \frac{g_m r_{\pi}}{R_B + r_{\pi}} \cdot \frac{r_o R_c}{r_o + R_c} = A_v = \text{voltage gain}$$

$$\text{if } r_o = \frac{V_A}{I_C} \text{ is large then } A_v \approx - \frac{g_m}{1 + R_B/r_{\pi}} \cdot R_c \approx - g_m R_c$$

$|A_v|$ can be large