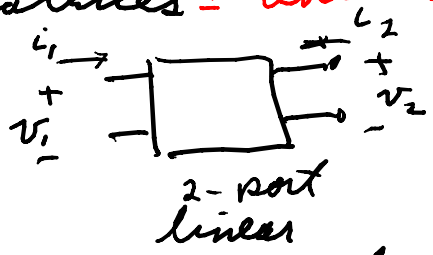


MOS Transistors = Chapter 5


Y matrices = admittance matrix (small signal linearized)



$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = i = Yv = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$


Equivalent circuits

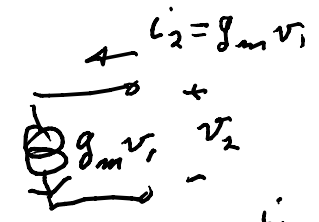MOS Ex 1:  $Y = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix} \Rightarrow \begin{matrix} i_1 = 0 \\ v_1 = 0 \\ i_2 = -a \end{matrix}$





BJT Ex 2:  $Y = \begin{bmatrix} y_{11} & 0 \\ g_m & y_{22} \end{bmatrix} \Rightarrow$
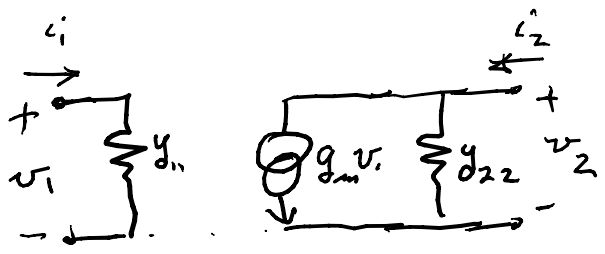
$$i_1 = y_{11} v_1 + 0 \cdot v_2 \Rightarrow \begin{matrix} + \\ v_1 \\ - \end{matrix} \left. \begin{matrix} \\ \\ \end{matrix} \right\} y_{11} (v) \\ i_2 = g_m v_1 + y_{22} v_2$$



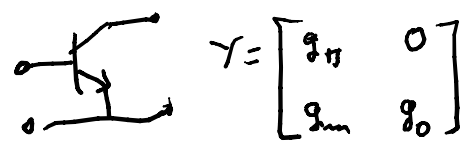
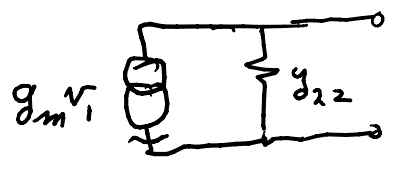
$$Y = \begin{bmatrix} y_{11} & 0 \\ g_m & y_{22} \end{bmatrix}$$




$$g_m = \frac{I_c}{V_T}, \quad g_o = \frac{I_c}{V_A}$$

Ex 3:  $Y = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$

$$g_{m1} = \frac{g_m}{\beta}$$

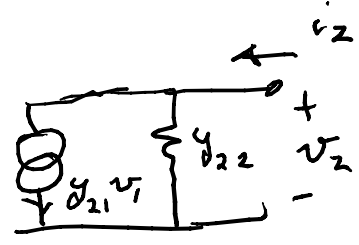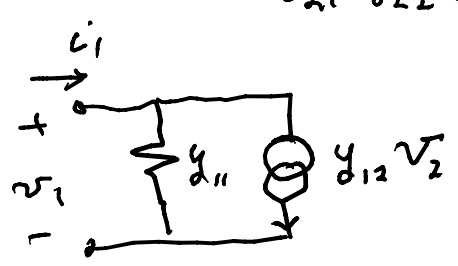

$\Pi$  equivalent

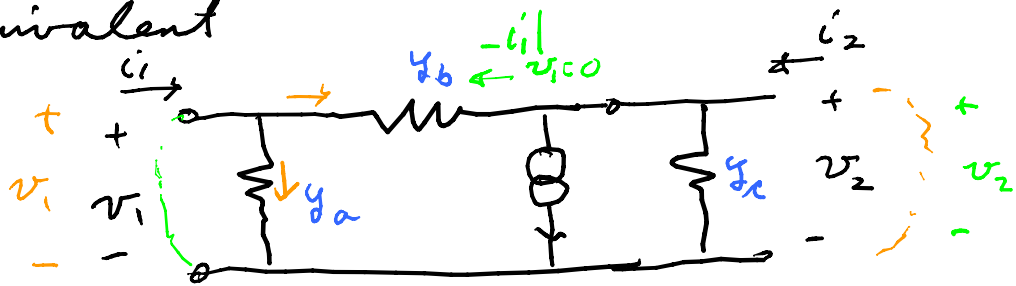

$$y_{11} = \left. \frac{i_1}{v_1} \right|_{v_2=0} = y_a + y_b$$

(a short on port 2)


$$y_{12} = \left. \frac{i_1}{v_2} \right|_{v_1=0} = -y_b$$

(a short on port 1)


$\therefore$  given  $Y$ :  $y_b = -y_{12}$ ,  $y_a = y_{11} - y_b = y_{11} + y_{12}$

for  $y_c$ :  $y_{22} = \left. \frac{i_2}{v_2} \right|_{v_1=0} = y_c + y_b \Rightarrow y_c = y_{22} - y_b = y_{22} + y_{12}$

$y_d$ :  $y_{21} = \left. \frac{i_2}{v_1} \right|_{v_2=0} = -y_b + y_d \Rightarrow y_d = y_{21} + y_b = y_{21} - y_{12}$

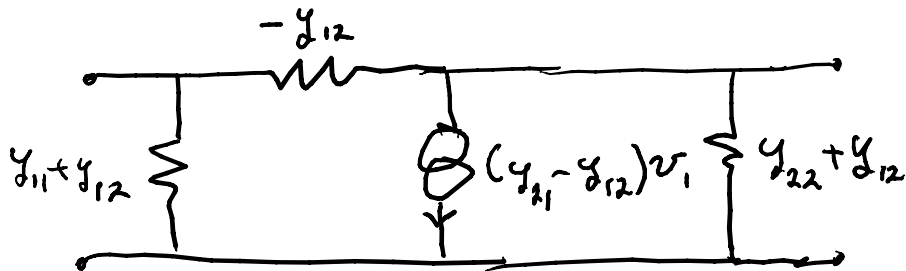

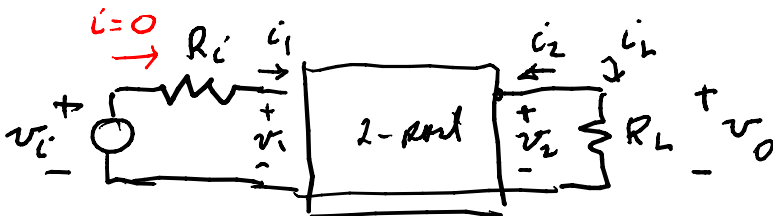$\Pi$  equivalent circuit of a linear 2-port with  $Y$  matrix



find  $\frac{v_o}{v_i}$

$$Y = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix}$$

KCL  $i_1 = -i_2 = G_L v_o = G_L v_2$

$-G_L v_o = g_m v_i \Rightarrow \frac{v_o}{v_i} = -R_L g_m = A_v$

$i_2 = g_m v_1$  (from  $Y$ )  $\Rightarrow i_2 = g_m v_i$

$i_1 = 0$

for  $Y = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$

1)  $v_i = R_i i_i + v_i = R_i (y_{11} v_i + y_{12} v_o) + v_i$

2)  $v_o = -R_L i_2 = -R_L (y_{21} v_i + y_{22} v_o)$  as  $v_2 = v_o$

1)  $\Rightarrow$  3)  $v_i = R_i (y_{11} v_i + y_{12} v_o) + v_i$

2)  $\Rightarrow$  4)  $R_L y_{21} v_i = (-R_L y_{22} - 1) v_o \Rightarrow v_i = \frac{-(1 + R_L y_{22})}{R_L y_{21}} v_o$

4)  $\Rightarrow$  3)

$$v_i = \left\{ R_i y_{11} + 1 \right\} \left[ \frac{-(1 + R_L y_{22})}{R_L y_{21}} \right] + R_i y_{12} v_o$$

$$= \frac{-R_i}{y_{21}} \left\{ (y_{11} + G_i)(G_L + y_{22}) - y_{12} y_{21} \right\} v_o$$

$$= \frac{-R_i}{y_{21}} (y_{11} G_L + y_{22} G_i + G_i G_L + \Delta_y) v_o$$

let  $\Delta_y = \det Y$   
 $= y_{11} y_{22} - y_{12} y_{21}$

$$\frac{v_o}{v_i} = - \frac{y_{21}}{R_i} \left( \frac{y_{11} G_L + y_{22} G_i + G_i G_L + \Delta_y}{y_{21}} \right)$$

(voltage gain of a loaded linear circuit)




ideal  $y_{11} = y_{22} = y_{12} = 0$   
 $\Delta_y = 0$




$$\frac{v_o}{v_i} = - \frac{y_{21}}{R_i} \cdot \frac{1}{G_i G_L} = - \frac{y_{21}}{G_L}$$

(as  $R_i G_i = 1$ )

check as  $y_{21} = I_{on} / V_{gs}$

for MOS transistors

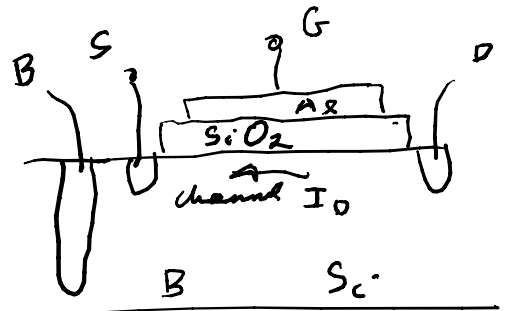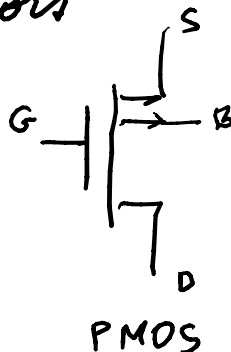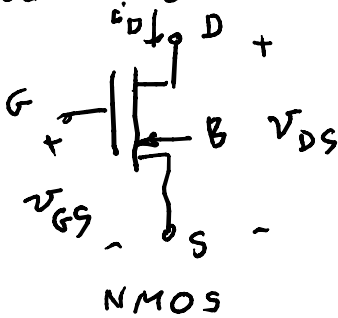

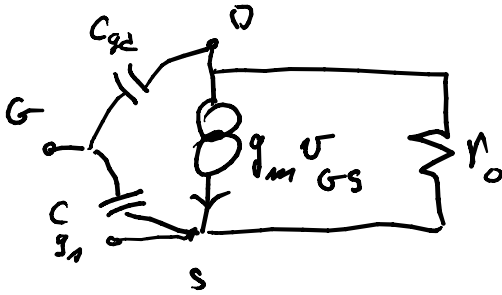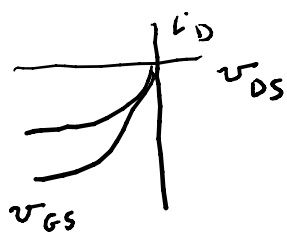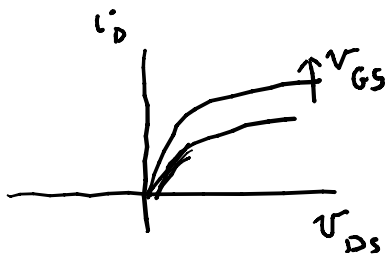

$$y = \begin{bmatrix} 0 & 0 \\ g_m & g_o \end{bmatrix} \begin{array}{l} \text{at DC} \\ \text{small} \\ \text{signal} \end{array}$$

$$\Rightarrow \begin{bmatrix} C_D & -C_D \\ -C_D + g_m & C_D + g_o \end{bmatrix} = Y(s)$$