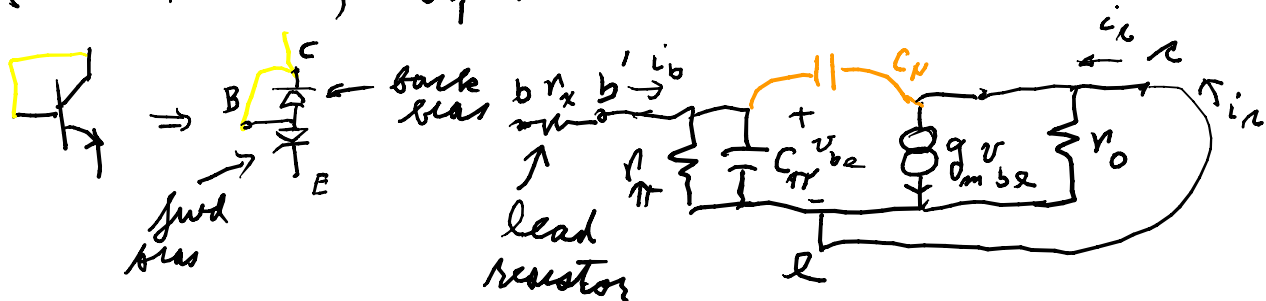


Hybrid- $\pi$  p. 708,  $f_T$  p. 709




make hybrid

$$\left. \frac{i_c}{i_b} \right|_{v_{ce}=0} = \beta(j\omega), \quad \omega=0 \Rightarrow \beta_0 = \left. \frac{i_c}{i_b} \right|_{\omega=0} \quad v_{be} = \frac{1}{g_{\pi} + sC_{\pi}} \cdot i_b$$


$$\beta(s) = \frac{g_m / g_{\pi}}{1 + sC_{\pi} / g_{\pi}} = \frac{\beta_0}{1 + s \frac{C_{\pi}}{g_{\pi}}} \quad i_c = g_m v_{be} = \frac{g_m}{g_{\pi} + sC_{\pi}} \cdot i_b$$

$$|\beta(j\omega)| = \frac{\beta_0}{\sqrt{1 + \omega^2 C_{\pi}^2 / g_{\pi}^2}} = 1 \quad \uparrow \text{in } \omega$$



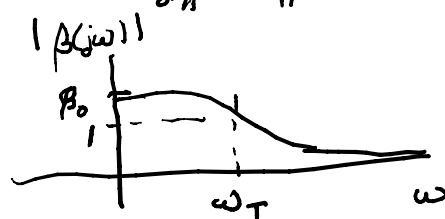



$$\beta_0^2 = 1 + \omega_T^2 C_{\pi}^2 / g_{\pi}^2 \approx \omega_T^2 = \frac{g_m \beta_0}{C_{\pi}} = \frac{(g_m / \beta_0) \beta_0}{C_{\pi}} = \frac{g_m}{C_{\pi}}$$

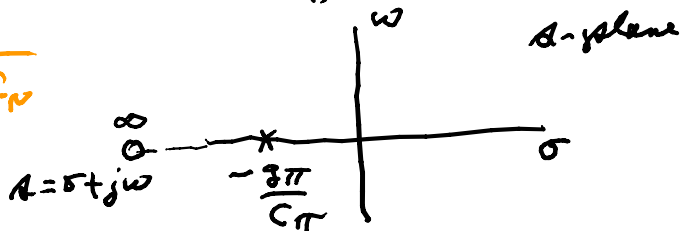with  $C_{\mu} \Rightarrow f_T = \frac{1}{2\pi} \cdot \frac{g_m}{C_{\pi} + C_{\mu}}$






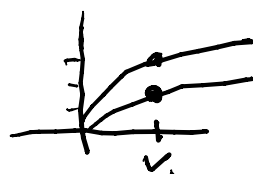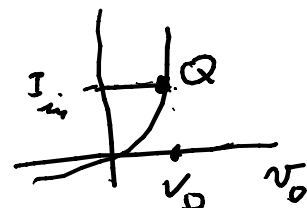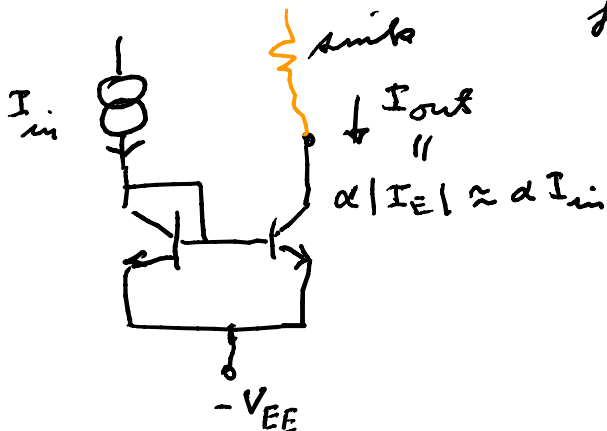Current mirror p. 452 & 534, analysis for base current present



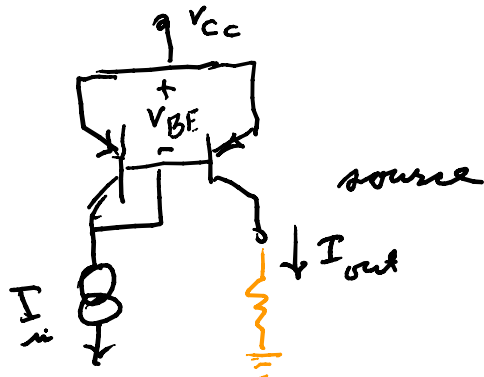

# MOS transistors

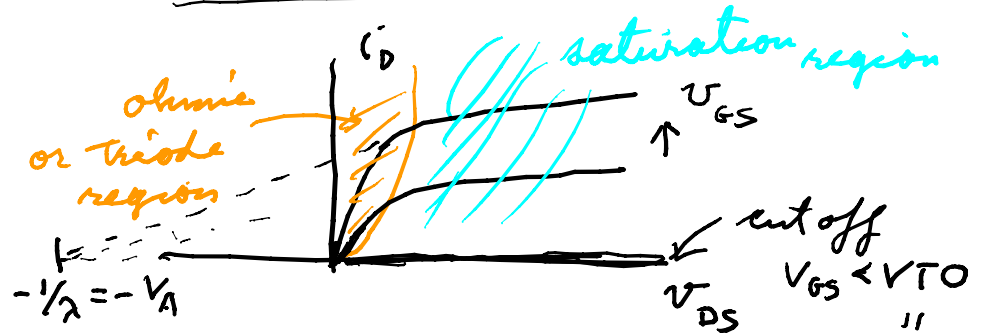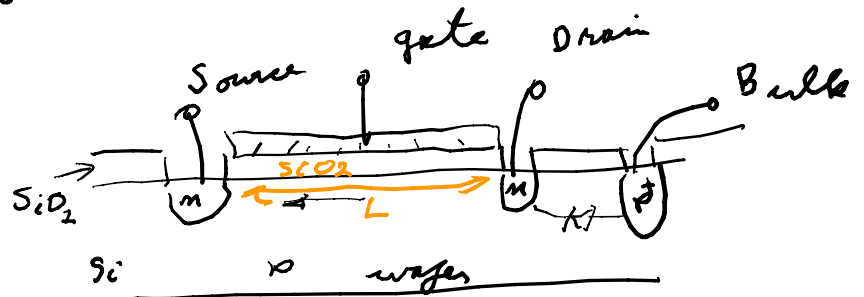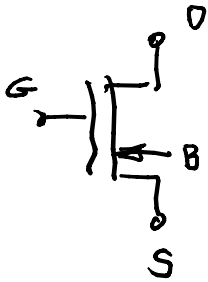

p. 250

fig. 5.13

assume tie off BS diode  
i.e. short B to S

$$i_D = \left(\frac{K_P}{2}\right) \cdot \frac{W}{L} \times \begin{cases} 0 & V_{GS} \leq V_{T0} \text{ (cut-off)} \\ \left\{ 2(V_{GS} - V_{T0})V_{DS} - V_{DS}^2 \right\} (1 + \lambda V_{DS}) & 0 \leq V_{DS} \leq V_{GS} - V_{T0} \text{ (ohmic)} \\ (V_{GS} - V_{T0})^2 (1 + \lambda V_{DS}) & V_{GS} - V_{T0} \leq V_{DS} \text{ (saturation)} \end{cases}$$

LAMBDA

$K_P$ ,  $V_{T0}$ ,  $\lambda$  are Spice parameters (also  $\gamma = \text{GAMMA}$ )

if  $V_{BS} \neq 0$ , then  $V_{T0} \Rightarrow V_{th}$  = threshold voltage

see p. 324

$$V_{th} = V_{T0} + \gamma \left[ \sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f} \right]$$

eq. (5.107)

$$2\phi_f \approx 0.6$$

cancel if  $V_{SB} = 0$

Small signal  $\pi$  equivalent  
 $V_{SB} = 0$

