
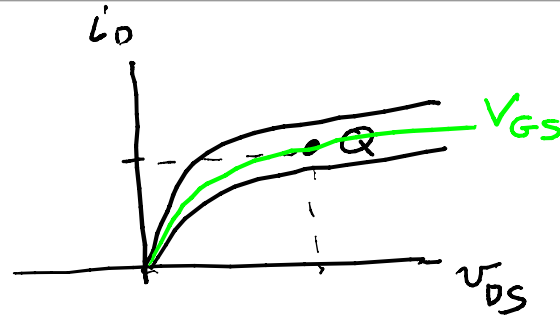


## Biasing MOS

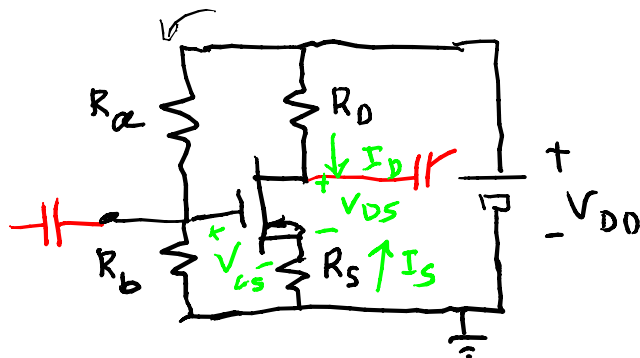

$Q \Rightarrow I_D, V_{GS}, V_{DS}$  ( $V_{TO}, K_P, \lambda$ )



$$V_{GS} = R_S I_D + \frac{R_b}{R_a + R_b} V_{DD}$$

$$V_{DS} = V_{DD} - R_D I_D - R_S I_D \\ = V_{DD} - (R_D + R_S) I_D$$

normally bias in saturation

$$V_{DS} > V_{GS} - V_{TO}$$

also usually given  $A_v = -g_m R_L$

$$= -g_m R_D$$

Ex:  $I_D = 2 \text{ ma}$ ,  $V_{GS} = 4 \text{ V}$ ,  $V_{TO} = 1$ ;  $V_{DD} = 9$

choose  $R_S = 1 \text{ k}\Omega \Rightarrow V_S = R_S I_D = 1 \times 10^3 \times 2 \times 10^{-3} = 2 \text{ V}$

$\therefore V$  at top of  $R_b = 6 \text{ V}$ ;  $\frac{R_b}{R_a + R_b} \cdot V_{DD} = 6 = \frac{1}{\frac{R_a}{R_b} + 1} \cdot 9$

$$\Rightarrow 6 + 6 \frac{R_a}{R_b} = 9 \Rightarrow \frac{R_a}{R_b} = \frac{1}{2}$$

$$R_b = 2 R_a$$

choose  $R_a = 10 \text{ M}\Omega \Rightarrow R_b = 20 \text{ M}\Omega$

$$V_{DS} = V_{DD} - R_D I_D - R_S I_D = 9 - 2 - R_D I_D = 7 - 2 \times 10^{-3} R_D = 7 - 2 \times 10^{-3} \frac{A \cdot V}{g_m}$$



assume that  $R_D = 1 \text{ k}\Omega \Rightarrow V_{DS} = 9 - 2 = 7 \text{ V}$

$\max R_D \Rightarrow V_{DS} \geq V_{GS} - V_{TO} \Rightarrow 4 - 1 = 3, V_{DD} = 9, V_{DD} - V_{GS} = 6$


$I_D = 2 \text{ ma} \Rightarrow R_D I_D \leq 6$

$R_D \times 2 \times 10^{-3} = 6 \Rightarrow R_D = \frac{6}{2} \text{ k}\Omega = 3 \text{ k}\Omega$

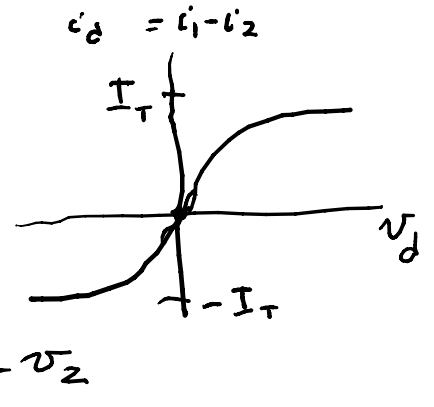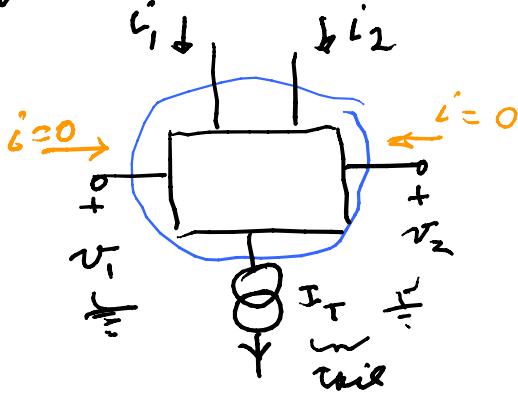Direct coupled  
 $\Rightarrow$  differential pair, p. 588




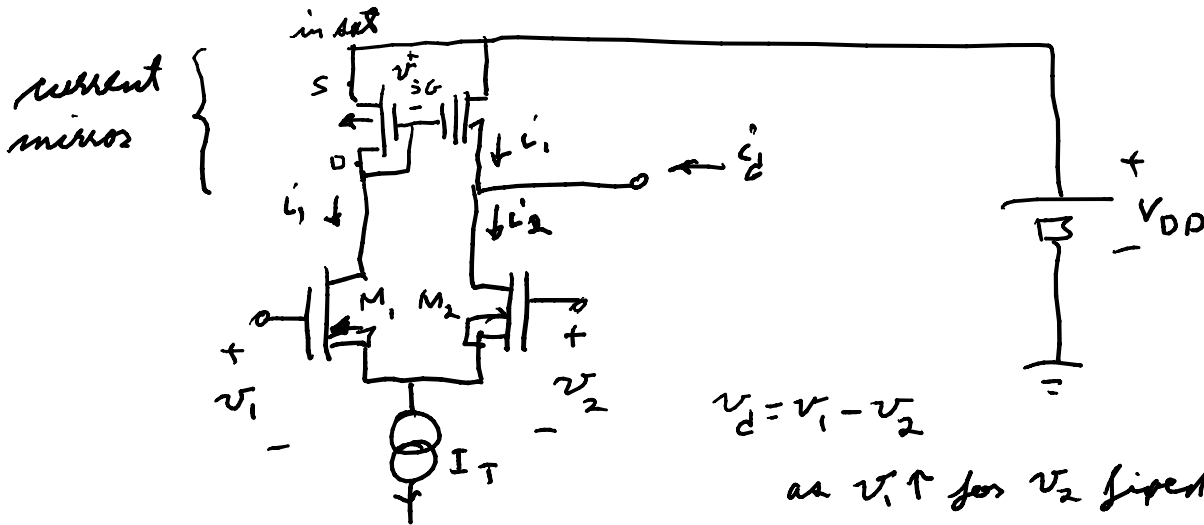KCL:  $0 = i_1 + i_2 - I_T \Rightarrow i_1 + i_2 = I_T$





NMOS differential pair

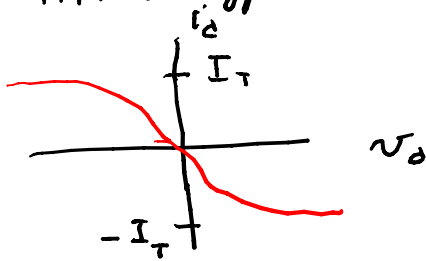as  $v_1 \uparrow$  for  $v_2$  fixed,  $v_D \uparrow \& i_1 \uparrow, i_2 \downarrow$   
 as  $i_1 + i_2 = \text{constant}$   
 $\& i_D \downarrow$




How to make  $I_T$

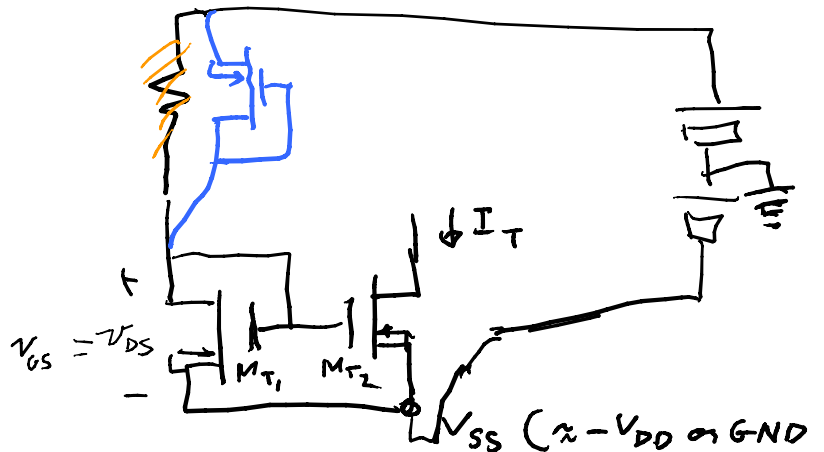

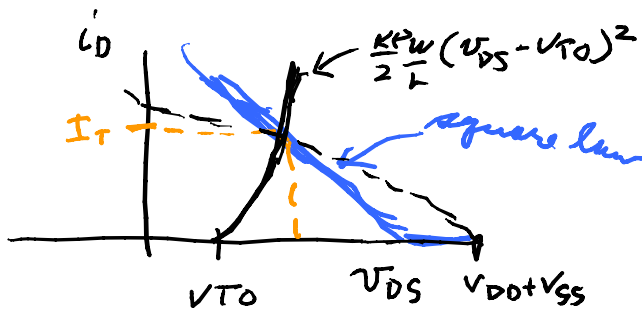


here  $v_{DS} = v_{GS}$  for  $M_{T1}$   
 $> v_{GS} - V_{T0}$  as  $V_{T0} > 0$   
 means  $M_{T1}$  is in saturation  
 $i_D = \frac{k_p W}{2 L} (v_{GS} - V_{T0})^2$  if  $v_{GS} = v_{DS} > 0$   
 $= \frac{k_p W}{2 L} (v_{DS} - V_{T0})^2$

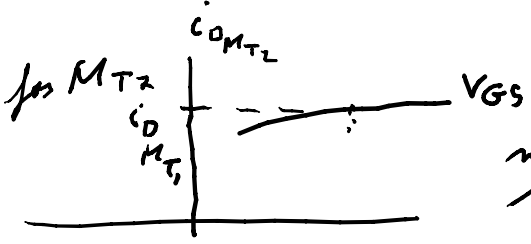but if  $v_{DS} = v_{GS} \leq V_{T0}$   $M_{T1}$  is off



need to keep  
 in saturation  
 then  $i_{D, M_{T1}}$

BJT version

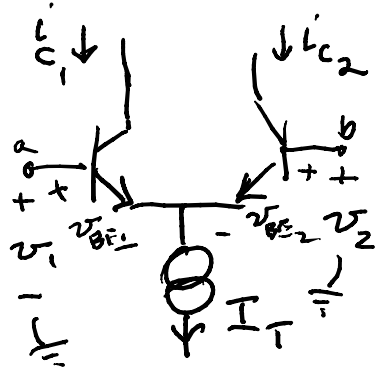

$$v_{d, d} = v_d = v_1 - v_2 = v_{BE1} - v_{BE2}$$

$$i_d = i_2 - i_1$$

$$i_{c1} = I_S e^{v_{BE1}/V_T}, \quad i_{c2} = I_S e^{v_{BE2}/V_T}$$


$$i_d = i_{c2} - i_{c1} = I_S (e^{v_{BE2}/V_T} - e^{v_{BE1}/V_T}) = I_S e^{v_{BE2}/V_T} (1 - e^{(v_{BE1} - v_{BE2})/V_T})$$

$$= I_S e^{v_{BE2}/V_T} (1 - e^{v_d/V_T})$$

$$I_T = i_{c2} + i_{c1} = I_S e^{v_{BE2}/V_T} (1 + e^{v_d/V_T})$$

$$\frac{i_d}{I_T} = \frac{1 - e^{v_d/V_T}}{1 + e^{v_d/V_T}} = \tanh\left(\frac{-v_d}{2V_T}\right) \Rightarrow i_d = I_T \tanh\left(\frac{-v_d}{2V_T}\right)$$
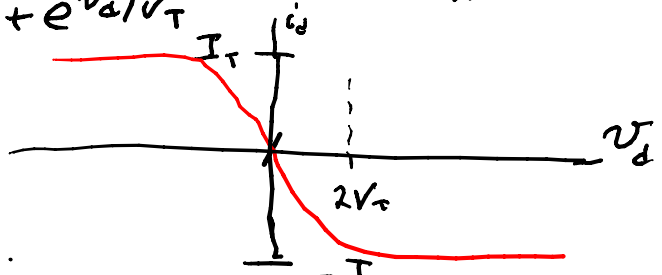
$$\text{as } \tanh x = \frac{e^x - e^{-x}}{e^x + e^{-x}}$$



$$\frac{d \tanh x}{dx} = \frac{e^x + e^{-x}}{e^x + e^{-x}} - \frac{(e^x - e^{-x})(e^x - e^{-x})}{(e^x + e^{-x})^2} = 1 - \tanh^2 x$$