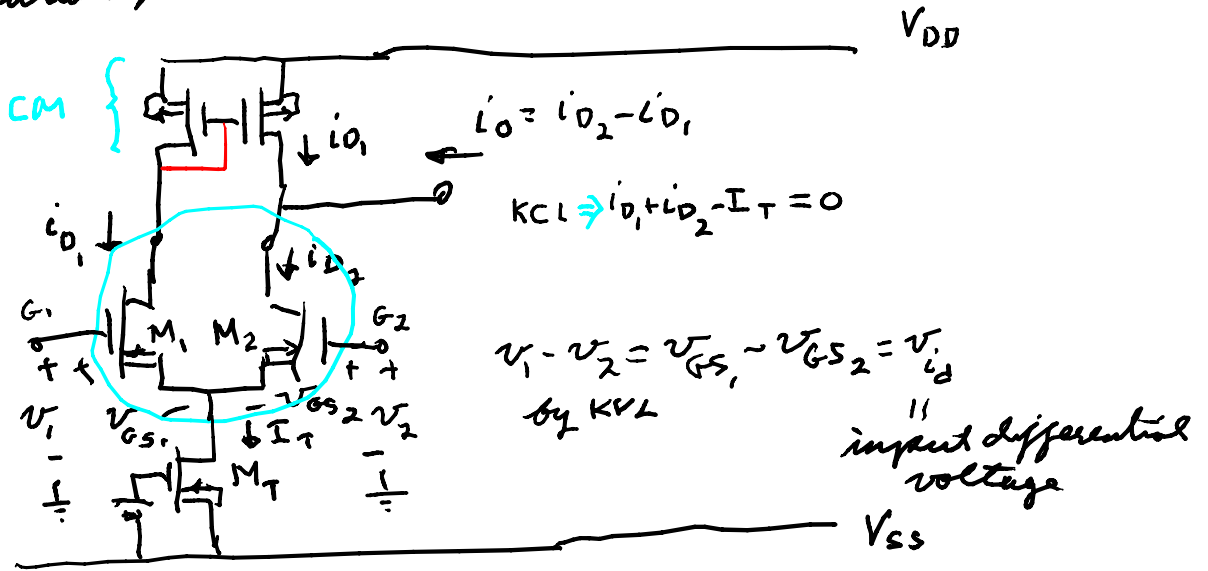


Differential pair

corrected

diff. pr.

tail



assume $M_1 = M_2$ are in saturation & $\lambda = 0$

$$i_{D1} = \frac{K_P}{2} \cdot \frac{W}{L} (v_{GS1} - V_{th})^2 = \beta (v_{GS1} - V_{th})^2$$

$$i_{D2} = \frac{K_P}{2} \cdot \frac{W}{L} (v_{GS2} - V_{th})^2 = \beta (v_{GS2} - V_{th})^2$$

both $V_{th1} = V_{th2} = V_{th}$

$$+\sqrt{\frac{i_{D1}}{\beta}} = v_{GS1} - V_{th}, \quad +\sqrt{\frac{i_{D2}}{\beta}} = v_{GS2} - V_{th}$$

$+\sqrt{\quad}$ as M_1 & M_2 assumed on in sat

$$0): \sqrt{\frac{i_{D2}}{\beta}} - \sqrt{\frac{i_{D1}}{\beta}} = v_{id}$$

desire i_o vs v_{id}

$$1): i_o = i_{D2} - i_{D1} \quad 2): I_T = i_{D1} + i_{D2}$$

$$2)+1) = 3): I_T + i_o = 2i_{D2} \quad 2)-1) = 4): I_T - i_o = 2i_{D1}$$

$$\sqrt{3) = 5): \sqrt{\frac{i_{D2}}{\beta}} = \sqrt{\frac{I_T + i_o}{2\beta}} \quad \sqrt{4) = 6): \sqrt{\frac{i_{D1}}{\beta}} = \sqrt{\frac{I_T - i_o}{2\beta}}$$

$$0) = 6) - 5) \Rightarrow 7): v_{id} = \sqrt{\frac{I_T + i_o}{2\beta}} - \sqrt{\frac{I_T - i_o}{2\beta}}$$

$$7)^2 = 8): v_{id}^2 = \frac{I_T + i_o}{2\beta} + \frac{I_T - i_o}{2\beta} - 2\sqrt{\frac{I_T^2 - i_o^2}{4\beta^2}} = \frac{I_T}{\beta} - \sqrt{\frac{I_T^2 - i_o^2}{\beta^2}}$$

$$\text{rearrange } \sqrt{\frac{I_T^2 - i_o^2}{\beta}} = \frac{I_T}{\beta} - v_{id}^2$$

$$8)^2 = 9): \frac{I_T^2 - i_0^2}{\beta^2} = \left(\frac{I_T}{\beta}\right)^2 + v_{id}^4 - 2\frac{I_T}{\beta} v_{id}^2$$

rearrange & cancel $(I_T/\beta)^2$

$$10): \frac{i_0^2}{\beta^2} = 2\frac{I_T}{\beta} v_{id}^2 - v_{id}^4$$

$$\sqrt{10} = 11): i_0 = \pm \beta v_{id} \sqrt{2\frac{I_T}{\beta} - v_{id}^2}$$


when M_1 & M_2 saturated
needs - sign as $i_0 \uparrow$ as $v_{id} \uparrow$

i_0 becomes max @ $\frac{di_0}{dv_{id}} = 0$;

$$12): \frac{di_0}{dv_{id}} = -\beta \sqrt{2\frac{I_T}{\beta} - v_{id}^2} - \beta v_{id} \cdot \frac{1}{2} \cdot \frac{-2v_{id}}{\sqrt{2\frac{I_T}{\beta} - v_{id}^2}} = \frac{-2I_T + \beta(v_{id}^2 + v_{id}^2)}{\sqrt{2\frac{I_T}{\beta} - v_{id}^2}}$$

$$= 0 \Rightarrow v_{id}^2 = \frac{I_T}{\beta} \Rightarrow i_0 = \beta \sqrt{\frac{I_T}{\beta}} \sqrt{2\frac{I_T}{\beta} - \frac{I_T}{\beta}} = I_T$$

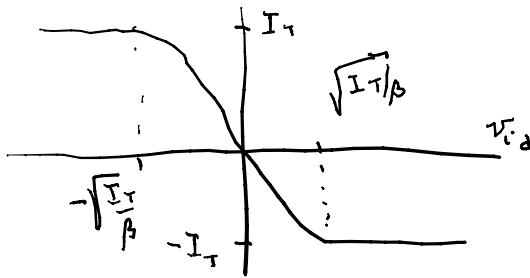\therefore all current is one of the transistors which turns the other off for $v_{id}^2 > \frac{I_T}{\beta}$



$$i_0 = -\beta v_{id} \sqrt{2\frac{I_T}{\beta} - v_{id}^2}, \quad v_{id}^2 \leq \frac{I_T}{\beta}$$

$$= +I_T \text{ for } v_{id} < -I_T/\beta$$

$$= -I_T \text{ for } v_{id} > I_T/\beta$$