
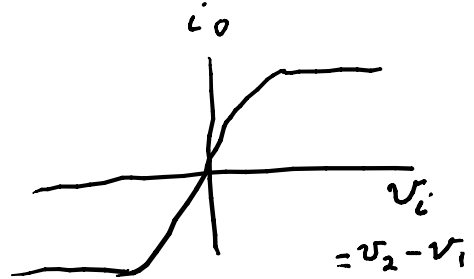


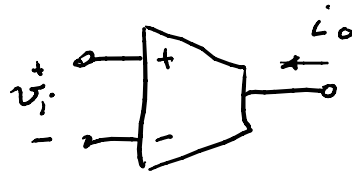Symbol  
OTA  
operational  
transconductance  
amplifiers



$$i_o = I_T f(v_i)$$


for the 4007

can use the breakout transistors in PSpice

MbreakN & MbreakP

read in the transistor models


using the OTA as a resistor

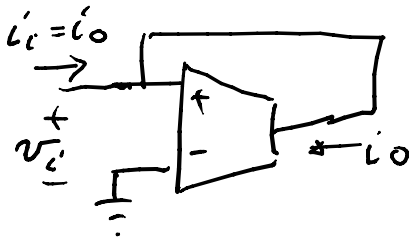



$$v_o = f(v_i) i_i =$$

$$i_i = f(v_i) =$$

⇒ curve  
of a resistor

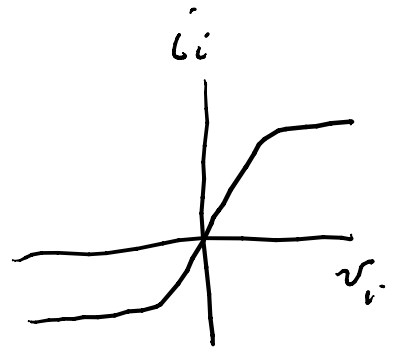


for the MOS = gives linear near origin

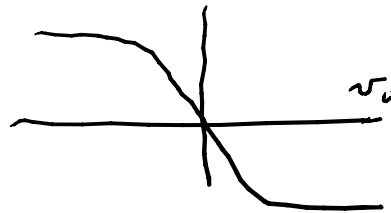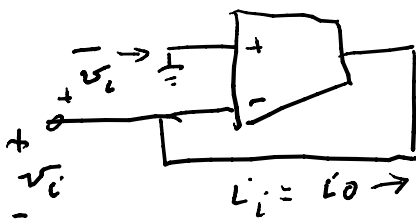


⇒ negative resistor

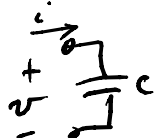How to make an inductor from OTA and a capacitor




$$i = C \frac{dv}{dt}$$

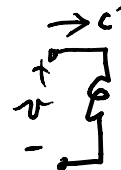

$$v = L \frac{di}{dt}$$

duals ( $v \leftrightarrow i$ )

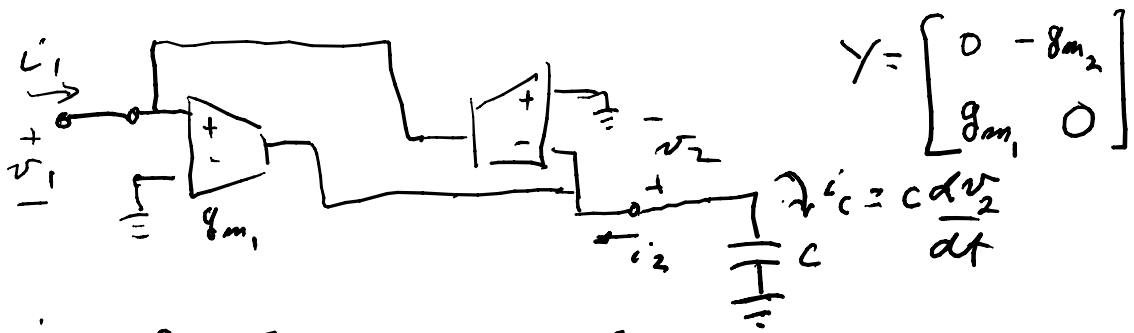

$$Y = \begin{bmatrix} 0 & -g_{m2} \\ g_{m1} & 0 \end{bmatrix}$$

1)  $i_1 = -g_{m2} v_2$  ;  $i_2 = -c \frac{dv_2}{dt} = g_{m1} v_1$  2) & 3)

4)  $\frac{di_1}{dt} = -g_{m2} \frac{dv_2}{dt} = (-g_{m2}) \left( -\frac{g_{m1}}{c} \right) v_1$


$v_1 = \frac{c}{g_{m1} g_{m2}} \cdot \frac{di_1}{dt} = h_{eq} \cdot \frac{di_1}{dt}$

$c = 1 \text{ pF}$

$g_{m1} = g_{m2} = 10^{-3}$

$h_{eq} = \frac{10^{-6}}{10^{-6}} = 1 \text{ k}\Omega$

Multiplies:

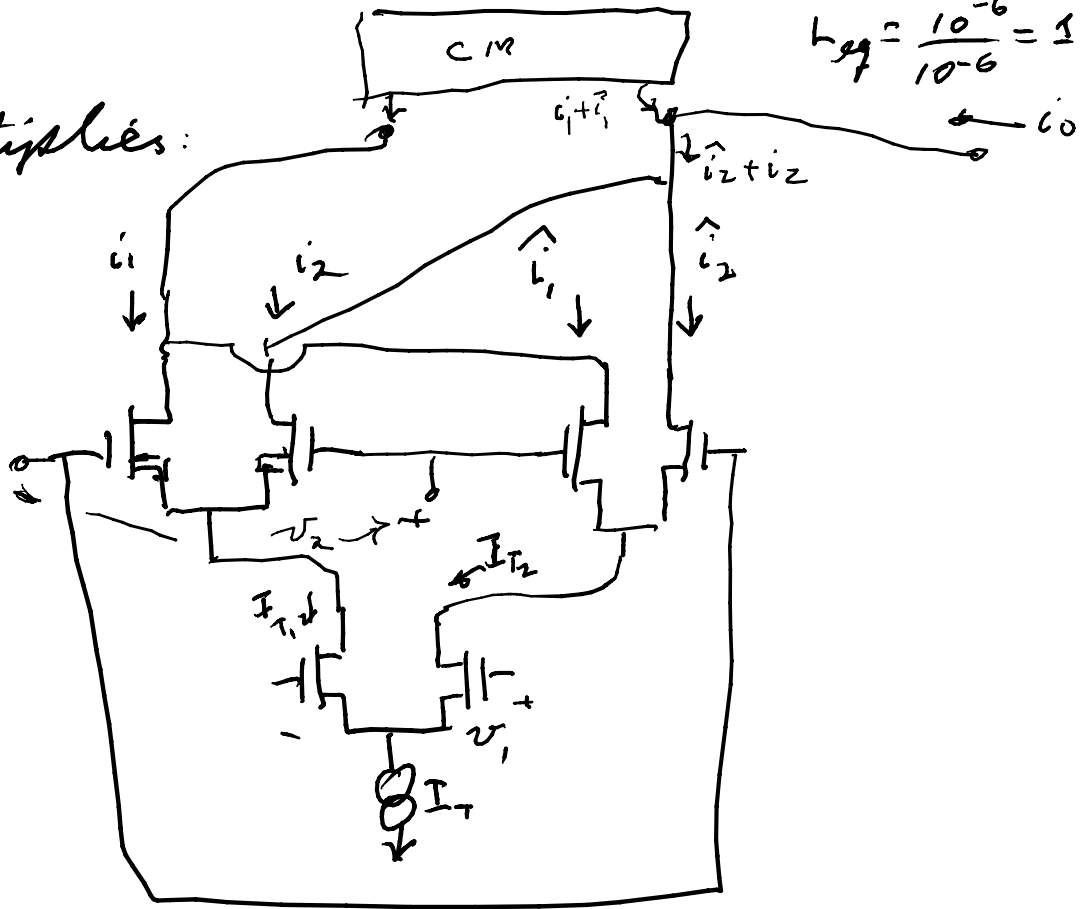

will give  $v_1, v_2$

1)  $i_2 - i_1 = I_{T1} f(v_2)$

$\hat{i}_2 - \hat{i}_1 = I_{T2} f(-v_2) = -I_{T2} f(v_2)$

2)  $\hat{i}_1 - \hat{i}_2 = I_{T2} f(v_2)$

3)  $I_{T2} - I_{T1} = I_T f(v_1)$

$$4) \quad 1) - 2) \Rightarrow (i_2 - \hat{i}_1) - (\hat{i}_1 - \hat{i}_2) = I_{T_1} f(v_2) - I_{T_2} f(v_2)$$

$$= (i_2 + \hat{i}_2) - (i_1 + \hat{i}_1) = (I_{T_1} - I_{T_2}) f(v_2)$$

$$\stackrel{3)}{=} -I_T f(v_1) \cdot f(v_2)$$

$$i_o = I_T f(v_1) f(v_2) = (i_1 + \hat{i}_1) - (i_2 + \hat{i}_2)$$

$$f(v) = \frac{I_T}{V_T} \tanh\left(\frac{v}{V_T}\right) \quad \text{BJT}$$

linear near origin

gives an excellent multiplier for small  $v$

