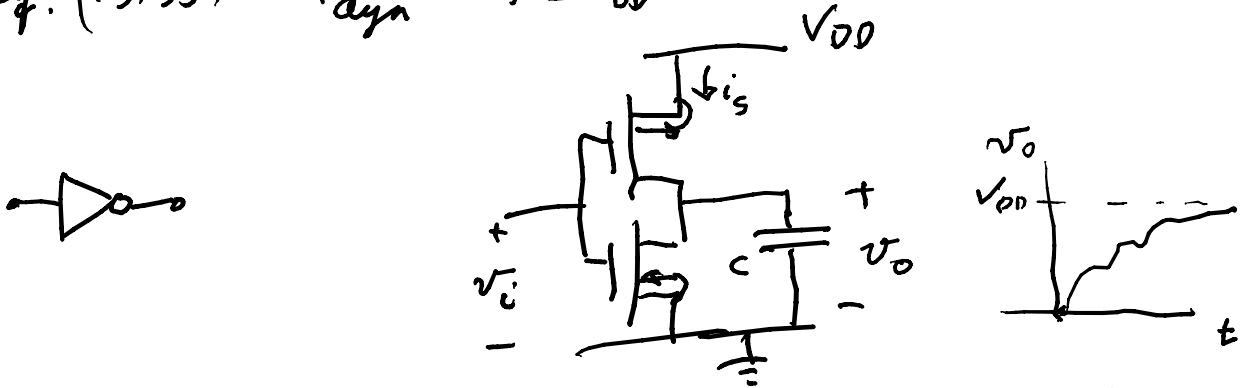


p. 1079 gives power dissipation

Eq. (13.35) $P_{dyn} = f C V_{DD}^2$



assume v_i switches from high to low after C is totally discharged
(V_{DD}) (0)

Power from the battery is $V_{DD} i_{s,p} t$

$$\text{Energy} = \int_0^t V_{DD} i_{s,p}(\tau) d\tau = V_{DD} \int_0^t i_{s,p}(\tau) d\tau = V_{DD} C v_c(t)$$

$\underbrace{\int_0^t i_{s,p}(\tau) d\tau}_{Q(t)}$

Energy into a capacitor is

$$\int_0^t i_{cap} v_{cap} d\tau = \int_0^t C \frac{dv_{cap}}{dt} v_{cap} d\tau = \int_{v_c(0)}^{v_c(t)} C v_c dv_c$$

$$= \int_{v_c(0)}^{v_c(t)} C \frac{dv_c^2}{2} = \frac{C}{2} v_c^2 \Big|_{v_c(0)}^{v_c(t)} = \frac{C}{2} v_c^2(t); \quad Q = C v_c$$

if fully charge the capacitor $\Rightarrow v_c \rightarrow V_{DD}$


after fully switched from a high input to a low input then the Energy in the capacitor is $\frac{1}{2} C V_{DD}^2$

& the Energy out of the battery is $C V_{DD}^2$


i.e. the PMOS dissipates $\frac{1}{2} C V_{DD}^2$

if switch at frequency $f = 1/T$ (period = T) then
 double the energy in each cycle \Rightarrow total energy
 lost in the CMOS inverters/cycle is $C V_{DD}^2$
 for f cycles $P_{diss} = f \cdot C V_{DD}^2$ (17.35)

Here

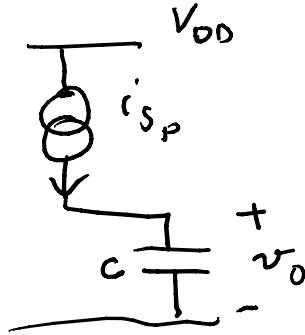


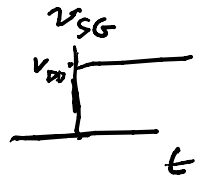at $t=0$
 $v_{SG} = V_{DD}$
 $v_0(0) = 0$
 $= v_{Drain}$
 here $v_{SD} = V_{DD} - v_0$
 $v_{SG} = V_{DD}$



at $t=0$ $v_{SG} - |V_{T0}| = V_{DD} - |V_{T0}| \leq v_{SD} = v_0$
 in saturation

remains in saturation until $v_0 \Rightarrow$ gives $v_{SD} = V_{DD} - |V_{T0}|$

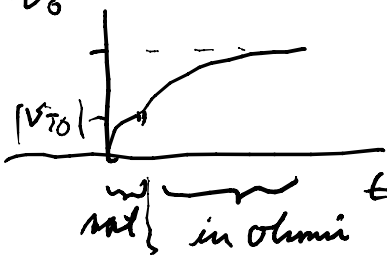

$$v_0 \Rightarrow i_S = C \frac{dv_0}{dt}$$

$$\text{for } v_0 < |V_{T0}| \Rightarrow \frac{\beta}{2} (V_{DD} - |V_{T0}|)^2 = C \frac{dv_0}{dt}$$

$t_s \Rightarrow$ linear increase until t_s

after t_s then $i_S = \frac{\beta}{2} \left\{ 2(V_{DD} - |V_{T0}|)v_{SD} - v_{SD}^2 \right\}$

$$\beta = \frac{\beta}{2} \left\{ 2(V_{DD} - |V_{T0}|)v_{SD} - v_{SD}^2 \right\}$$

$$C \frac{dv_0}{dt} = \beta \left\{ 2(V_{DD} - |V_{T0}|)(V_{DD} - v_0) - (V_{DD} - v_0)^2 \right\}$$

a Riccati differential equation

$$\frac{d(V_{DD} - v_0)}{dt} = - \frac{dv_0}{dt} ; \quad x = V_{DD} - v_0 \quad (\text{varies between } x(0) = V_{DD}, x(t_s) = 0)$$

$$-C \frac{dx}{dt} = \beta (2(V_{DD} - |V_{T0}|)x - x^2) = \beta (ax - x^2)$$

$$-\frac{c}{\beta} \cdot \frac{dx}{(ax-x^2)} = dt \Rightarrow \frac{dx}{x^2-ax} = \frac{\beta}{c} dt$$

$$\frac{\beta}{c} \int_0^{t_s} dt = \frac{\beta}{c} t_s = \int_{x(0)}^{x(t_s)} \frac{dx}{x^2-ax} = \int_{x(0)}^{x(t_s)} \left[\frac{k_1}{x} + \frac{k_2}{x-a} \right]$$

\uparrow
 $x(x-a)$

$$\frac{1}{x(x-a)} = \frac{k_1}{x} + \frac{k_2}{x-a} \Rightarrow \frac{1}{x(x-a)} = \frac{k_1 + \frac{k_2 x}{x-a}}{x(x-a)} = \frac{1}{x-a} = \frac{1}{-a}$$

$x=0$ $x=0$ $x=0$

partial fraction expansion

$$\frac{x-a}{x(x-a)} = \frac{1}{x} = \frac{k_1(x-a) + k_2}{x} \Rightarrow k_2 = 1/a$$

$x(x-a)$ $x=a$ $x=a$

$$\frac{\beta}{c} \cdot t_s = \int_{x(0)}^{x(t_s)} \frac{-1/a}{x} dx + \int_{x(0)-a}^{x(t_s)-a} \frac{1/a}{x-a} d(x-a)$$