

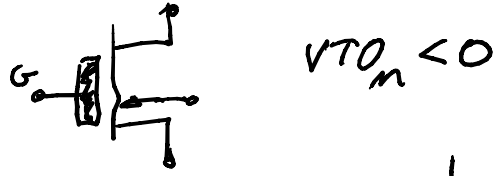




Depletion mode
MOS

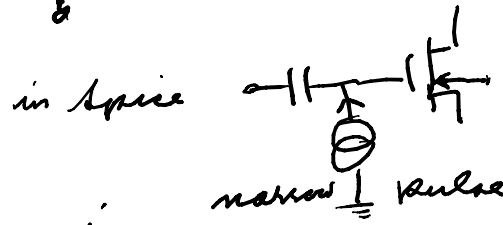

Floating gate
MOS

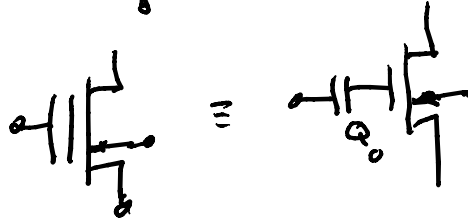


Zener diode

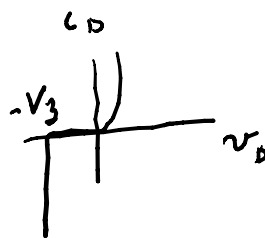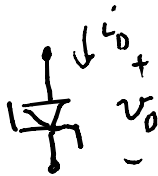


see p. 190

Tunnel diode
(Esaki)

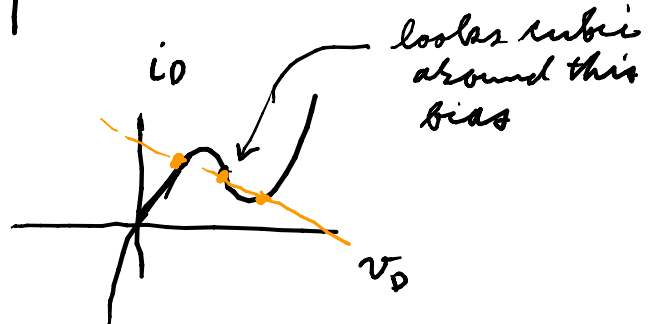


looks cubic
around this
bias


Resonant tunnel diode

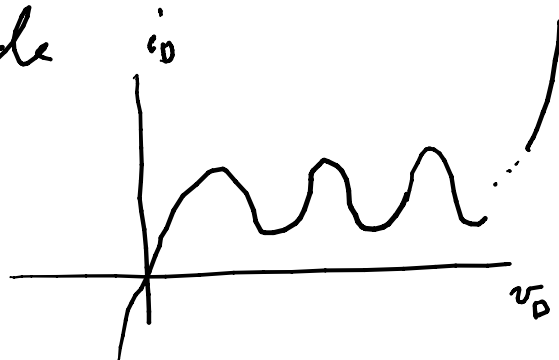

Quartz Crystal

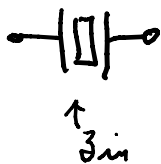

⇒

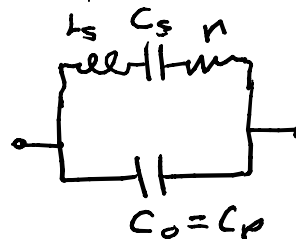

$r = \text{small}$
⇒ high Q
has a precise
resonant frequency

see Pierce oscillators, p. 1355

$$Z_{in} = \frac{1}{Y_{in}} \Rightarrow Y_{in}(s) = C_0 s + \frac{1}{L_s s + \frac{1}{C_s s} + R} = C_0 s + \frac{C_s s}{L_s C_s^2 + R C_s s + 1}$$

$$= C_0 s + \frac{\frac{1}{L_s} s}{s^2 + \frac{R}{L_s} s + \frac{1}{L_s C_s}} = C_0 s + \frac{\frac{1}{L_s} s}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

$$\frac{r}{L_s} = \frac{\omega_0}{Q} \Rightarrow Q = \frac{\omega_0 \cdot L_s}{r}$$


$$= \frac{1}{r} \cdot \sqrt{L_s / C_s} \Rightarrow \text{if } r=0 \quad Q = \infty$$

$$\omega_0^2 = \frac{1}{L_s C_s}$$

$Y_{in}(s) \Rightarrow$ has a zero @ $s=0$

\Rightarrow poles near zeros of $s^2 + \omega_0^2 \Rightarrow s = \pm j\omega_0$

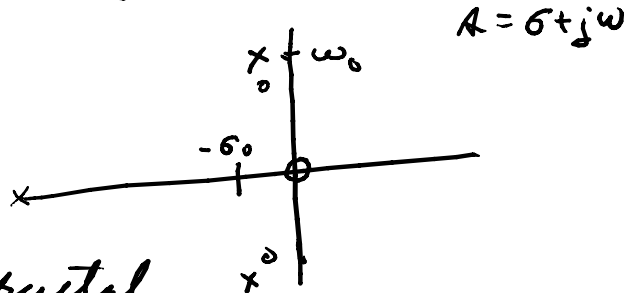if $r \neq 0$, $s = \sigma_0 \pm j\omega_0$



actual poles of Y_{in} of the crystal

are zeros of $s^2 + \frac{\omega_0}{Q} s + \omega_0^2 = D(s)$

$$s_{1,2} = -\frac{\omega_0}{2Q} \pm \frac{j}{2} \sqrt{\left(\frac{\omega_0}{Q}\right)^2 - 4\omega_0^2} = \frac{\omega_0}{2Q} \left[-1 \pm \sqrt{1 - 4Q^2} \right], \quad Q \neq 0$$

if Q is high then $s_{1,2} = \frac{\omega_0}{2Q} (1 \pm 2jQ)$

$$= \frac{\omega_0}{2Q} \pm j\omega_0$$

$$= \frac{r}{2L_s} \pm j \sqrt{\frac{1}{L_s C_s}}$$



Pierce oscillator


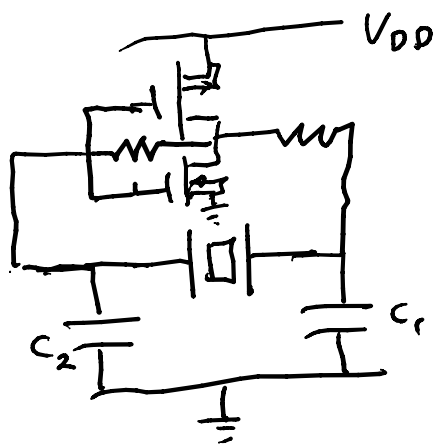
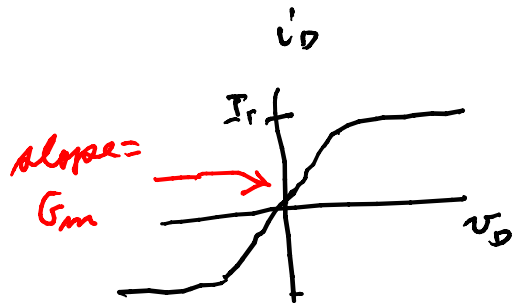


Fig 17.16





How to get a negative R

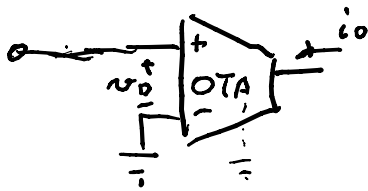

from 10/04/11
$$i_o = \beta v_D \sqrt{\frac{2I_T}{\beta} - v_D^2} \text{ for } |v_D| \leq \frac{I_T}{\beta}$$

for $|v_D|$ small
$$i_o \sim \beta v_D \sqrt{\frac{2I_T}{\beta}} = \underbrace{\sqrt{2\beta I_T}}_{G_m} v_D$$

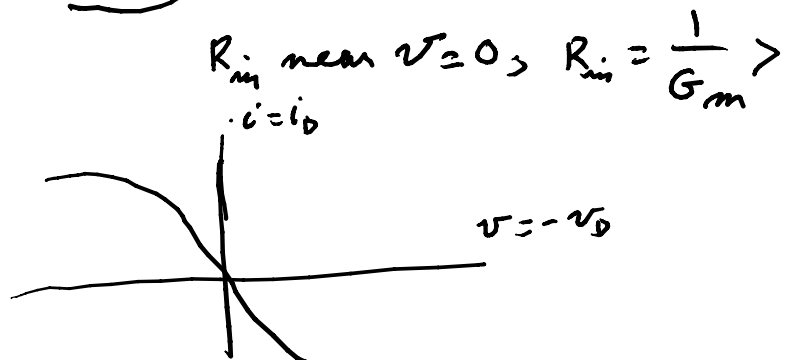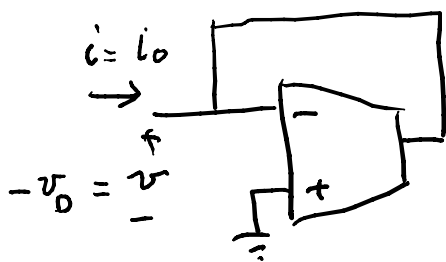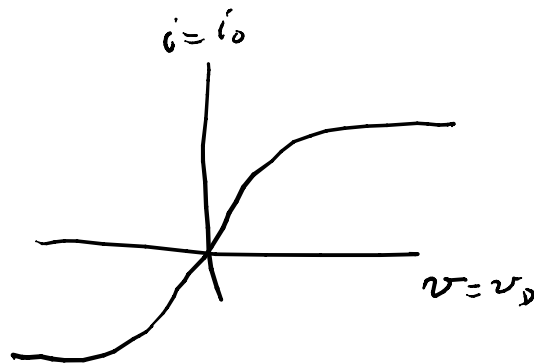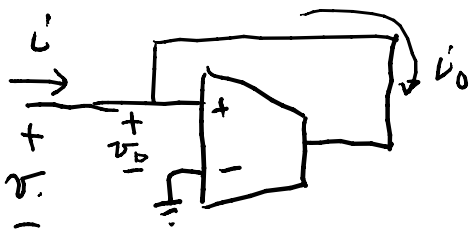$\beta = \frac{K_P \cdot W}{2 \cdot L}$ of differential pair transistors



slope $< 0 \Rightarrow$ a negative R

for hysteresis from last time

$$\text{slope} = 1 + \frac{G_1}{G_2} = \frac{V_{DD}}{V_{D2}}$$

$$-V_{D2} = \frac{G_1}{G_2} \cdot \frac{1}{1 + \frac{G_1}{G_2}} V_{i2}$$

$$\Rightarrow 1 + \frac{G_1}{2} = \frac{V_{DD}}{V_{D2}}$$

$$- \frac{G_1}{G_2} \left(\frac{1}{1 + \frac{G_1}{G_2}} \right) V_{i2}$$

← voltage input to hysteresis for the jump down

same for V_{i1} do the same on the other

side: $V_{i2} = - \frac{G_1}{G_2} V_{DD}$; $V_{i1} = \frac{G_1}{G_2} (-V_{SS}) = \frac{G_1}{G_2} V_{DD}$

width: $V_{i1} \rightarrow V_{i2} = 2 \frac{G_1}{G_2} V_{DD}$