

s -plane $P_1(s)y(s) = P_2(s)u(s)$ $D = d/dt$, $u = \text{input}$
 $y = \text{output}$

$P(s) = \text{polynomial}$ Then $u(t) = Ue^{st}$

$$y(t) = Ye^{st}$$

$$P_1(s)Ye^{st} = P_2(s)Ue^{st} \Rightarrow \frac{Y}{U} = \frac{P_2(s)}{P_1(s)}$$

Ex: $\frac{d^2}{dt^2}y + a_1\frac{d}{dt}y + a_0y = \frac{d}{dt}u + b_1u$, $-\infty < t < \infty$

$$y = Ye^{st}, u = Ue^{st}, \frac{d}{dt} = D, \frac{d}{dt}e^{st} = se^{st}$$

$$\frac{d^2}{dt^2}e^{st} = s^2e^{st}$$

$$s^2Y + a_1sY + a_0Y = sU + b_1U$$

$$\frac{Y}{U} = \frac{s + b_1}{s^2 + a_1s + a_0} = \text{transfer function}$$

$$= \frac{P_2(s)}{P_1(s)} \Rightarrow P_2(s) = s + b_1, \text{ zero @ } s = -b_1, \infty$$




$$P_2(s) = (s + k_1)(s + k_2), s = -k_1, -k_2$$

$$= s^2 + a_1s + a_0 \text{ are the roots}$$

$$= s^2 + \frac{\omega_0}{Q}s + \omega_0^2$$

$$Q = \infty$$
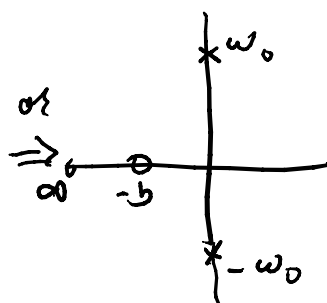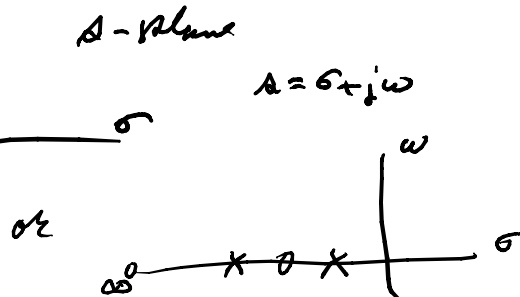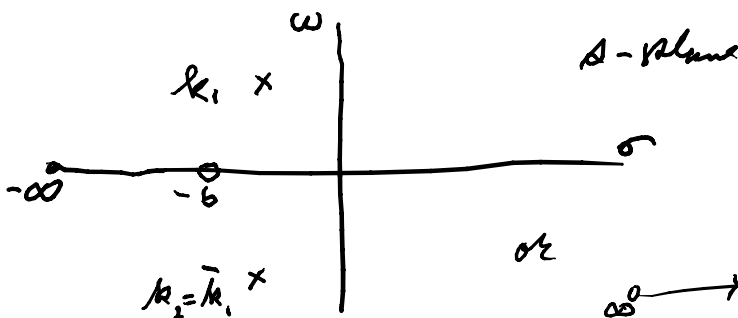
$$k_{1,2} = -\frac{a_1}{2} \pm \frac{1}{2}\sqrt{a_1^2 - 4a_0}$$




poles @ $s = \pm j\omega_0$

$$y(t) = Ae^{j\omega_0 t} + Be^{-j\omega_0 t}$$

$$= A(\cos\omega_0 t + j\sin\omega_0 t) + B(\cos(-\omega_0 t) + j\sin(-\omega_0 t))$$

zeros give frequencies, $s = \sigma_1 + j\omega_1$, at which the system gives zero output


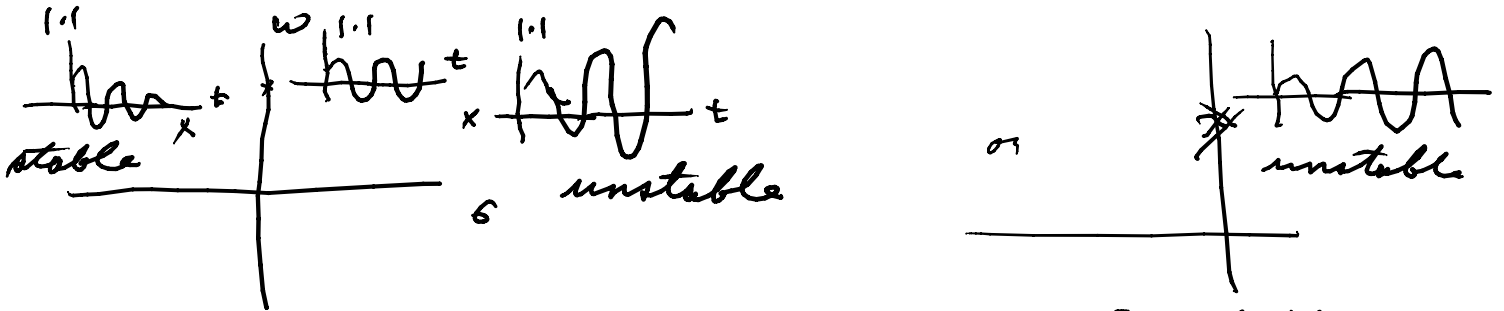
poles give frequencies, $s = \sigma \pm j\omega$, at which the system responds in a natural way, due to initial conditions.



For stability with poles in $s < 0$ or simple if on $\sigma = 0$
 ($s = \sigma + j\omega$)

polynomials with these zeros are called Hurwitz, or strictly Hurwitz if no poles on $\sigma = 0$.

Colpitts oscillator Fig. 17.12

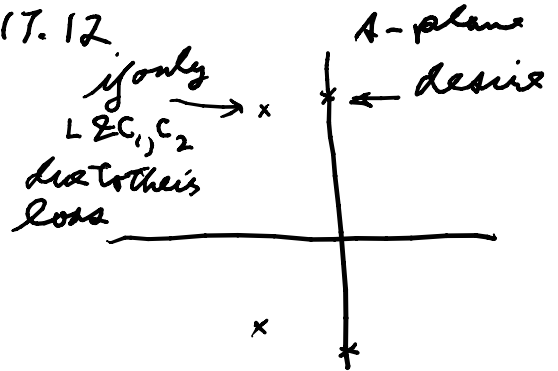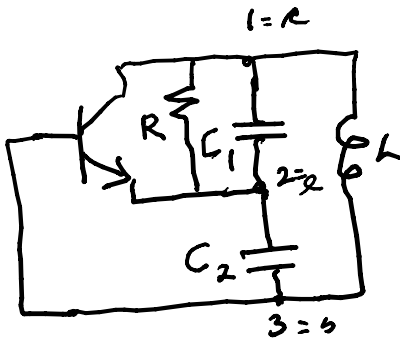


For small oscillations can use the π equivalent circuit of the BJT \Rightarrow


SS eq. wrt.

$$g_m = \frac{I_C}{V_T}, g_o = \frac{I_C}{V_A}$$

$$g_{\pi} = \frac{g_m}{\beta}$$

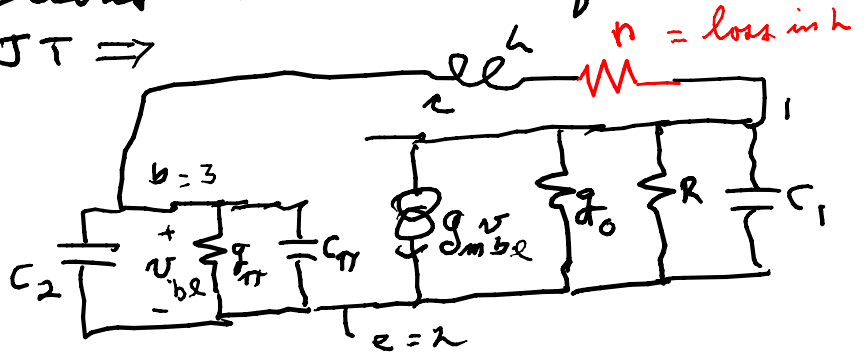

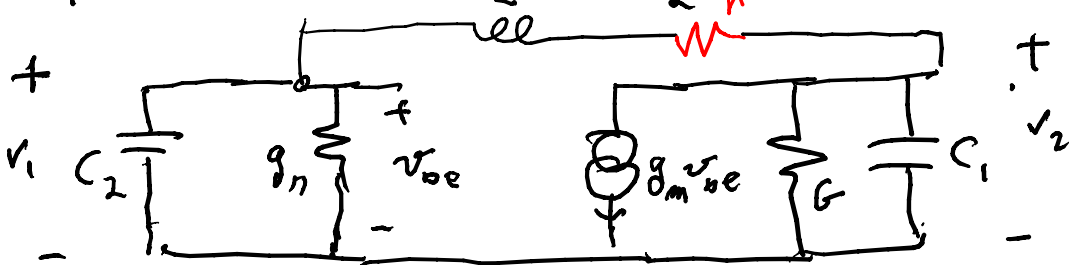can lump $C_2 + C_{\pi} \Rightarrow C_2$, $R + r_o + \text{loss of } C_1, \text{ loss of } C_2 \text{ in } g_{\pi} \Rightarrow R$




$$Y = g_{\pi} + \frac{1}{sL} + g$$

$$Y_{21} = g_m - \frac{1}{sL} - g$$

$$Y_{12} = -\frac{1}{sL} - g$$

$$Y_{22} = G + sC_1 + \frac{1}{sL} + g$$

$$g = 1/r$$

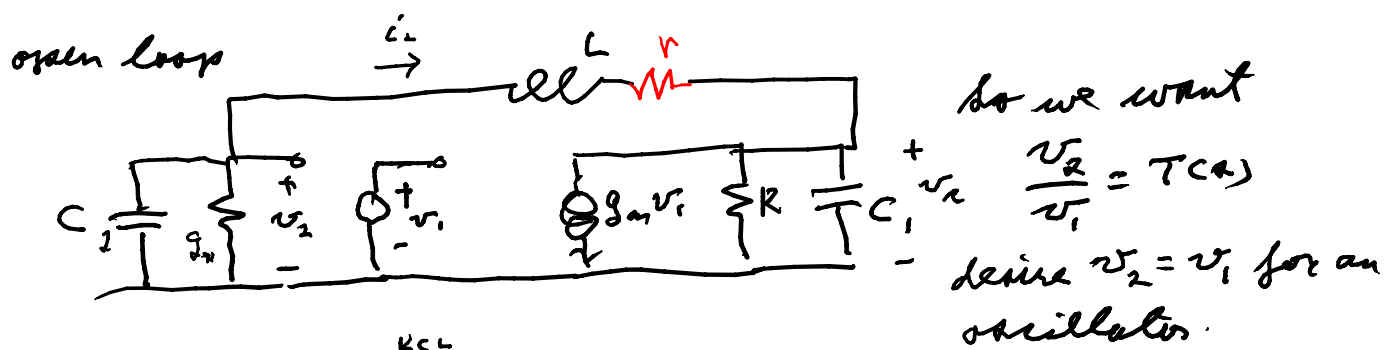

(1a, b, c) $i_L = \frac{1}{L(sL+r)} (v_2 - v_1) \stackrel{KCL}{=} g_m v_1 + G v_2 + sC_1 v_2 = g_m v_1 + (G + sC_1) v_2$

(2) $= -(g_{\pi} + sC_2) v_2 =$

from (1)=(2) $\left[\frac{1}{sL+r} + (g_{\pi} + sC_2) \right] v_2 = \frac{1}{sL+r} v_1 \Rightarrow$

(3) $[1 + (sL+r)(g_{\pi} + sC_2)] v_2 = v_1$

(3) \Rightarrow (1)=(2) $g_m v_1 = -\{ (g_{\pi} + sC_2) + (G + sC_1)[1 + (sL+r)(g_{\pi} + sC_2)] \} v_2$

This gives the "return ratio" $T(s) = \frac{v_2}{v_1} = \frac{-g_m}{\{ (g_{\pi} + sC_2) + (G + sC_1)[1 + (sL+r)(g_{\pi} + sC_2)] \}}$
 which has 3 zeros @ ∞ , 3 finite poles

For the closed loop, $v_2 = v_1 \Rightarrow T(s) = 1$, which yields the "natural frequencies" as zeros of the degree 3 polynomial

$P(s) = (g_{\pi} + sC_2) + (G + sC_1)[1 + (sL+r)(g_{\pi} + sC_2)] + g_m$

For sinusoidal oscillations, $s = j\omega_0$ so we want $P(j\omega_0) = 0$

$$\begin{aligned} P(j\omega_0) &= (g_{\pi} + j\omega_0 C_2) + (G + j\omega_0 C_1) + (G + j\omega_0 C_1)(j\omega_0 L + r)(g_{\pi} + j\omega_0 C_2) + g_m \\ &= (g_{\pi} + G) + j\omega_0 (C_2 + C_1) + [j\omega_0 G L + G r - \omega_0^2 L C_1 + j\omega_0 C_1 r](g_{\pi} + j\omega_0 C_2) + g_m \\ &= (g_{\pi} + G + g_m) + j\omega_0 (C_2 + C_1) + [j\omega_0 G L g_{\pi} - \omega_0^2 G L C_2 + G r g_{\pi} + j\omega_0 C_2 G r \\ &\quad - \omega_0^2 L C_1 g_{\pi} - j\omega_0^3 L C_1 C_2 + j\omega_0 C_1 r g_{\pi} - \omega_0^2 C_1 C_2 r] \\ &= (g_{\pi} + G + g_m - \omega_0^2 G L C_2 + G r g_{\pi} - \omega_0^2 L C_1 g_{\pi} - \omega_0^2 C_1 C_2 r) \\ &\quad + j\omega_0 (C_2 + C_1 + G L g_{\pi} + C_2 G r + C_1 r g_{\pi}) \end{aligned}$$

Real: $g_m = +\omega_0^2 L G + \{ \omega_0^2 L C_1 g_{\pi} + \omega_0^2 C_1 C_2 r \} - G - g_{\pi} - G r g_{\pi}$


Imag: $0 = -\omega_0^2 L C_1 C_2 + C_2 + C_1 + G L g_{\pi} + C_2 G r + C_1 r g_{\pi}$

The imaginary part gives

$$\omega_0^2 = \frac{1}{L} \left(\frac{C_1 + C_2}{C_1 C_2} \right) + \underbrace{\left\{ \frac{G L g_{\pi} + C_2 G r + C_1 r g_{\pi}}{L C_1 C_2} \right\}}_{\text{correction due to losses over}}$$

end result \approx Eq. (17.16)
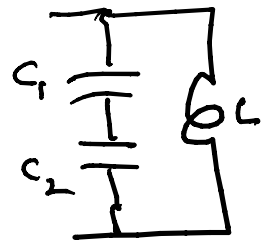
$$\omega_0 = \sqrt{\frac{1}{LC_1 C_2}} = \frac{1}{\sqrt{LC_{eq}}}$$



and $\frac{g_m}{C} \approx C_2/C_1$ (eq. 17.21) gives gain, from real part