
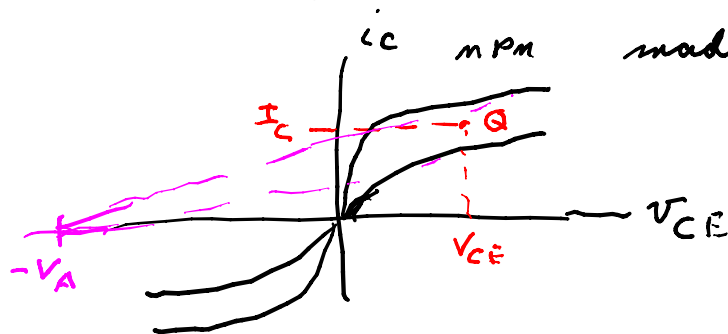



Exam: open book, notes

question topics

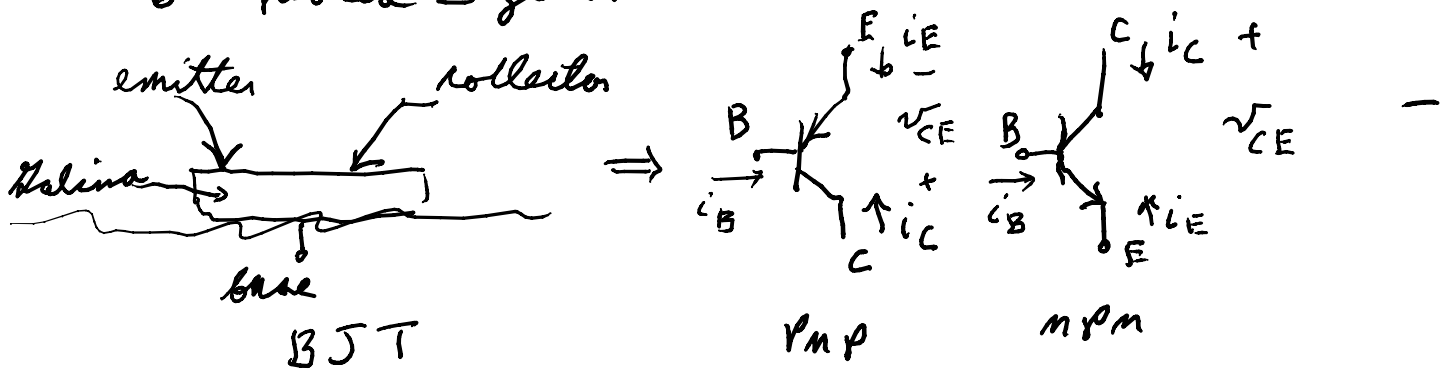1. npn vs pnp (BJT)
2. Small signal π equivalents BJT & MOS
3. emitter followers
4. current mirrors, CMOS & input vs. output
5. op-amp with frequency response
6. poles & zeros



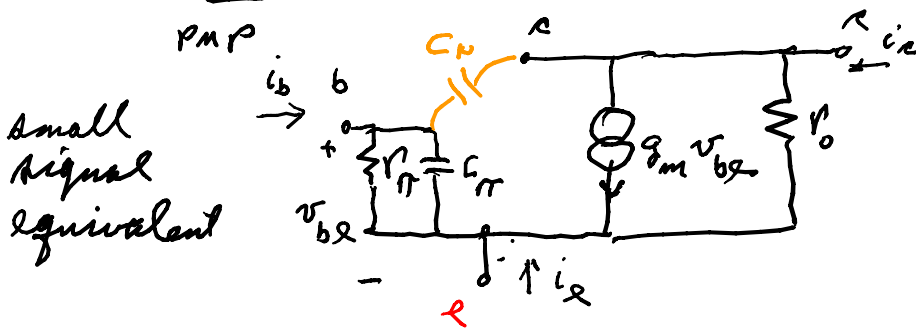
KCL: $0 = i_B + i_C + i_E$
 $i_C = \alpha(-i_E) = \beta i_B$; $\alpha > 0$, $\beta > 0$
 $\beta = \frac{\alpha}{1-\alpha}$, $\alpha = \frac{\beta}{1+\beta} < 1$
 > 1



Small signal equivalent


fixed, $V_{BE} \sim 0.7$
 $g_m = \frac{|I_C|}{V_T}$; $V_T = \frac{kT}{|Q|} \approx 26 \text{ mV}$ @ room T
 $g_{\pi} = \frac{g_m}{\beta}$, $g_o = \frac{|I_C|}{V_A}$

an emitter follower

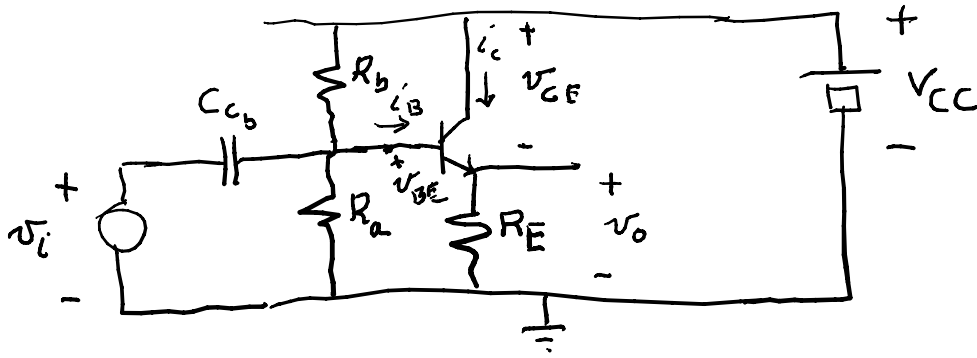


$$V_{BE} = 0.7$$

for bias

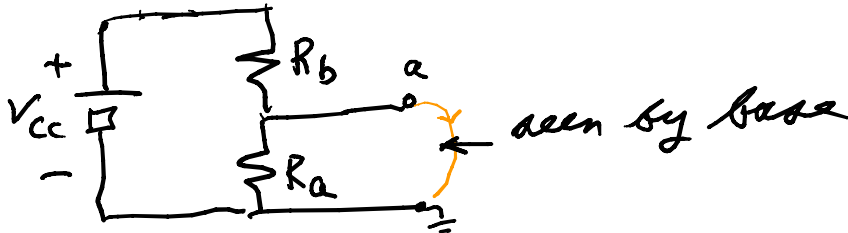

Use Thevenin's equivalent

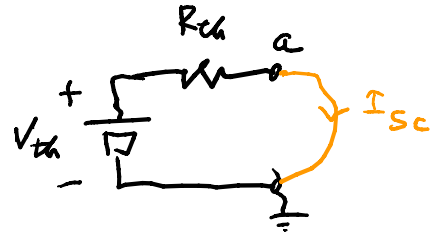


$$V_{oc} = V_{th} = \frac{R_a}{R_a + R_b} V_{cc}$$

$$I_{sc} = \frac{V_{th}}{R_{th}} = \frac{V_{cc}}{R_b}$$

$$\Rightarrow R_{th} = \frac{R_b}{V_{cc}} \times V_{th} = \frac{R_b}{V_{cc}} \cdot \frac{R_a}{R_a + R_b} \cdot V_{cc} = \frac{R_a R_b}{R_a + R_b} = R_a || R_b$$

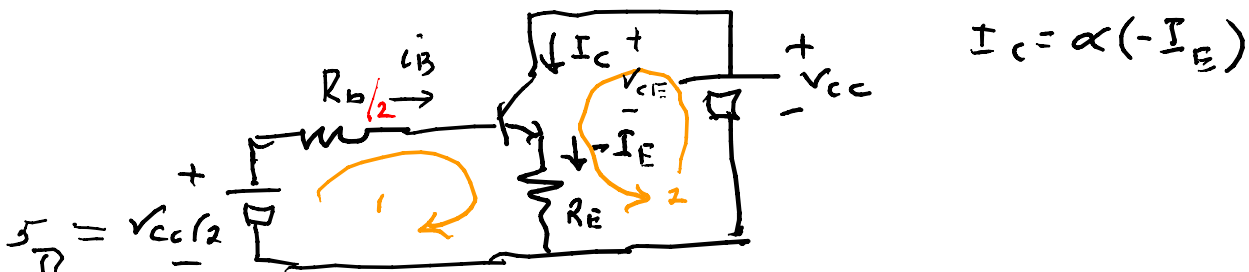if $R_a = R_b \Rightarrow R_{th} = \frac{1}{2} R_a$ so let $R_a = R_b$



$$V_{cc} = 10, V_{CE} = 6, R_a = R_b = 10^6 \Omega = 1 \text{ MEG}, \beta = 99$$

find R_E

DC

$$\text{KVL} = 0 \quad -V_{cc} + R_b I_b + V_{BE} + R_E (-I_E) = 0 \quad , I_c = \beta I_B$$

$$\text{loop 1} \Rightarrow -5 + 0.7 + \left(\frac{10^6}{200} + R_E \right) (-I_E) = 0$$

$$= -\alpha I_E$$

$$I_B = \frac{\alpha}{\beta} (-I_E)$$

$$= \frac{1}{\beta + 1} (-I_E)$$

$$\text{loop 2} \text{ KVL} = 0 \quad -V_{cc} + V_{CE} + R_E (-I_E) = 0$$

$$-10 + 6 + R_E (-I_E) = 0$$



$$(-I_E) \stackrel{||}{=} \frac{4.3}{5 \times 10^3 + R_E} = \frac{4}{R_E} \Rightarrow 4.3 R_E = 2 \times 10^4 + 4 R_E$$

$$0.3 R_E = 2 \times 10^4 \Rightarrow R_E = \frac{2}{3} \times 10^5 = 6.66 \times 10^4 \approx 67 \text{ k}\Omega$$

$$-I_E = \frac{4}{\frac{2}{3} \times 10^5} = 6 \times 10^{-5} = 60 \times 10^{-6} = 60 \mu\text{A}$$

$$I_C = \alpha(-I_E) = \frac{\beta}{\beta+1} (-I_E) = \frac{99}{100} \times 60 \mu\text{A} ; I_D = \frac{I_C}{\beta} = \frac{60}{100} \mu\text{A}$$

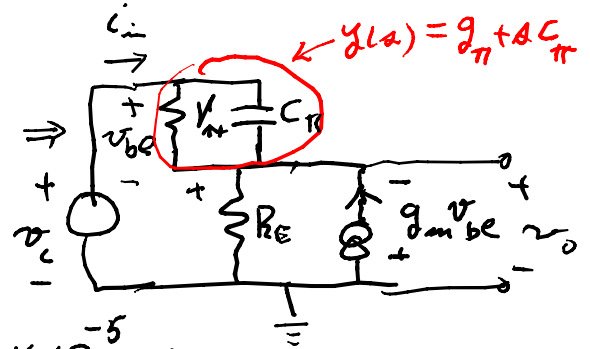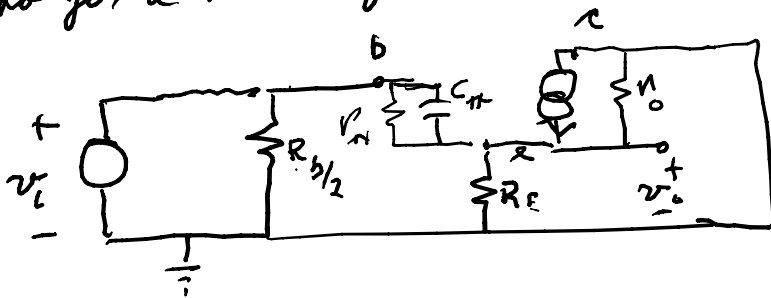small signal gain assume $V_A = 100$
(also for a source follower)



$$g_m = \frac{I_C}{V_T} = \frac{60 \times 10^{-6}}{26 \times 10^{-3}} = (3/1.3) \times 10^{-5} \text{ S}$$

$$g_{\pi} = \frac{g_m}{\beta} = \frac{3}{1.3} \times \frac{10^{-5}}{99} \approx 2 \times 10^{-7} \text{ S}, \quad g_o = \frac{I_C}{V_A} = \frac{60}{(100)^2} \times 10^{-6}$$

desire $\frac{v_o}{v_i} \Rightarrow v_i = v_{be} + v_o ;$ 1)

$y v_{be} = i_{in} = G_E v_o - g_m v_{be}$ 2)

2) $\Rightarrow (y + g_m) v_{be} = G_E v_o \Rightarrow v_{be} = \frac{G_E}{y + g_m} v_o$


\Rightarrow 1) $v_i = \left(\frac{G_E}{y + g_m} + 1 \right) v_o \Rightarrow \frac{v_o}{v_i} = \frac{y + g_m}{G_E + g_m + y}$

$$= \frac{1}{1 + \frac{G_E + g_m}{y}}$$

$\left| \frac{v_o}{v_i} \right| < 1 ; \frac{v_o}{v_i} = \frac{(g_{\pi} + g_m) + j\omega C_{\pi}}{(G_E + g_m + g_{\pi}) + j\omega C_{\pi}}$

pole: $s = -(G_E + g_m + g_{\pi}) / C_{\pi} = -1 / R_{eq} C_{\pi}$

zero: $s = -(g_m + g_{\pi}) / C_{\pi}$

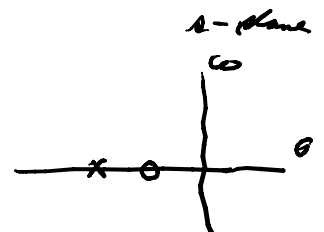




for sine waves, $s = j\omega$

$$\frac{v_o}{v_i} = \frac{g_1 + j\omega C_{\pi}}{(g_E + g_1) + j\omega C_{\pi}} \quad ; \quad \left| \frac{v_o}{v_i} \right| = \frac{\sqrt{g_1^2 + \omega^2 C_{\pi}^2}}{\sqrt{(g_1 + g_E)^2 + \omega^2 C_{\pi}^2}} \approx 1 \quad \text{for } \omega < \infty$$

Look $\frac{v_o}{v_i}(s) = \frac{k\sigma_0}{s + \sigma_0} \quad ; \quad \left| \frac{v_o}{v_i}(j\omega) \right| = \frac{|k\sigma_0|}{\sqrt{\sigma_0^2 + \omega^2}}$

$\sigma_0 > 0$

$$d = \sqrt{\omega^2 + (-\sigma_0)^2}$$

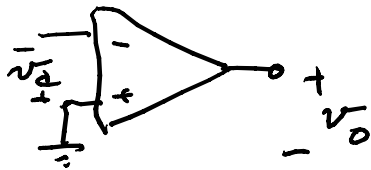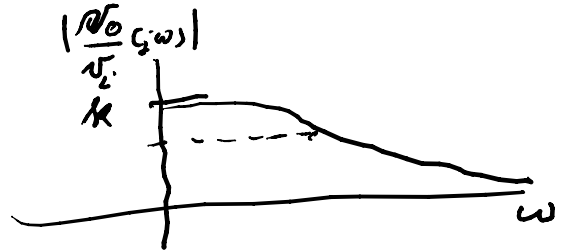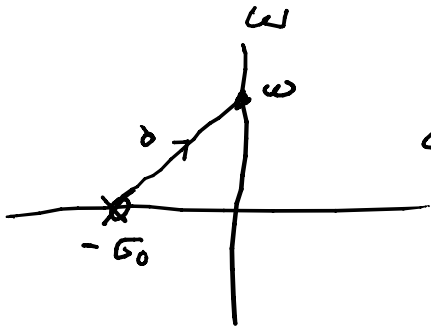

$$\frac{v_o}{v_d} = \frac{k\sigma_0}{s + \sigma_0}$$

