

a)

1) $v_3 = v$

KCL 2) $L' = AC(v_3 - v_0) \Rightarrow L' = AC(v - v_0)$

3) $v_0 = k v_d$

KVL 4) $v_d = v_3 - v_2 \Rightarrow v_d = v - v_2$

5) $v_2 = \frac{R_1}{R_1 + R_2} v_0 \Rightarrow v_d = v - \frac{R_1}{R_1 + R_2} v_0$

6) = 5) + 3) $\Rightarrow v_0 = k v - k \frac{R_1}{R_1 + R_2} v_0 \Rightarrow (1 + \frac{k R_1}{R_1 + R_2}) v_0 = k v$

7) = 6) + 2) $\Rightarrow L' = AC(v - \frac{k}{1 + \frac{k R_1}{R_1 + R_2}} v) = AC(1 - \frac{(R_1 + R_2)k}{(R_1 + R_2) + k R_1}) v$
 $= AC(\frac{R_1 + R_2 - R_2 k}{R_1 + R_2 + k R_1}) v = AC(\frac{1/G_1 + 1/G_2 - k/G_2}{1/G_1 + 1/G_2 + k/G_1}) v$
 $= AC(\frac{G_2 + G_1 - k G_1}{G_2 + G_1 + k G_2}) v$

$\Rightarrow y(s) = AC(\frac{G_2 + G_1 - k G_1}{G_2 + G_1 + k G_2})$

b) $y(s) = AC(\frac{G_2 + G_1 - \frac{k \infty \sigma_1 \sigma_2 G_1}{(s + \sigma_1)(s + \sigma_2)}}{G_2 + G_1 + \frac{k \infty \sigma_1 \sigma_2 G_2}{(s + \sigma_1)(s + \sigma_2)}})$

$= AC(\frac{(G_1 + G_2)(s + \sigma_1)(s + \sigma_2) - k \infty \sigma_1 \sigma_2 G_1}{(G_1 + G_2)(s + \sigma_1)(s + \sigma_2) + k \infty \sigma_1 \sigma_2 G_2})$


$= AC(\frac{s^2 + (G_1 + G_2)s + \sigma_1 \sigma_2 [1 - k \infty G_1 / (G_1 + G_2)]}{s^2 + (G_1 + G_2)s + \sigma_1 \sigma_2 [1 + k \infty G_2 / (G_1 + G_2)]})$

zeros: $s = 0, s_{1,2} = -\frac{(G_1 + G_2)}{2} \pm \frac{1}{2} \sqrt{(G_1 + G_2)^2 - 4 \sigma_1 \sigma_2 [1 - k \infty G_1 / (G_1 + G_2)]}$
 $= -\frac{(G_1 + G_2)}{2} \pm \frac{1}{2} \sqrt{(G_1 - G_2)^2 + 4 \sigma_1 \sigma_2 k \infty G_1 / (G_1 + G_2)}$

poles: $s_{3,4} = -\frac{(G_1 + G_2)}{2} \pm \frac{1}{2} \sqrt{(G_1 - G_2)^2 - 4 \sigma_1 \sigma_2 k \infty G_1 / (G_1 + G_2)}$

If $k \infty = 0$ the poles cancel the non-zero zero, as $k \infty > 0$ increases the zeros remain real, moving away from $s_0 = -\frac{(G_1 + G_2)}{2} \pm \frac{1}{2} \sqrt{(G_1 - G_2)^2}$ while the poles move toward $p_0 = -(G_1 + G_2)/2$ and become complex conjugate with real part p_0

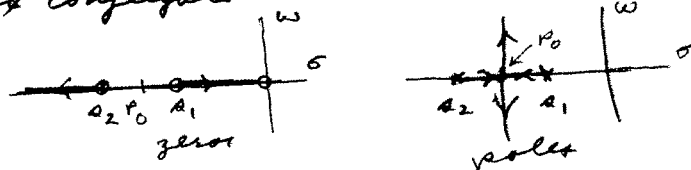(for $k \infty < 0$ the poles behave as the $k \infty > 0$ nonzero zero & vice versa)



c) If $k \infty = 0$ $y(s) = -AC \cdot G_1 / G_2$

which is a capacitor of $C_{equivalent} = -(G_1 / G_2) C$

When attached to a load $y_L(s)$ instability can occur unless $y_L(s)$ as $s \rightarrow \infty$ has $C_L > -C_{equivalent}$.