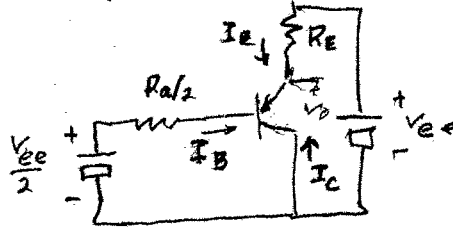


#1 By Thevenin's theorem



$$1) V_{cc} - V_c = 10 - 8 = 2 = R_E I_E$$

$$2a) I_E = -\frac{I_C}{\alpha} = -\frac{\beta I_B}{\alpha} = -\frac{\beta}{\beta+1} I_B \quad I_B = -(1+\beta) I_E$$

$$2b) \Rightarrow I_B = \frac{-1}{(1+\beta)} I_E$$

$$3) \text{ KVL: } -\frac{V_{cc}}{2} + \frac{R_A}{2} I_B + (V_{BE}) + V_c = 0 = -5 + \frac{10^6}{2} \times \left(\frac{-1}{1+99}\right) I_E + (-0.7) + 8 = 0$$

$$3a) \Rightarrow 3 - 0.7 = 2.3 = \frac{10^6}{2 \times 10^2} I_E = \frac{10^4}{2} I_E$$

$$* 4) \Rightarrow I_E = 4.6 \times 10^{-4} = 0.46 \text{ milli Amp}$$

$$* \quad \text{From 1) } R_E = \frac{2}{I_E} = \frac{10^4}{2.3} = \frac{10}{2.3} \times 10^3 = 4.35 \text{ k}\Omega$$

$$\# 2. \quad T(s) = \frac{s(s^2+4)}{(s+3)(s+5)} = \frac{s(s+j2)(s-j2)}{(s+3)(s+5)} \Rightarrow \frac{s^3}{s^2} \Rightarrow \infty \text{ as } s \rightarrow \infty$$

$$\text{zeros: } s = 0, \pm j2$$

$$\text{poles: } s = \infty, -3, -5$$

seen by inspection

#3. $I_c = \beta(V_{GS} - V_{TO})^2(1 + \lambda V_{GS})$

$$= 10^{-4}(4-1)^2(1 + 0.01 \times 4)$$

a) $= 10^{-4}(9)(1.04) = 9.36 \times 10^{-4} A = 0.936 \text{ milli A}$

b) for $I_o = I_c$ need $V_{DS} = V_{GS} = V_o = 4V$

c) at $V_{GS} = 4$, the right transistor is in saturation when $V_{DS} \geq V_{GS} - V_{TO} = 3V$

$\therefore$ for $V_D = V_{DS} = 7$

$$I_o = \beta(V_{GS} - V_{TO})^2(1 + \lambda V_{DS}) = I_c \cdot \left(\frac{1 + \lambda V_{DS}}{1 + \lambda V_{GS}} \right)$$

$$= 9.36 \times 10^{-4} \left(\frac{1 + 0.01 \times 7}{1 + 0.01 \times 4} \right) = 9.36 \times 10^{-4} \times 1.0288 =$$

$$= 9.63 \times 10^{-4} A \text{ when } V_o = 7$$

*K.)

For $V_o = 2$ or $V_o < 3$, the right transistor is in Ohmic region

$$I_o = \beta(2(V_{GS} - V_{TO})V_{DS} - V_{DS}^2)(1 + \lambda V_{DS})$$

$$= 10^{-4}(2(3)2 - 4)(1 + 0.02) = 10^{-4}(8)(1.02)$$

$$= 8.16 \times 10^{-4} A$$


#4.

$$g_m = I_E / V_T = -\frac{\alpha I_E}{V_T} = -\frac{\beta}{1 + \beta} \cdot \frac{I_E}{V_T} = \frac{100}{101} \times \frac{50 \times 10^{-3}}{26 \times 10^{-3}} = 1.90 \times 10^{-3} S$$

$$g_\pi = \frac{g_m}{\beta} = \frac{1.90 \times 10^{-3}}{102} = 1.90 \times 10^{-5} S$$

$$g_o = \frac{I_C}{V_A} = -\frac{\beta}{1 + \beta} \frac{I_E}{V_A} = \frac{100}{101} \times \frac{50 \times 10^{-3}}{100} = 0.495 \times 10^{-6} S$$

f_T is the frequency at which $|\beta(j\omega)| = 1$

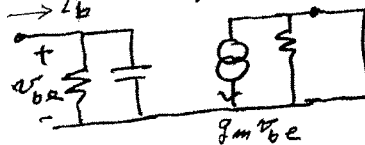

$$\Rightarrow \frac{i_c}{i_b} = \frac{g_m v_{be}}{(g_\pi + \alpha C_\mu) v_{be}} = \frac{g_m}{\alpha C_\mu + g_\pi} = \beta(j\omega)$$

$$|\beta(j\omega)| = \frac{g_m}{\sqrt{g_\pi^2 + C_\pi^2 \omega^2}} \Rightarrow 1 = \frac{g_m}{g_\pi^2 + C_\pi^2 \omega_T^2} \Rightarrow$$

$$\Rightarrow g_m^2 - g_\pi^2 = C_\pi^2 \omega_T^2$$

$$\Rightarrow \omega_T \approx g_m / C_\pi$$

$$\Rightarrow f_T = \frac{1}{2\pi} \times \frac{g_m}{C_\pi} = \frac{1.90 \times 10^{-3}}{2\pi \times 20 \times 10^{-12}} = \frac{1.90 \times 10^{-3}}{1.256 \times 10^{-10}} = 1.513 \times 10^7$$

$$= 15.13 \times 10^6 \text{ Hz} = 15.13 \text{ Meg Hz}$$

#5. Let $v_3 = v_{30}$, $v_2 = v_{20}$ then

1) $v_d = v_3 - v_2 = v - v_2$

as node 283 of op-amp draws no current

2) $v_2 = \frac{R_1}{R_1 + R_2} v_0$

3) $i = AC(v_3 - v_0)$

4) = 2) $\rightarrow$ 1) $v_d = v - \frac{R_1}{R_1 + R_2} v_0$

5) = 3) $+ v_3 = v \Rightarrow i = ACv - ACv_0$

But

6) $v_0 = K v_d \equiv v_d = \frac{1}{K} v_0$

7) = 6) $\rightarrow$ 4) $\frac{1}{K} v_0 = v - \frac{R_1}{R_1 + R_2} v_0 \equiv \left(\frac{1}{K} + \frac{R_1}{R_1 + R_2}\right) v_0 = v$

8) = 7) $\rightarrow$ 5

9) $i = ACv - AC\left(\frac{v}{\frac{1}{K} + \frac{R_1}{R_1 + R_2}}\right) = AC\left\{1 - \frac{(R_1 + R_2)}{\frac{1}{K}(R_1 + R_2) + R_1}\right\}v$

a) 10) $\therefore y = AC\left\{\frac{\frac{1}{K}(R_1 + R_2) - R_1}{\frac{1}{K}(R_1 + R_2) + R_1}\right\} = i/v$

For $K \rightarrow \infty$

b) $y = -AC \times \frac{R_2}{R_1} = AC_{eq}$; $C_{eq} = -\frac{R_2}{R_1} C$

The circuit gives a scaled negative capacitor
(so for stability would need $C > -C_{eq}$ in a parallel load)