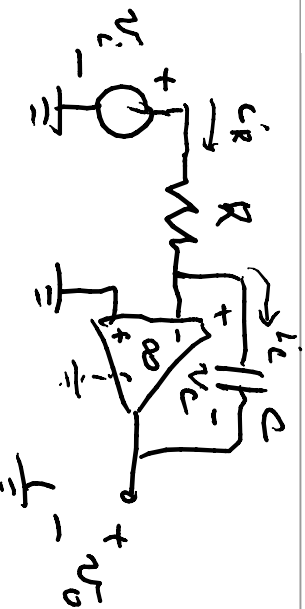


EE 610  
09/06/11

Note Title


9/5/2011



$i_R = v_i/R = i_C = AC \cdot v_i$   
 $v_o = -v_c$  by virtual ground  
 at OP-amp input

$$\frac{v_o}{R} = AC(-v_o)$$

$$\frac{v_o}{v_i} = \frac{-1}{RAC}$$

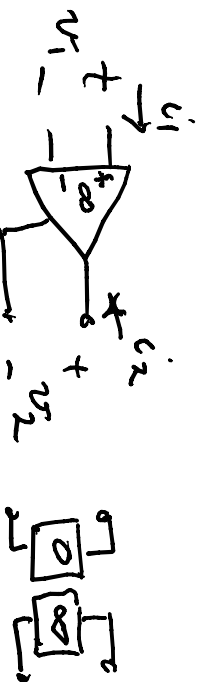

$$\begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

describes a nullor


input = nullator  $v_i = i = 0$



output = norator  $\Rightarrow v_i = \text{arbitrary}$   
 $i_i = \text{arbitrary}$



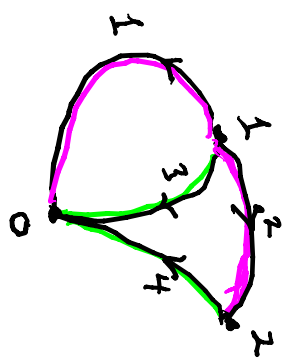Use KCL, KVL & laws of components  
use graph theory:



$$i_b = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix}_b, \quad v_b = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix}_b$$



$$v_T = \text{tree branch voltages} = \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}_b, \quad v_L = \text{links} = \begin{bmatrix} v_3 \\ v_4 \end{bmatrix}_b$$

$$i_L, i_R$$

$$i_b = \sigma^T i_R, \quad v_b = C^T v_T \iff \text{KCL, KVL}$$


forces in from outside  $\equiv 0 = v_b^T \cdot i_b = [v_1, v_2, v_3, v_4] \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix}_b$

$$0 = v_b^T \sigma^T i_R \quad \text{holds for all } i_R$$

$$\implies v_b^T \sigma^T = 0 = [0, \dots, 0] \implies 0 = \sigma^T v_b$$

$$0 = v_b^T C i_b \quad \text{holds for all } v_T \implies 0 = C i_b$$

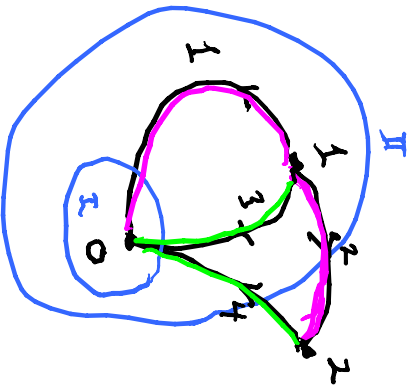$C = \text{cut set matrix, } t \times b \text{ matrix,}$   $t = \# \text{ of branches in the tree}$   
 $\mathcal{J} = \text{tie set matrix, } l \times b \text{ matrix}$   $b = \# \text{ of branches}$   
 $b = t + l$   $l = \# \text{ of links}$



$$[0] = C L_b = \begin{bmatrix} 1 & 0 & 1 & 1 \\ 0 & 1 & 0 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix}$$

$\underbrace{\quad}_{1_t}$   $\underbrace{\quad}_{k_l}$

*parameters*  
*linearly independent KCL*



$$\begin{bmatrix} 0 \\ 0 \end{bmatrix} = \mathcal{J} v_b = \begin{bmatrix} -1 & 0 & 1 & 0 \\ -1 & 1 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix}$$

$\underbrace{\quad}_{k_t}$   $\underbrace{\quad}_{1_l}$

*parameters*  
*linearly independent KVL*

here  $k_r = -k_i^T$        $P = 0 = v_b^T l_b = v_b^T e \sigma^T l_r \Rightarrow e \sigma^T = 0_{t \times r}$

$$0_{t \times r} = \begin{bmatrix} 1 & \vdots & k_i^T \\ -1 & \vdots & k_i^T \end{bmatrix} \begin{bmatrix} k_r^T \\ 1_r \end{bmatrix} \Rightarrow 0 = 1 \cdot k_r^T + k_i^T \cdot 1_r \Rightarrow k_i^T = -k_r^T$$

$$Av = Bi$$

$$v_b \downarrow \left\{ \begin{matrix} v_b = \\ 0_{t-}^+ e \end{matrix} \right. \Rightarrow v_b = v + e$$

in the example:  $e = \begin{bmatrix} e_1 \\ 0 \\ 0 \\ 0 \end{bmatrix}$

$$\begin{bmatrix} G & 0 & 0 & 0 \\ 0 & ac & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} \quad G = 1/R$$

leaves for components