

graph = set of lines & dots (= nodes)
(lines have dots at each end)

connected graph = travel on lines from any node to any other





$b = \#$ of lines = branches, $n = \#$ dots = nodes

oriented graph, put an arrow on each branch numbered, put a unique number on each branch and on each node




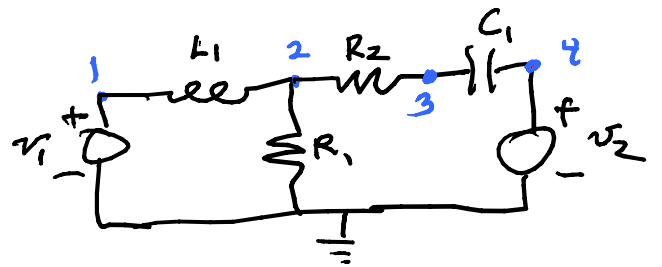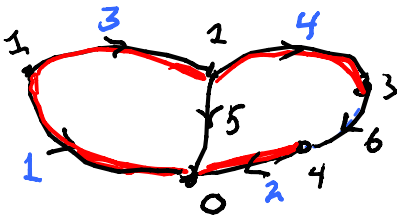a tree in a connected graph = set of branches on which can travel to any node but no closed paths



→ tree branch $t=4, n=5, b=6, \lambda=1 = \#$ of separate parts
 $n = t + 1, b = t + \lambda, \lambda = 2$
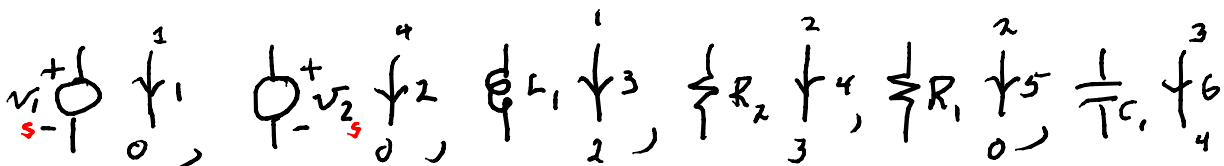
$$O_4 = C I_b, O_2 = T V_b, V_b = E^T V_t, I_b = T^T I_t \quad \left. \vphantom{O_4} \right\} \text{ laws of connection}$$



$$i_b = i + j$$

$$v_b = v + e$$

$e =$ voltage sources
 $j =$ current sources

$$i_b = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix}, \quad e = \begin{bmatrix} v_{1s} \\ v_{2s} \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}, \quad j = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}, \quad \begin{bmatrix} 1 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & \frac{1}{L_1 R} & 0 & 0 \\ 0 & 0 & 0 & G_2 & 0 \\ 0 & 0 & 0 & 0 & G_1 \\ 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix}$$

branch by
branch
admittance
sub matrix

linear components
 $A v = B i$

$$v = v_b - e, \quad i = i_b - j, \quad A v = B i$$

$$\downarrow$$

$$A v_b - A e = B i_b - B j$$

$$A v_b - B i_b = A e - B j$$

$$A e^T v_t - B j^T i_x = A e - B j$$

$$= \underbrace{\begin{bmatrix} A e^T & -B j^T \end{bmatrix}}_{\text{circuits}} \underbrace{\begin{bmatrix} v_t \\ i_x \end{bmatrix}}_{\text{unknowns}} = \underbrace{A e - B j}_{\text{sources}}$$

⇐ circuit equations
for linear circuits

$$= [E^{(1)} - Q] x = u$$

$u = \text{input}$

$x = \text{semi state, if } A = d/dt$

old example:

$$e = \begin{bmatrix} e_1 \\ 0 \\ 0 \\ 0 \end{bmatrix}, \quad i_b = j^T i_x = \begin{bmatrix} -1 & -1 \\ 0 & 1 \\ 1 & 0 \\ 0 & 1 \end{bmatrix} i_x, \quad v_b = C^T v_t = \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ 1 & 0 \\ 1 & -1 \end{bmatrix} v_t$$

$$\begin{bmatrix} G & 0 & 0 & 0 \\ 0 & 2G & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix}$$

$$\begin{bmatrix} G & 0 & 0 & 0 \\ 0 & aC & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ 1 & 0 \\ -1 & -1 \end{bmatrix} v_t + \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} 1 & -1 \\ 0 & 1 \\ -1 & 0 \\ 0 & 1 \end{bmatrix} i_L =$$

$$\begin{bmatrix} G & 0 & 0 & 0 \\ 0 & aC & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} e_1 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} Ge_1 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

correction

$$\begin{bmatrix} G & 0 & 1 & -1 \\ 0 & aC & 0 & -1 \\ 1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 0 \end{bmatrix} \begin{bmatrix} v_t \\ \vdots \\ i_L \end{bmatrix} = \begin{bmatrix} Ge_1 \\ 0 \\ 0 \\ 0 \end{bmatrix} \Rightarrow \left\{ \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & aC & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix} + \begin{bmatrix} G & 0 & 1 & -1 \\ 0 & 0 & 0 & -1 \\ 1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 0 \end{bmatrix} \right\} x$$

input

$$\begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix} \frac{dx}{dt} = \begin{bmatrix} -G & 0 & 1 & -1 \\ 0 & 0 & 0 & -1 \\ -1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 0 \end{bmatrix} x + \begin{bmatrix} G \\ 0 \\ 0 \\ 0 \end{bmatrix} e_1 \Rightarrow \underbrace{E \frac{dx}{dt} = Ax + Bu}_{\text{semi-state equations}}$$

$$y = Cx, \quad x = \begin{bmatrix} v_t \\ \vdots \\ i_L \end{bmatrix} \doteq \text{semistate}$$

output

$$u = e_1 \text{ (a scalar here)}$$