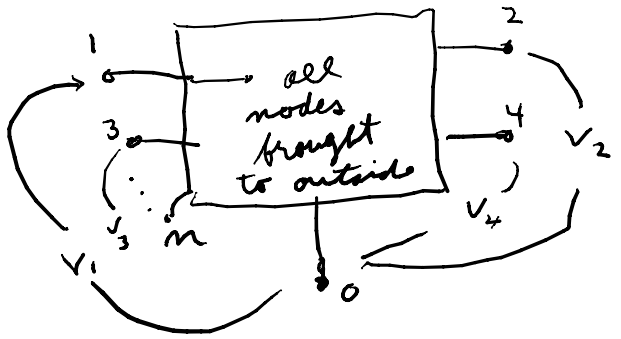


$$Y = \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix} = -Y^T$$

$$v_1 = V_1 - V_3, \quad v_2 = V_2 - V_4$$



$$I_1 = i_1 \quad I_2 = i_2$$

$$I_3 = -i_1 \quad I_4 = -i_2$$



$$I = Y_{\text{nodal}} V$$

Ex:

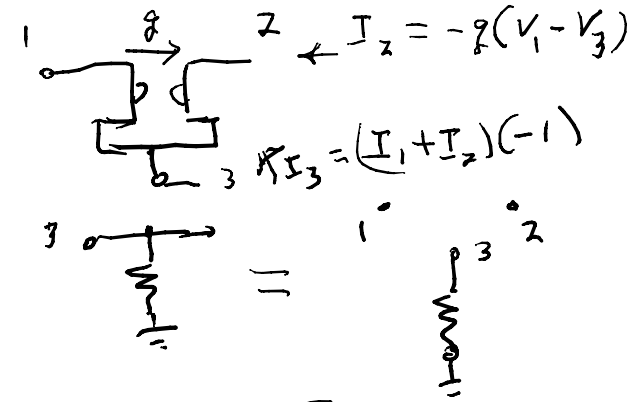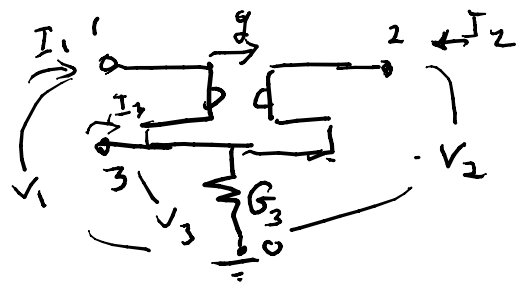


$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} Y_{\text{nodal}} = \underbrace{\begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & G_3 \end{bmatrix}}_{\text{for } G_3} + \underbrace{\begin{bmatrix} 0 & g & -g \\ -g & 0 & g \\ g & -g & 0 \end{bmatrix}}_{\text{for the g's}} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

(indefinite; \sum of row entries = 0
 \sum of coln entries = 0)

$$Y_{\text{nodal}} = \begin{bmatrix} 0 & g & -g \\ -g & 0 & g \\ g & -g & G_3 \end{bmatrix}$$

to get in general use indefinite admittances

move ground off of circuit

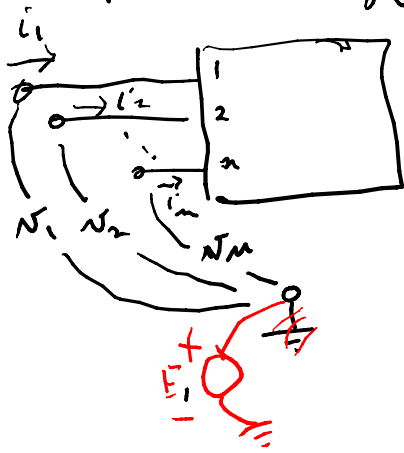

by KCL $\sum_{j=1}^n i_j = 0$; $i = Y v$

$$= \begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i_m \end{bmatrix} = \begin{bmatrix} y_{11}v_1 + y_{12}v_2 + \dots \\ y_{21}v_1 + y_{22}v_2 + \dots \\ \vdots \\ y_{m1}v_1 + \dots \end{bmatrix}$$

shows if choose $v_k = 1$, $k=j$, $v_i = 0$

$$\sum_{j=1}^n y_{jk} \cdot 1 = 0 \text{ for a fixed } k \text{ for any } k$$

$1 \leq k \leq n$

\Rightarrow sum of entries in any column of this $Y = 0$


$$i = Y v + Y E \quad \text{choose the } v = 0, E = \begin{bmatrix} E_1 \\ \vdots \\ E_n \end{bmatrix}$$

$$\Rightarrow \text{sum of } y_{1k}E_1 + y_{2k}E_2 + \dots + y_{nk}E_n = 0$$

or $\sum y_{jk}$ in a row = 0

for this Y , call the indefinite Y_i , the sum of entries in a row is 0 and in a column is zero

Ex:

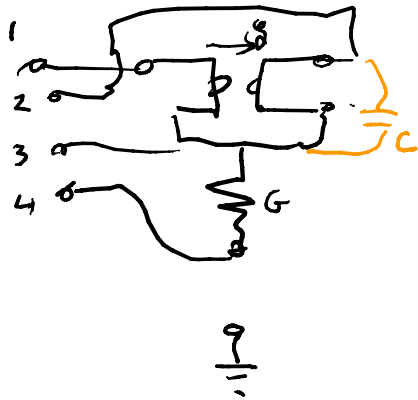


$$Y_{ind} = \begin{bmatrix} 0 & g & -g & 0 \\ -g & 0 & g & 0 \\ g & -g & G & G \\ 0 & 0 & G & G \end{bmatrix} + \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & AC & -AC & 0 \\ 0 & -AC & AC & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$

if bring the ground to node k , sets $v_k = 0$ so can remove the k th column (as multiply by 0)

can remove the k th row as the $i_k = \sum_{j \neq k} i_j$


gives Y_{nodal} . if want port descriptions we need

to "remove" internal nodes

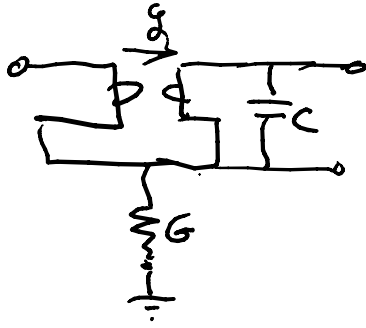

$$Y_{\text{nodal}} = \begin{bmatrix} 0 & g & -g \\ -g & sC & g-sC \\ \hline g & -g-sC & G+sC \end{bmatrix}$$

grounded node 4

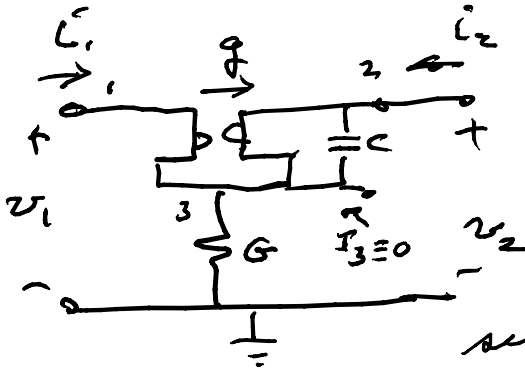

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ \hline Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

$$I_3 = 0 = Y_{21} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + Y_{22} \cdot v_3$$

$$\Rightarrow v_3 = -Y_{22}^{-1} Y_{21} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = Y_{11} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + Y_{12} \cdot v_3 = \left[Y_{11} - Y_{12} Y_{22}^{-1} Y_{21} \right] \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$


$$\Rightarrow Y_{2\text{-port}} (2 \times 2) = Y_{11} - Y_{12} Y_{22}^{-1} Y_{21}$$

$$= \begin{bmatrix} 0 & g \\ -g & sC \end{bmatrix} - \begin{bmatrix} -g \\ g-sC \end{bmatrix} \frac{1}{G+sC} \begin{bmatrix} g & -g-sC \end{bmatrix}$$

$$Y_{2\text{-port}} = \begin{bmatrix} 0 & g \\ -g & sC \end{bmatrix} + \begin{bmatrix} -g \\ g-sC \end{bmatrix} \begin{bmatrix} -g & g+sC \end{bmatrix} \frac{1}{G+sC}$$

$$\begin{bmatrix} g^2 & -g^2 - g sC \\ -g^2 + sCg & g^2 - s^2 C^2 \end{bmatrix} \frac{1}{G+sC}$$

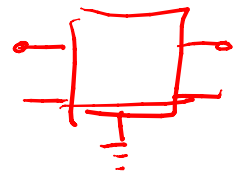
$$Y(s) = \begin{bmatrix} \frac{g^2}{G+sC} & g + \frac{-g^2 - g sC}{G+sC} \\ -g - \frac{g^2 - g sC}{G+sC} & sC + \frac{g^2 - s^2 C^2}{G+sC} \end{bmatrix}$$



$$= \frac{1}{s + G/C} \begin{bmatrix} g^2/C & -\frac{g}{C}(g-G) \\ -\frac{g}{C}(g+G) & \frac{g^2}{C} + sG \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ 0 & G \end{bmatrix} + \frac{1}{s + G/C} \begin{bmatrix} g^2/C & -\frac{g}{C}(g-G) \\ -\frac{g}{C}(g+G) & \frac{g^2}{C} - G^2 \end{bmatrix}$$

residue at ∞ singular residue @ $s = -G/C \Rightarrow \delta[Y] = 1$

assume we got a 2-port $Y(s)$

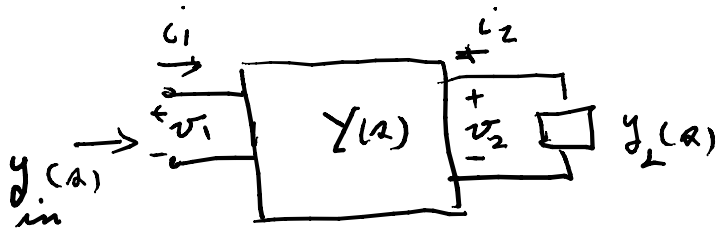

find y_{in} given $Y(s)$
& $y_L(s)$

$$-i_2 = y_L(s) v_2 = -y_{21} v_1 - y_{22} v_2$$

solve for v_2 in terms of $v_1 \Rightarrow -y_{21} v_1 = (y_L + y_{22}) v_2$


$$v_2 = \frac{-y_{21}}{y_L + y_{22}} v_1 ; i_1 = y_{11} v_1 + y_{12} v_2$$

$$= (y_{11} - y_{12} (y_L + y_{22})^{-1} y_{21}) v_1$$

$$\frac{i_1}{v_1} = \frac{y_{11} y_L + y_{11} y_{22} - y_{12} y_{21}}{y_L + y_{22}} = \frac{y_{11} y_L + \Delta_y}{y_L + y_{22}} , \Delta_y = \det Y = y_{11} y_{22} - y_{12} y_{21}$$

$$y_{in} = \frac{y_{11} y_L + \Delta_y}{y_L + y_{22}}$$

Ex:

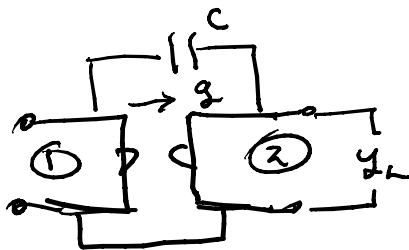

$$Y_{2-port} = \begin{bmatrix} aC & g - aC \\ -g - aC & aC \end{bmatrix}$$

$$\begin{aligned} \Delta_y &= (aC)(aC) - (g - aC)(-g - aC) \\ &= (aC)^2 - (-g^2 + a^2 C^2) \\ &= g^2 \end{aligned}$$

$$y_{in} = \frac{aC \cdot y_L + g^2}{y_L + aC}$$