

$$y_{in}(y_L + \mathcal{A}C) = \mathcal{A}C \cdot y_L + g^2$$

$$Y_{coupling} = \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix} + \begin{bmatrix} \mathcal{A}C & -\mathcal{A}C \\ -\mathcal{A}C & \mathcal{A}C \end{bmatrix} = \begin{bmatrix} \mathcal{A}C & g - \mathcal{A}C \\ -g - \mathcal{A}C & \mathcal{A}C \end{bmatrix}$$

$$-y_L v_2 = \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$y_{in} = \frac{\mathcal{A}C \cdot y_L + g^2}{y_L + \mathcal{A}C}$$

$$(-y_L - y_{22})v_2 = y_{21}v_1$$

$$\Rightarrow v_2 = -(y_L + y_{22})^{-1} y_{21} v_1$$

$$i_1 = y_{11}v_1 + y_{12}v_2 = \left[y_{11} - y_{12}(y_L + y_{22})^{-1} y_{21} \right] v_1$$

$$\frac{i_1}{v_1} = y_{in} = y_{11} - y_{12}(y_L + y_{22})^{-1} y_{21}$$



$$= \mathcal{A}C - (g - \mathcal{A}C) \frac{1}{y_L + \mathcal{A}C} \cdot (-g - \mathcal{A}C)$$

$$= \frac{\mathcal{A}C y_L + \mathcal{A}C^2 - (-g^2 + \mathcal{A}^2 C^2)}{y_L + \mathcal{A}C} = \frac{g^2 + \mathcal{A}C y_L}{y_L + \mathcal{A}C}$$

$$y_{in} \cdot y_L + y_{in} \cdot \mathcal{A}C = g^2 + \mathcal{A}C y_L$$

$$(y_{in} - \mathcal{A}C) y_L = g^2 - y_{in} \mathcal{A}C \Rightarrow y_L(\mathcal{A}) = \frac{g^2 - y_{in}(\mathcal{A}) \cdot \mathcal{A}C}{y_{in} - \mathcal{A}C}$$

(like a Richards' function) p.361

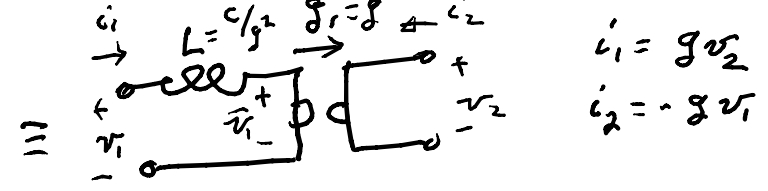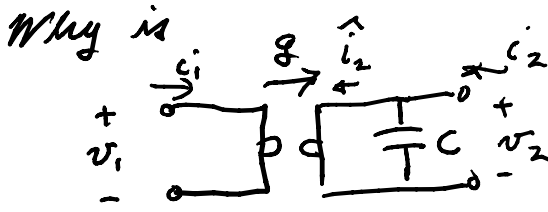

$$i_1 = g v_2$$

$$i_2 = -g v_1$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 & g \\ -g & aC \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$i_1 = \frac{1}{aL} \cdot (v_1 - \hat{v}_1) = g_1 v_2 \Rightarrow \hat{v}_1 = v_1 - aL g_1 v_2$$

$$i_2 = -g_1 \hat{v}_1 = -g_1 [v_1 - aL g_1 v_2]$$

$$i_1 = g v_2$$

$$i_2 = aC v_2 + (-g v_1)$$


$$\Rightarrow \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 & g_1 \\ -g_1 & aL g_1^2 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$Y = \begin{bmatrix} 0 & g \\ -g & aC \end{bmatrix} = \begin{bmatrix} 0 & g_1 \\ -g_1 & aL g_1^2 \end{bmatrix} \text{ if } g_1 = g$$

$$L g_1^2 = L g^2 = C$$

$$\Rightarrow L = C/g^2$$

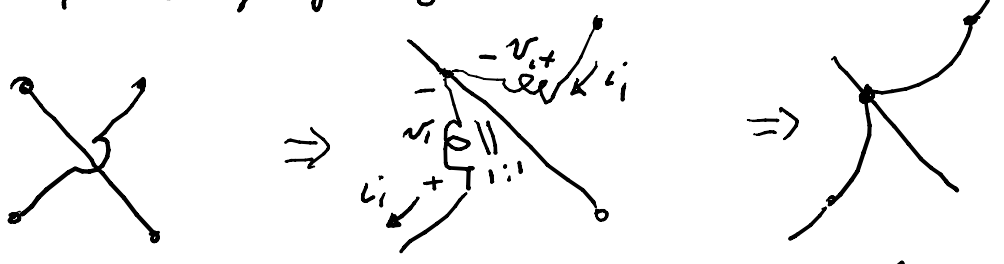To get a planar graph from a nonplanar one



allows preservation of circuit equations

Semistate equation

$$E \dot{x} = Ax + Bu$$

$$y = Cx$$

Let $P = \text{nonsingular} \Rightarrow PE \dot{x} = PAx + PB \cdot u$

$$y = Cx$$

here x is a k -vector

A is $k \times k \Rightarrow P$ is $k \times k$, u is an n -vector

y is an m -vector

Let Q be nonsingular & $X = Q \hat{x}$; $\hat{x} = Q^{-1} X$

$$PEQ \hat{x} = PAQ \hat{x} + PB u$$


$$y = CQ \hat{x}$$

preserver $T(a) U(a) = Y(a)$

$$T(a) = C(Ea - A)^{-1} B = CQ (PEQ - PAQ)^{-1} PB$$

$$CQ (P[Ea - A]Q)^{-1} PB$$

$$i_1 = y_{11} u$$

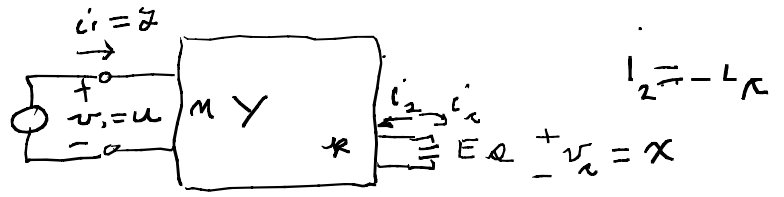

$$y = i_1 = y_{11} v_1 + y_{12} v_2 = y_{11} u + y_{12} x$$

$$i_2 = -E x v_2 = y_{21} v_1 + y_{22} v_2 = y_{21} u + y_{22} x$$

$$E \dot{x} = -y_{22} x - y_{21} u$$

$$E \dot{x} = A x + B u$$

$$i_1 = y = y_{12} x + y_{11} u$$

$$y = C x + D u$$

↓

$$Y = \begin{bmatrix} D & C \\ -B & -A \end{bmatrix}$$

$$i_2 = E = 1_{1 \times 1}$$

$$Y = \frac{(Y + Y^T)}{2} + \frac{(Y - Y^T)}{2}$$

Symmetric
resistors

skew symmetric
gyrators

given $\dot{x} = A x + B u$

$$E \dot{\hat{x}} = \hat{A} \hat{x} + \hat{B} u$$

$$y = C x + D u$$

$$y = \hat{C} \hat{x}$$