


$$i_1 = y_{11}v_1 + y_{12}v_2$$

$$i = y_c v = 1$$

$$y_{11} = \alpha C$$


$$Y = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$$

$$y_{11} = \left. \frac{i_1}{v_1} \right|_{v_2=0}, \quad y_{12} = \left. \frac{i_1}{v_2} \right|_{v_1=0} = -y_{11}$$

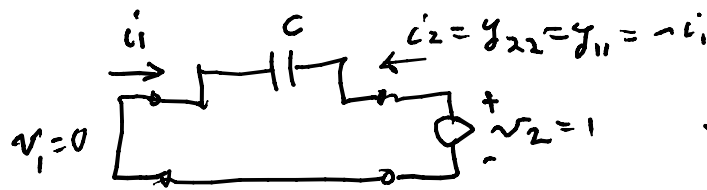

$$Y = \begin{bmatrix} \alpha C & -\alpha C \\ -\alpha C & \alpha C \end{bmatrix}$$

$$y_{12}$$

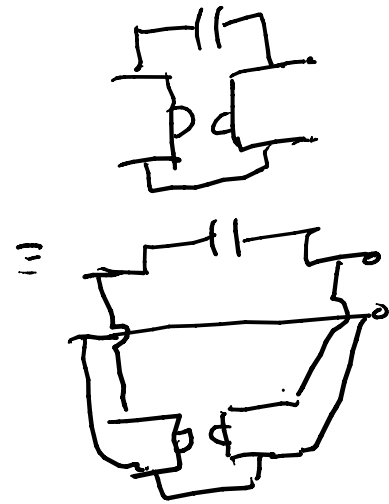

$$T(s) = \frac{1}{s+a}, \quad a > 0; \quad \mathcal{L}[f(t)] = \int_{-\infty}^{\infty} f(t) e^{-st} dt$$


$$\text{if } f(t) = e^{-at} u(t), \quad u(t) = \begin{cases} 1 & \text{if } t > 0 \\ 0 & \text{if } t < 0 \end{cases}$$



$$\begin{aligned} \mathcal{L}[e^{-at} u(t)] &= \int_{-\infty}^{\infty} e^{-at} u(t) e^{-st} dt = \int_0^{\infty} e^{-(s+a)t} dt \\ &= \left. \frac{-1}{s+a} e^{-(s+a)t} \right|_{t=0}^{t=\infty} = \frac{1}{s+a} + \frac{-1}{s+a} e^{-(s+a)\infty} \end{aligned}$$

$s = \sigma + j\omega$

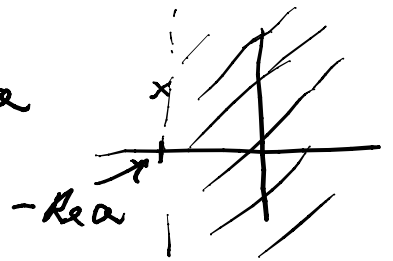we require $\text{Re}(s+a) > 0 \Rightarrow \sigma > -\text{Re}a$




if $f(t) = -e^{-at} u(-t)$ is not causal


$$\mathcal{L}[-e^{-at} u(-t)] = \int_{-\infty}^{\infty} -e^{-at} u(-t) e^{-st} dt$$

$$= - \int_{-\infty}^0 e^{-(s+a)t} dt = \left. \frac{-1}{s+a} e^{-(s+a)t} \right|_{t=-\infty}^{t=0} = \frac{1}{s+a} - \frac{1}{s+a} e^{(s+a)\infty}$$

needs $\text{Re}(s+a) < 0$

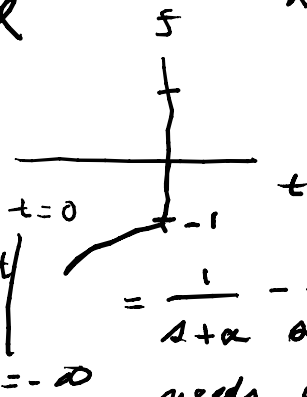


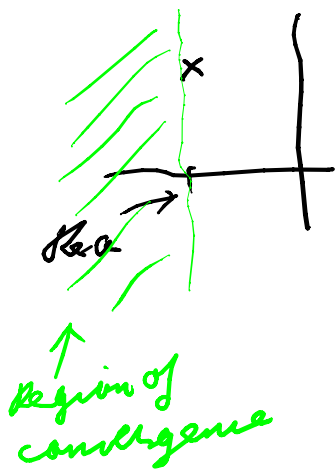i.e. $T(s) = \frac{1}{s+a} \Rightarrow S(f) = -e^{-at} \mathbb{1}(t)$ if $\text{Re } a < \text{Re } a$



\Rightarrow is to go back to time from $T(s)$
we need the region of convergence in s

Return to passive

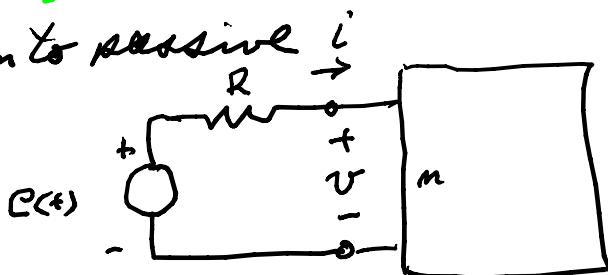

$e = Ri + v$
normalize $R = 1 \Omega$

$$e^{T^*} e(t) = (i+v)^{T^*} (i+v) = i^{T^*} i + v^{T^*} i + i^{T^*} v + v^{T^*} v$$

$$= i^{T^*} i + 2 \text{Re } v^{T^*} i + v^{T^*} v$$

$$\int_{-\infty}^t e^{T^*} e(\tau) d\tau = \int_{-\infty}^t \sum_{i=1}^n |e_i|^2 d\tau \quad \text{assume finite for all } t \text{ also for } t=\infty$$

assume this to have e in L_2

$$= \int_{-\infty}^t (i^{T^*} i + 2 \text{Re } v^{T^*} i + v^{T^*} v) d\tau \Rightarrow \text{if the circuit is passive } v \& i \text{ are } L_2 \text{ functions}$$

this is power

This means $\mathcal{L}[v]$ & $\mathcal{L}[i]$ exist
 $s = j\omega \quad z = j\omega$

Look at Parseval's result:

$$\int_{-\infty}^{\infty} F^*(j\omega) G(j\omega) \frac{d\omega}{2\pi} = \int_{-\infty}^{\infty} f^*(\tau) g(\tau) d\tau$$

$$\frac{\mathcal{L}[v]^* \mathcal{L}[i]}{s = j\omega} \geq 0$$

add on $\mathcal{L}[i]^* V$


$i^{T^*} v$

$$\int_{\sigma=j\omega} v^{*T} (Y(s) + Y^*(s)) |V| \frac{ds}{2\pi} = \int v^{*T} L + L^T v \, ds \geq 0$$

for any constant vectors v

$$\Rightarrow v^{*T} (Y(s) + Y^*(s)) |V| \text{ needs to be } \geq 0$$

↑
no poles in $\sigma > 0$

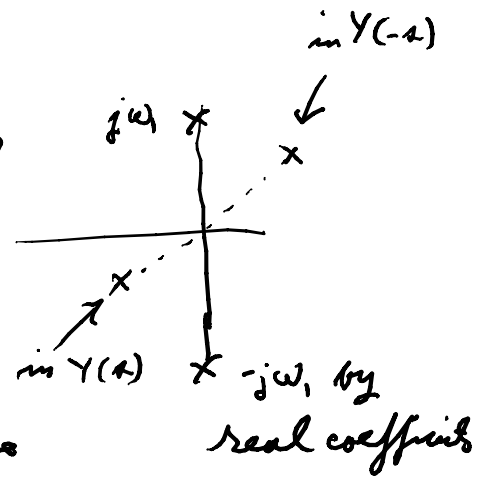

for $Y(s) = Y^*(s)$

poles on $s = j\omega$ are simple with positive

real residue (real)

$$Y(s) \approx \frac{k}{s + j\omega_1} + \frac{k}{s - j\omega_1} = \frac{2k s}{s^2 + \omega_1^2}$$

near the pole

near the pole $Y(s) + Y(-s) \approx \frac{2k s}{s^2 + \omega_1^2} + \frac{-2k s}{s^2 + \omega_1^2} \approx 0$

here $\frac{Y(s) + Y(-s)}{2} = \text{Ev } Y(s)$

$$\frac{Y(s) + Y^*(s)}{2} = \text{Re } Y(s) = \text{Ev } Y(s) \text{ if } s = j\omega$$

for $Y(s)$ rational with real coefficients

then $\text{Ev } Y(s)$ is rational

$$e^{-Y(s)} = |e^{-Y(s)}|$$

$$= |e^{-\text{Re } Y(s)}| \cdot |e^{-j \text{Im } Y(s)}| = |e^{-\text{Re } Y(s)}| \text{ max on } j\omega \text{ axis}$$

at $\sigma > 0$

$$e^{jx} = \cos x + j \sin x$$

$$|e^{jx}| = \sqrt{\cos^2 x + \sin^2 x} = 1$$

$$= e^{-\text{Re } Y(j\omega)} \text{ then}$$

$$\Rightarrow \frac{1}{e^{\text{Re } Y(s)}} \Rightarrow \text{Re } Y(s) \geq 0$$

in $\sigma > 0$

do an analytic continuation off of $s = j\omega$

$$Y(j\omega) \rightarrow Y(s) \text{ is analytic in } \sigma > 0$$

$\omega = s/j$



$\Rightarrow Y(s)$ is positive real, PR for rational case

To create a circuit, use Richards' function, p. 361
 1st do LC synthesis \Rightarrow lossless; $P_{in}(j\omega) \equiv 0$

$$\sum \text{Res } y = y(s) + y(-s) = 0$$

all poles are on $\sigma = j\omega$
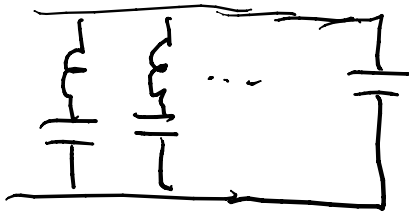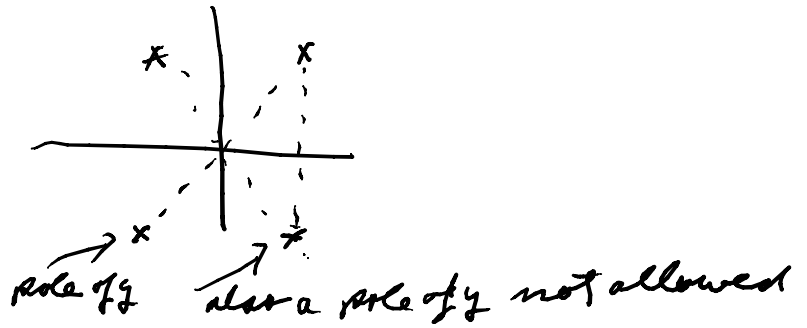
$$y(s) = \sum \frac{2k_i s}{(s^2 + \omega_i^2)} + k_\infty s$$



gives this circuit
 (and Foster form)