

- PR scalar  $y(s)$
- 1) coefficients real      real elements
  - 2) no poles in open RHP      stable
  - 3)  $\operatorname{Re} y(s) \geq 0$  in the open RHP      passive

SSS = sinusoidal steady state;  $s = j\omega$

average power  $\operatorname{Re} V^* I \geq 0$ ;  $\operatorname{Re}(V^* I) = \frac{V^* I + V I^*}{2}$

if  $I = Y(j\omega) V \Rightarrow 2 \operatorname{Re}(V^* I) = V^* Y(j\omega) V + V Y^*(j\omega) V^*$   
 (scalar)  $= V^* V (Y(j\omega) + Y^*(j\omega))$   
 $= |V|^2 (Y(j\omega) + Y(-j\omega))$  if PR  
 $= |V|^2 (Y(s) + Y(-s))$   
 $s = j\omega$

$\operatorname{Re} y(s) = \frac{y(s) + y^*(s)}{2}$ ,  $\operatorname{Ev} y(s) = \frac{y(s) + y(-s)}{2}$  = analytic in  $\sigma$

if  $\operatorname{Re} V^* I = 0$  in SSS we call "lossless"

$\Rightarrow$  no poles of  $y(s)$  outside of  $j\omega$  axis if lossless  $y(s)$



near such a pole  $y(s) \approx \frac{k}{(s - j\omega_0)^n}$

desire to know  $n=1$ ,  $k$  real

$y(s) \approx \frac{k}{(s - j\omega_0)^n} = \frac{|k| e^{j\Delta k}}{|s - j\omega_0|^n e^{m\angle(s - j\omega_0)}} = \frac{|k|}{|s - j\omega_0|^n} e^{j(\Delta k - n\angle(s - j\omega_0))}$

$\operatorname{Re} y(s) = \left| \frac{k}{s - j\omega_0} \right|^n \cos(\underbrace{\Delta k - n\angle(s - j\omega_0)}_{\theta})$  must be  $\geq 0$   
 for  $y(s)$  to be PR

$\Delta \sin \theta > 0$   
 on a small  
 ripple

$\Rightarrow -\frac{\pi}{2} < \theta \leq \frac{\pi}{2}$

requires  $\Delta k = 0$ ,  $n=1$

$\Rightarrow$  poles on  $j\omega$  axis are simple with positive residues ( $k=0$ )


If  $y(s)$  is LPR (= lossless PR) then all poles are on  $j\omega$  axis & simple with positive residue (also any pole comes with its conjugate)

$$y(s) = \sum_{i=1}^m \left( \frac{k_i}{s - j\omega_i} + \frac{k_i}{s + j\omega_i} \right) + \frac{k_0}{s} + k_\infty s$$


partial fraction expansion

$$= \sum_{i=1}^m \frac{k_i [2s]}{s^2 + \omega_i^2} + \frac{k_0}{s} + k_\infty s = -y(-s)$$

can synthesize:  $y_i(s) = \frac{2k_i s}{s^2 + \omega_i^2} = \frac{1}{\frac{s}{2k_i} + \frac{\omega_i^2}{2k_i s}} = \frac{1}{z_i(s)}$
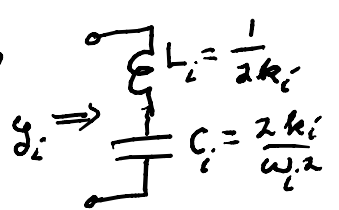
$$z_i(s) = \frac{s}{2k_i} + \frac{\omega_i^2}{2k_i s} \Rightarrow$$

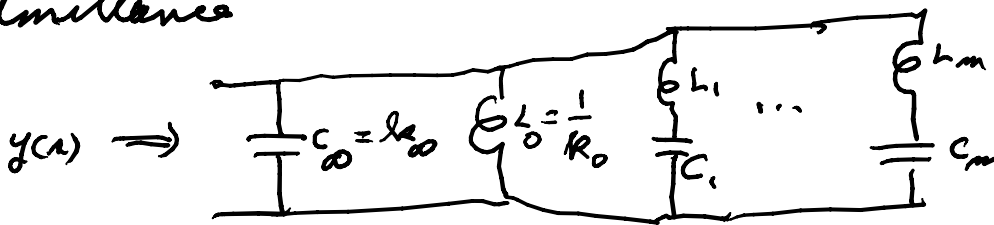
Synthesis of a lossless 1-port PR admittance



minimal as  $S[y] = 2m + 2$  is number of reactive elements (L's & C's)


Look on  $s = j\omega$  at

$$y(j\omega) = \sum_{i=1}^m \frac{2k_i(j\omega)}{-\omega^2 + \omega_i^2} + \frac{k_0}{j\omega} + k_\infty j\omega = jB(\omega)$$

$$\frac{dB(j\omega)}{d\omega} = k_\infty + \frac{k_0}{\omega^2} + \sum_{i=1}^m \frac{2k_i}{(-\omega^2 + \omega_i^2)} - \frac{2k_i \omega (-2\omega)}{(-\omega^2 + \omega_i^2)^2}$$

$$= k_\infty + \frac{k_0}{\omega^2} + \sum_{i=1}^m \frac{2k_i(\omega^2 + \omega_i^2)}{(-\omega^2 + \omega_i^2)^2} \geq 0$$

$B(\omega)$

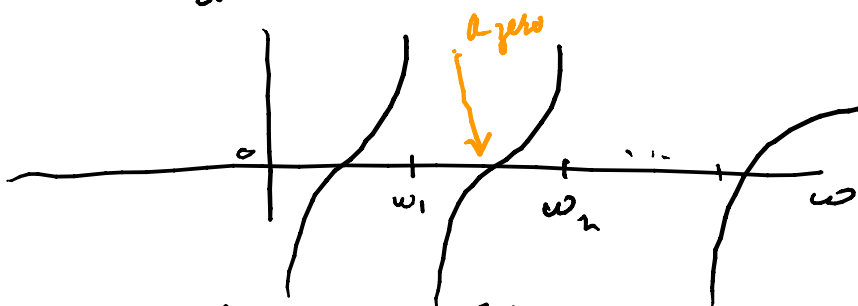

as  $\frac{dB}{d\omega} > 0$

$\therefore$  poles and zeros alternate on  $j\omega$  axis for a lossless PR  $y(s)$


same for  $Z(s)$

Ex:  $Y(s) = \frac{1}{s} \frac{(s^2+1)}{(s^2+2)}$  is PR & lossless,  $Y(s) = -Y(-s)$

$$= \frac{k_0}{s} + \frac{2k_1 s}{s^2+2} \Rightarrow$$

$$\times 1 \left. \frac{s}{s} \frac{(s^2+1)}{(s^2+2)} \right|_{s=0} = k_0 + \frac{2k_1 s^2}{s^2+2} \Big|_{s=0} \Rightarrow k_0 = 1/2$$

$= 0 @ s=0$

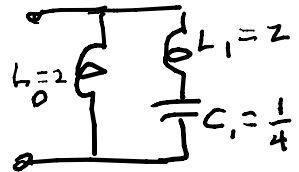

2nd Foster


$$\times \frac{s^2+2}{s} \left. \frac{s^2+2}{s^2} \cdot \frac{s^2+1}{s^2+2} \right|_{s^2=-2} = \frac{k_0(s^2+2)}{s^2} + 2k_1 \Rightarrow \frac{s^2+1}{s^2} \Big|_{s^2=-2} = \frac{-2+1}{-2} = +1 = 2k_1$$

$= 0 @ s^2 = -2$

$$Y(s) = \frac{1/2}{s} + \frac{1/2 s}{s^2+2} = \frac{1/2 s^2 + 1 + 1/2 s^2}{s(s^2+2)} = \frac{s^2+1}{s(s^2+2)}$$

$$Z(s) = \frac{s(s^2+2)}{s^2+1} = s + \frac{2k_1 s}{s^2+1} \Rightarrow 2k_1 = \left. \frac{s^2+2}{s^2+1} \right|_{s^2=-1} = 1$$


$$= s + \frac{2s}{s^2+1}$$

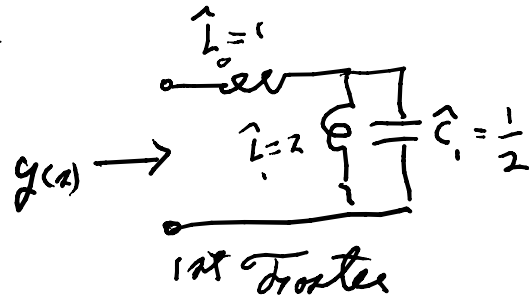

$$Z(s) \Rightarrow \frac{s}{(s^2+1)} \left[ \begin{array}{r} s \leftarrow \beta_0 \\ \hline s^3 + 2s \\ s^3 \rightarrow s \\ \hline s \\ \hline s^2+1 \end{array} \right]$$

$$s \left[ \begin{array}{r} s \leftarrow \beta_0 \\ \hline s^2+1 \\ \hline s^2 \\ \hline 1 \\ \hline s \leftarrow \beta_1 \\ \hline s \\ \hline 0 \leftarrow \end{array} \right]$$

continued fraction about  $s = \infty$

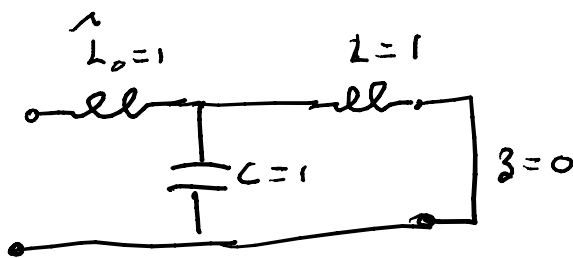

1st Ladder

gives a ladder

2nd Ladder  $\Rightarrow$  continued fraction expansion about  $s=0$   
i.e. lowest power of  $s$  into lowest power of  $s$

