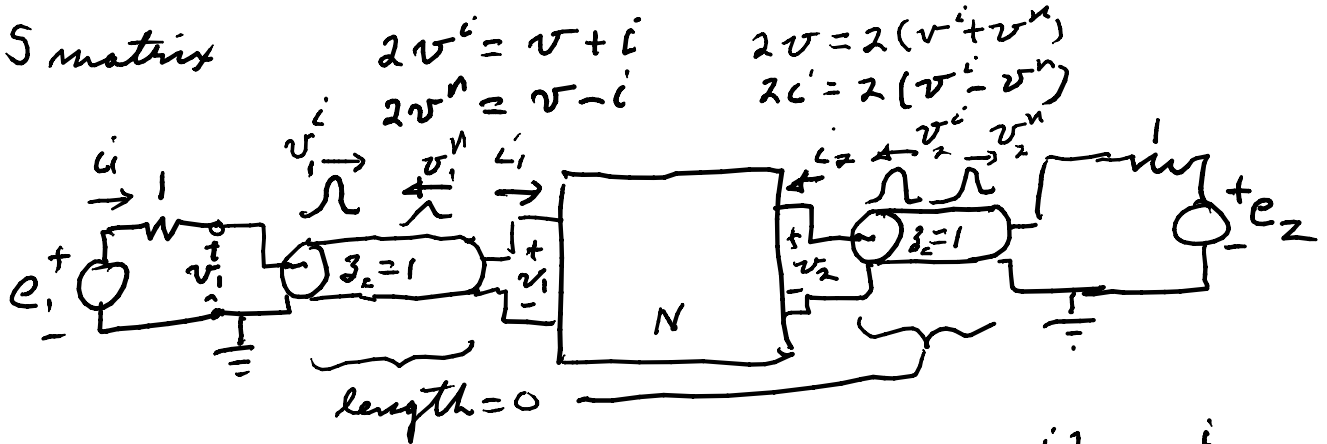


S matrix



$$v^n = S v^i \Rightarrow \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} v_1 + i_1 \\ v_2 + i_2 \end{bmatrix} = \begin{bmatrix} 2v_1^i \\ 2v_2^i \end{bmatrix} = 2v^i$$

$$\text{if } e_2 = 0 \Rightarrow v_2 = -i_2 \Rightarrow v_2^i = 0$$

$$2v_2^n = v_2 - i_2 = 2v_2 \Rightarrow v_2 = v_2^n$$

$$v^n = \begin{bmatrix} v_1^n \\ v_2^n \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} v_1^i \\ v_2^i \end{bmatrix} \quad \text{for } e_2 = 0 \Rightarrow v_2^i = 0$$

$$\Rightarrow v_2^n = S_{21} v_1^i = S_{21} \frac{1}{2} e_1$$

$$S_{21} = \frac{2v_2^n}{e_1} \Rightarrow S_{21} \text{ is the loaded voltage transfer function}$$

$$\text{also } v^n = S v^i \Rightarrow \frac{1}{2}(v - i) = S \frac{1}{2}(v + i)$$

$$\Rightarrow v - S v = i + S i =$$

$$(1_n - S)v = (1_n + S)i$$

$$\text{but } i = \gamma v \Rightarrow i = (1_n + S)^{-1} (1_n - S) \cdot v$$

$$\gamma = (1_n + S)^{-1} (1_n - S) = \frac{(1_n - S)(1_n + S)^{-1}}{1}$$


or see

$$\times (1_n + S) \text{ on left} \Rightarrow (1_n + S)(1_n + S)^{-1} (1_n - S) = 1_n - S \stackrel{?}{=} (1_n + S)(1_n - S)(1_n + S)^{-1}$$

$$\text{on right} \Rightarrow (1_n - S)(1_n + S) \stackrel{?}{=} (1_n + S)(1_n - S)$$

$$1_n + S - S - SS \stackrel{?}{=} 1_n - S + S - SS$$

as time can go backwards if  $(I_m + S)^{-1}$  exists

Ex:   $\Rightarrow Y = \begin{bmatrix} ca & -ca \\ -ca & +ca \end{bmatrix} = ca \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix}$

need S as a function

$$(I_m + S)Y = (I_m - S) \Rightarrow Y + SY = I_m - S$$

$$(I_m + Y)S = -I_m - S$$

$$Y - I_m = -SY - S = -S(I_m + Y)$$

$$S = (I_m - Y)(I_m + Y)^{-1}$$

$$S = \left\{ \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} - ca \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix} \right\} \left\{ \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} + ca \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix} \right\}^{-1}$$

$$= \begin{bmatrix} 1-ca & ca \\ ca & 1-ca \end{bmatrix} \begin{bmatrix} 1+ca & -ca \\ -ca & 1+ca \end{bmatrix}^{-1} \quad \det(I+Y) = 1+2ca$$

$$= \begin{bmatrix} 1-ca & ca \\ ca & 1-ca \end{bmatrix} \frac{1}{1+2ca} \begin{bmatrix} 1+ca & ca \\ ca & 1+ca \end{bmatrix} =$$


$$S_{11} = \frac{1-ca^2+ca^2}{1+2ca} = \frac{1}{1+2ca}, \quad S_{12} = \frac{(1-ca)ca + (1+ca)ca}{1+2ca}$$

$$= \frac{2ca}{1+2ca}$$

$$S = \frac{1}{1+2ca} \begin{bmatrix} 1 & 2ca \\ 2ca & 1 \end{bmatrix}$$

we know  $Y(ca) = -Y(-ca)$  for a lossless  $Y$

$$\Rightarrow S(ca)S(-ca) = I_m$$

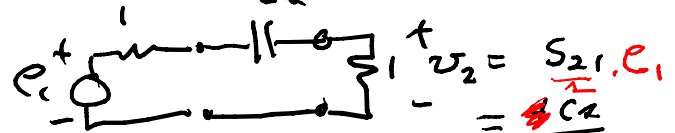

lossless  $Y(ca) = -Y(-ca)^T = -Y_x^T$

$$\frac{v_2}{e_1} = \frac{1}{2 + \frac{1}{ca}} = \frac{ca}{2ca+1} = \frac{1}{2} S_{21}$$

$$(I_m + S)^{-1} (I_m - S) = - \left\{ \begin{bmatrix} I_m + S_x \\ I_m - S_x \end{bmatrix} \right\}^{-1} \begin{bmatrix} I_m - S_x \\ I_m + S_x \end{bmatrix} \begin{bmatrix} I_m + S_x \\ I_m - S_x \end{bmatrix}^T$$

$$= (-I_m + S_x^T) (I_m + S_x)$$

$$(I_m - S) (I_m + S_x^T) = (I_m + S) (-I_m + S_x^T)$$


$$(I_m - S) (I_m + S_x^T) = (I_m + S) (-I_m + S_x^T)$$

$$1 - S + S_x^T - S S_x^T = -\mathbf{1}_m - S + S_x^T + S S_x^T$$

$$2\mathbf{1}_m = 2S S_x^T \Rightarrow S \cdot S_x^T = \mathbf{1}_m$$

$$\Rightarrow S^{-1} = S_x^T \Rightarrow \text{lossless condition}$$

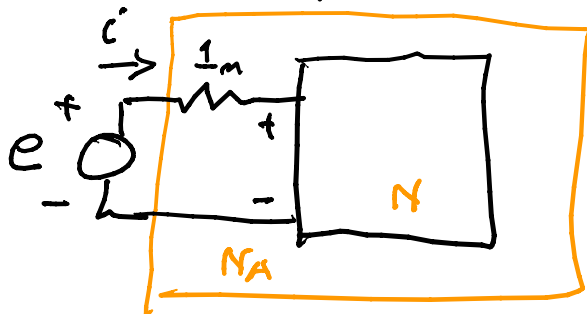for passive  $S$  has no poles in  $\sigma \geq 0$



augmented

$$e = 2v^i = v + i; \quad i = Y_A \cdot e = Y_A(v + i) \Rightarrow Y_A v = (\mathbf{1}_m - Y_A) i^i$$

$$2Y_A v^i = Y_A e = Y_A v + Y_A i = \mathbf{1}_m i^i - Y_A i^i + Y_A i^i = i^i$$

$$2 \cdot v^n = v - i^i$$

$$2Y_A v^n = Y_A v - Y_A i^i = (\mathbf{1}_m i^i - Y_A i^i) - Y_A i^i = (\mathbf{1}_m - 2Y_A) i^i$$

$$= (\mathbf{1}_m - 2Y_A) \cdot 2Y_A v^i$$

$$= (2Y_A - 4Y_A^2) v^i = 2Y_A (\mathbf{1}_m - 2Y_A) v^i$$

$$v^n = (\mathbf{1}_m - 2Y_A) v^i \Rightarrow S = \mathbf{1}_m - 2Y_A$$

this has loss in  $Y_A$  (as had series resistors)

$\therefore S$  has no poles in  $\sigma \geq 0$

here  $S$  will exist for "any" passive circuit

$$A \cdot v = B \cdot i \Rightarrow A(v^i + v^n) = B \cdot (v^i - v^n)$$

$$(A - B)v^i = (B - A)v^n \Rightarrow v^n = (B + A)^{-1} (B - A)v^i$$

$$\Rightarrow S = (B + A)^{-1} (B - A) \quad \text{for } Z, A = \mathbf{1}_m, B = Z$$

$$S = (\mathbf{1}_m + Z)^{-1} (\mathbf{1}_m - Z)$$

$$Y_A v = (\mathbf{1}_m - Y_A) i^i \Rightarrow A = Y_A, B = \mathbf{1}_m - Y_A$$

$$S = (\mathbf{1}_m - Y_A + Y_A)^{-1} (\mathbf{1}_m - Y_A - Y_A) = \mathbf{1}_m - 2Y_A$$

$$S = \frac{1}{1+2ca} \begin{bmatrix} 1 & 2ca \\ 2ca & 1 \end{bmatrix} \quad \text{form } S S_x^T \stackrel{?}{=} \mathbf{1}_2$$

$$\frac{1}{1+2ca} \begin{bmatrix} 1 & 2ca \\ 2ca & 1 \end{bmatrix} \begin{bmatrix} 1 & -2ca \\ -2ca & 1 \end{bmatrix} \frac{1}{1-2ca} \stackrel{?}{=} \frac{1}{1-4c^2a^2} \begin{bmatrix} 1-4c^2a^2 & 0 \\ 0 & 1-4c^2a^2 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$$

Condition for passive, rational; BR = bounded real

1) S has real coefficients

2) S no poles in  $\sigma \geq 0$

3)  $\mathbf{1}_m - S(j\omega)S^T(-j\omega)$  is positive semidefinite

$$\Rightarrow v_{j\omega}^{iT} \left[ \mathbf{1}_m - S(j\omega)S^T(-j\omega) \right] v_{j\omega}^i \geq 0$$

for all  $v_{j\omega}^i$

next  $\Rightarrow$  sensitivity via adjoint