

ENEE 303 Final Exam – Fall 2012

150 points, open book, open notes. Notebooks are due at the end of the exam.


Good luck and have a good semester break

For the CMOS transistors assume $KP=3 \cdot 10^{-4}$, $|V_{TO}|=1$, $LAMBDA=\lambda=10^{-6}=0.000001$, $W=L=10^{-6}$. Use $V_{DD} = 10V$.

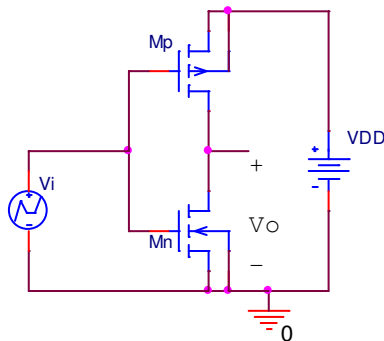1. (50 points)

For the following inverter, using the above transistor models, the input voltage, $v_i(t)$ is a triangular wave with period 2 rising linearly from 0V to $V_{DD}=10V$ in 2 seconds.


- Sketch (in separate sketches) the input, $v_i(t)$, and output, $v_o(t)$, voltages versus time, for 2 periods.
- Find the input voltage at which M_p switches from Ohmic (=triode) to Saturation.



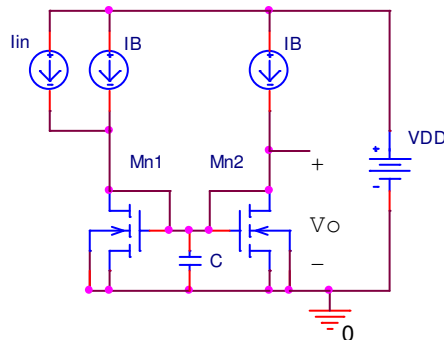2. (50 points)


The following circuit has the DC bias current as $I_B=0.6mA$ and the small signal input current as $i_{in}=0.0002\sin(t)$.

- Find g_m of $Mn1$ at the Q point V_o .
- Set up the differential equation for the small signal steady state output voltage solution, $v_{o_{ss}}(t)$. Assume C includes the two C_{gs} and is normalized to $C=2g_m$
- Assume $v_{o_{ss}}(t)=A\sin(t) + B\cos(t)$ determine A and B .
- Give the total output voltage, $v_o(t)$ [including bias]



3. (50 points,)

A new device has the following symbol

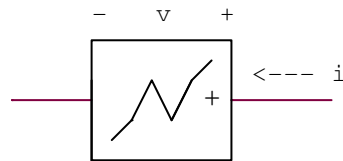

and is described by the 2-terminal device equation

$$i = v[1 + \sin(2\pi v)]$$

- Sketch the i versus v curve for $0 < v < +1$ giving values at $v=0, 1/4, 1/2, 3/4, 1$.
- Find the small signal conductance for any v in $0 < v < 1$.
- Draw the small signal equivalent circuit for the following circuit and give its small signal voltage gain transfer function, $T(s) = v_o/v_i(s)$.
- Find numerically the zeroes and poles of $T(s)$ if the battery voltage is $V_B = 1$ Volt, $C = 1$ Farad, and the load resistance, R_L , is chosen to give a Q point of $1/2$ Volt ($=V_O$) across the device.

