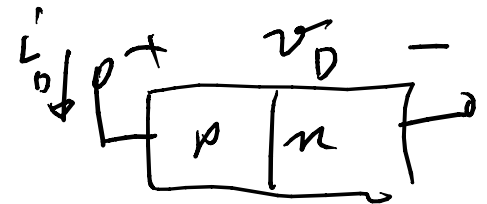






Parameters of interest in MOS models

K_P , W , L , $\lambda = \text{LAMBDA}$, V_{TO}


$\gamma = \text{GAMMA}$ threshold
 V_{GS} , $B = S$



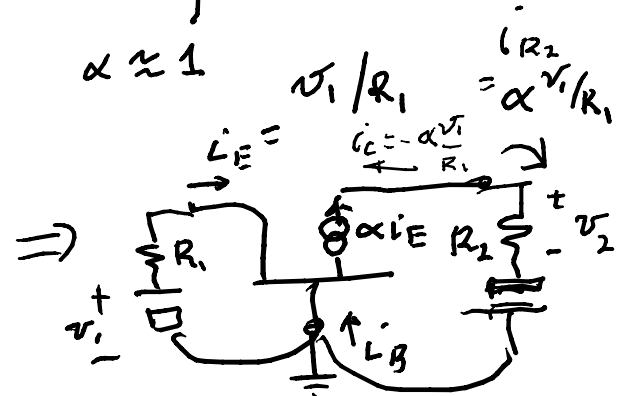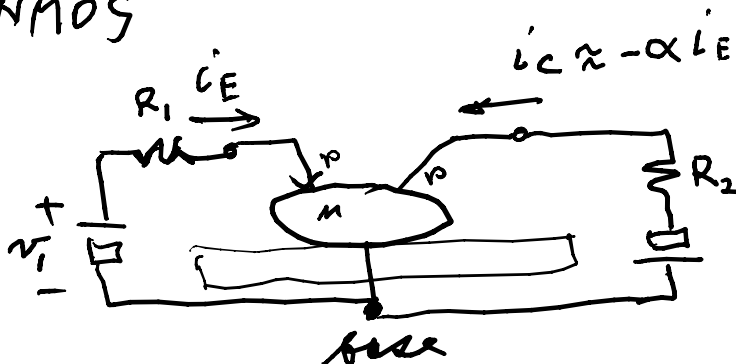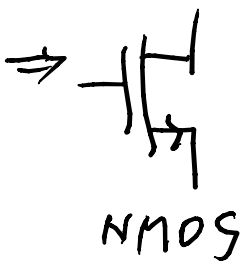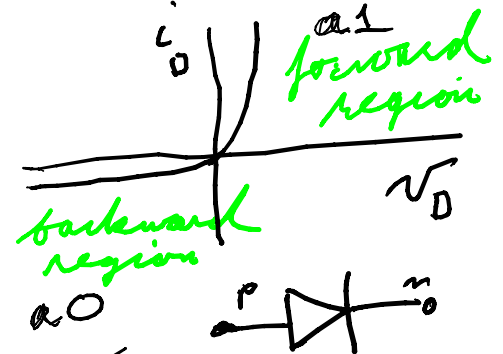
if $V_B < V_S$ these diodes are back biased only small bulk current; if $V_B = V_S$ then $i_B = 0$



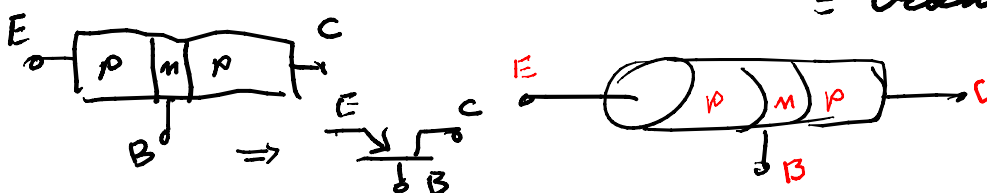
$$V_2 = \alpha \frac{V_1 \cdot R_2}{R_1} = \frac{\alpha R_2}{R_1} \cdot V_1 \Rightarrow \text{transfer resistor} = \text{transistor}$$



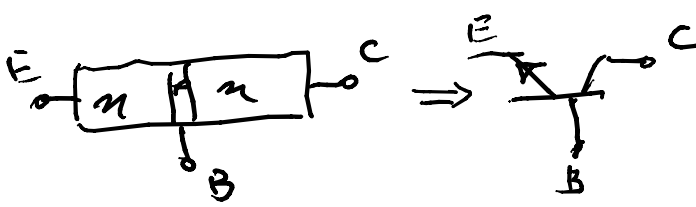
transfers small R_1 to larger R_2 gives voltage gain $V_2/V_1 = \alpha \frac{R_2}{R_1}$



voltage divides

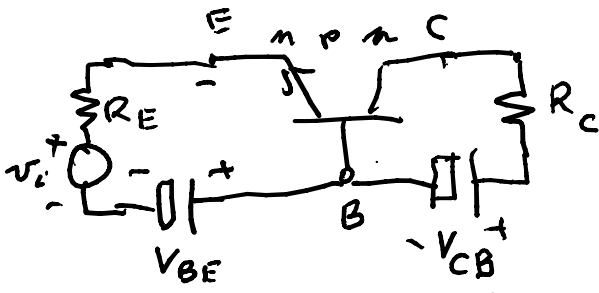

back biases
CB junction

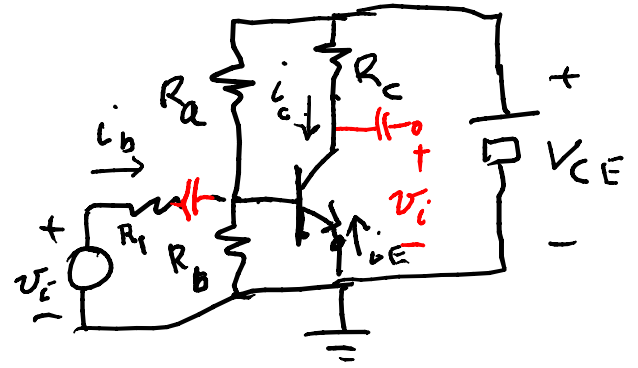

here inject i_b rather than i_E to get a large i_c




$$i_c + i_b + i_E = 0$$

$$i_b = -i_c - i_E = -i_c - (-\frac{1}{\alpha} i_c) = \frac{1-\alpha}{\alpha} i_c$$

$$\Rightarrow i_c = \frac{\alpha}{1-\alpha} i_b = \beta \cdot i_b$$

$$\beta R_2 \cdot i_b = R_2 i_c = V_2 \Rightarrow \frac{V_2}{V_1} = \frac{\beta R_2}{R_1}$$

$$i_b = V_1 / R_1$$

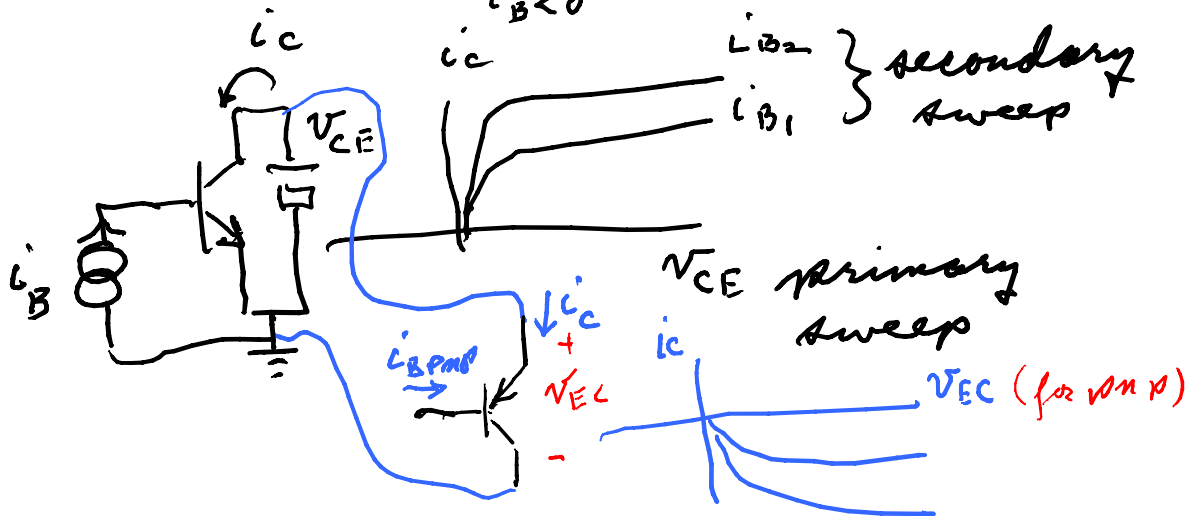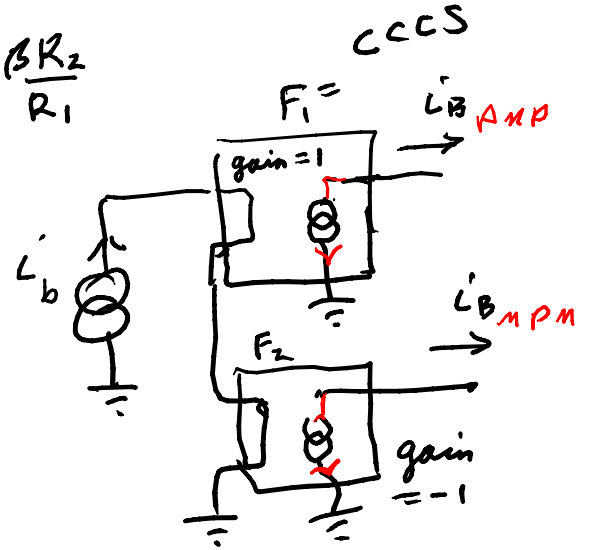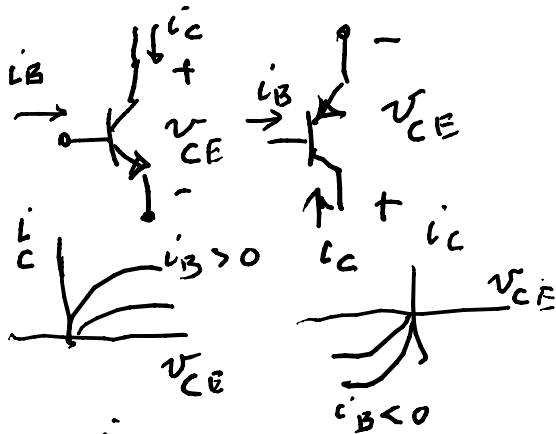

NMOS

