

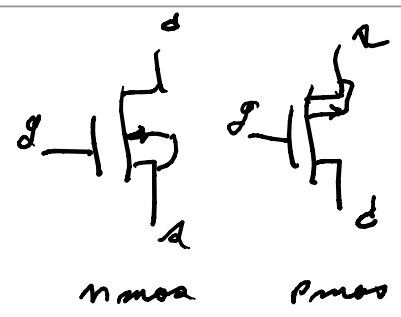
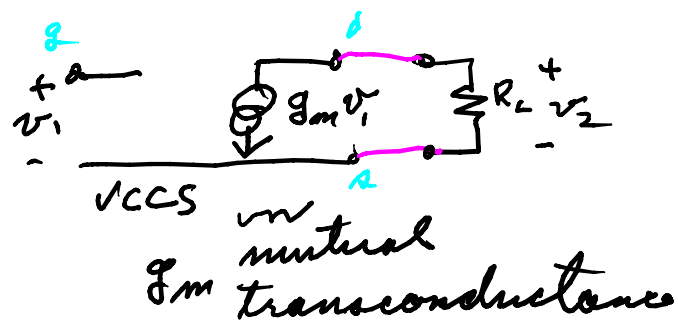




small signal near DC

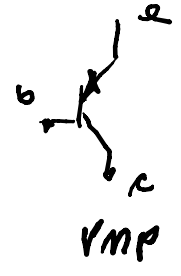





$\frac{v_2}{v_1} = -g_m R_L$

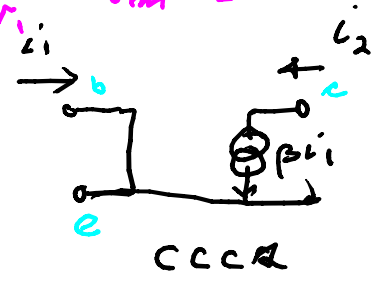



for higher frequencies & some loss

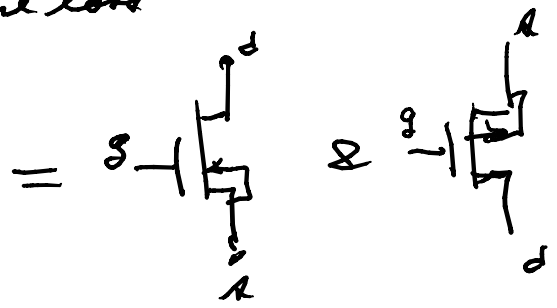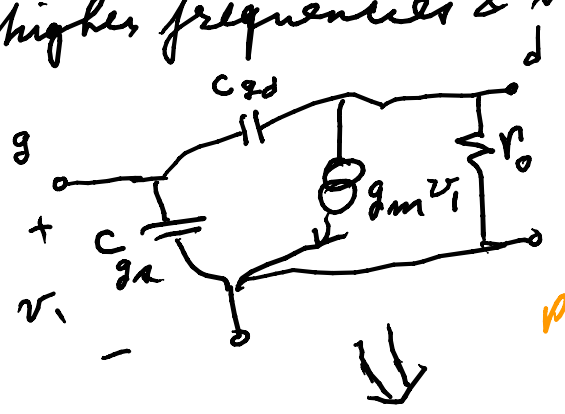


P. 705

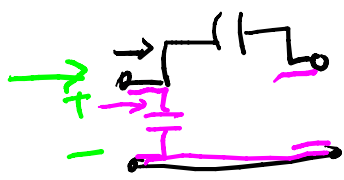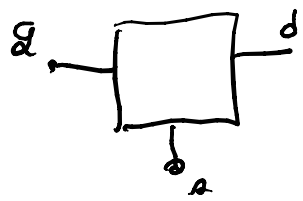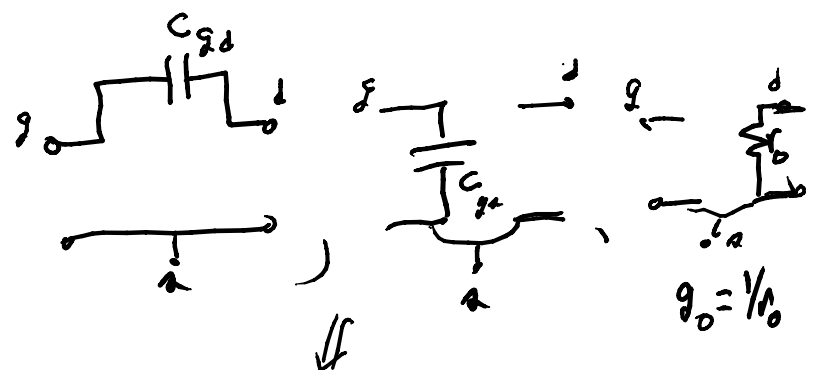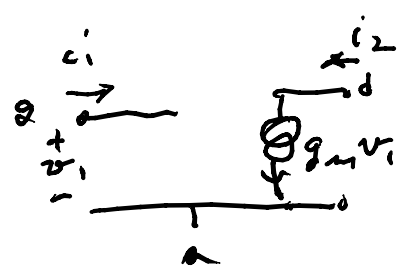
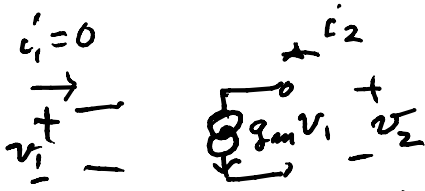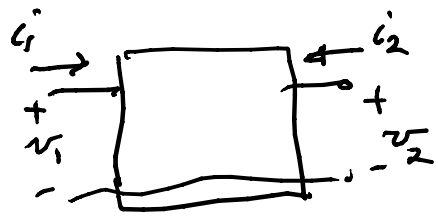
$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$



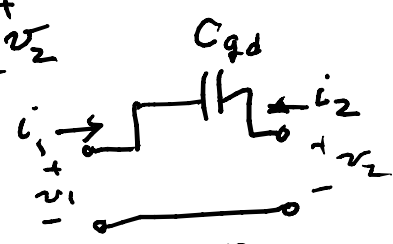
$$y_{gm} = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix}$$




$$Y_{Cgd} = \begin{bmatrix} \omega C_{gd} & -\omega C_{gd} \\ -\omega C_{gd} & \omega C_{gd} \end{bmatrix}$$
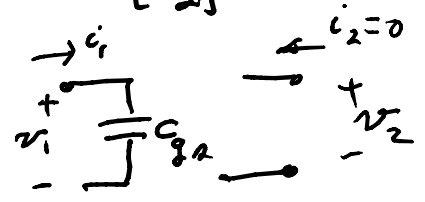
$$i = \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} \quad v = \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}; \quad i = Yv$$



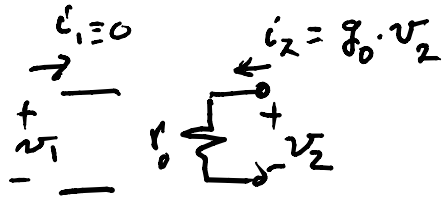
$$Y_{Cga} = \begin{bmatrix} \omega C_{ga} & 0 \\ 0 & 0 \end{bmatrix}$$



$$Y_{g0} = \begin{bmatrix} 0 & 0 \\ 0 & g_0 \end{bmatrix}$$

$$Y_{TH}(\omega) = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix} + \begin{bmatrix} \omega C_{gd} & -\omega C_{gd} \\ -\omega C_{gd} & \omega C_{gd} \end{bmatrix} + \begin{bmatrix} \omega C_{ga} & 0 \\ 0 & 0 \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ 0 & g_0 \end{bmatrix}$$


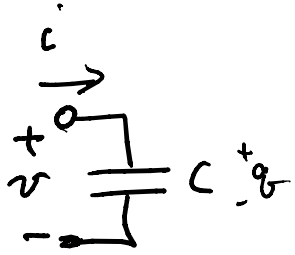
$$= \begin{bmatrix} \omega(C_{gd} + C_{ga}) & -\omega C_{gd} \\ g_m - \omega C_{gd} & \omega C_{gd} + g_0 \end{bmatrix}$$



$$i = \frac{dq}{dt} = \frac{dCv}{dt} = C \frac{dv}{dt} = \omega C \cdot v = y(\omega) v$$

C independent of time & v



$$q = Cv$$

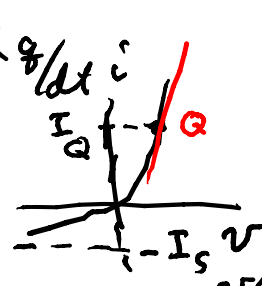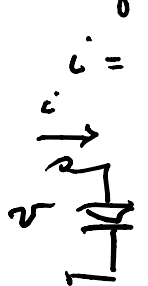

slope =  $\frac{di}{dv} \approx \frac{I_s}{V_T} \cdot \frac{1}{e^{v/V_T}} = \frac{I_Q}{V_T} = g_{diode}$



$$i = I_s (e^{v/V_T} - 1)$$

$\approx I_s e^{v/V_T}$  in forward bias

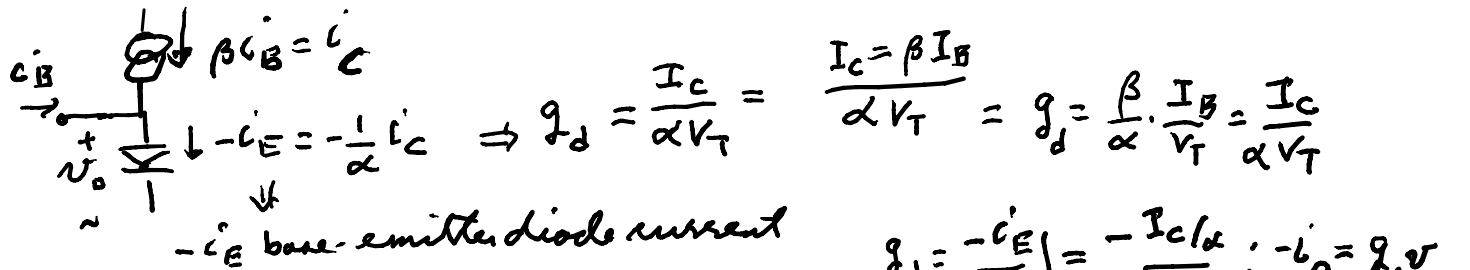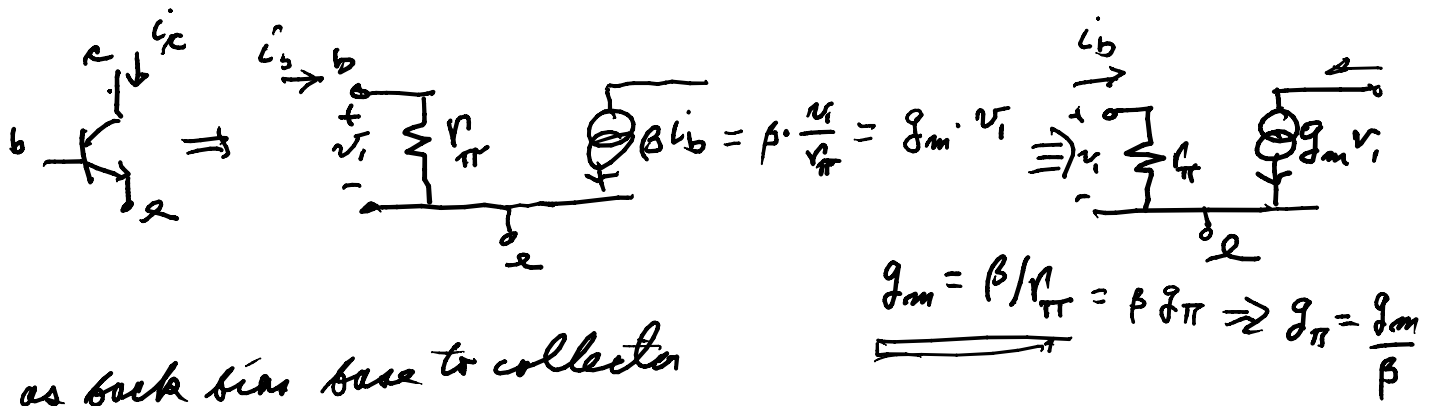

for  $g_{\pi} = \frac{1}{r_{\pi}} = \frac{i_b}{v_{be}} = \frac{\frac{1}{\beta} i_c}{v_{be}} = \frac{-\frac{i_e}{\alpha} \cdot \frac{1}{\beta}}{v_{be}} = \frac{\alpha}{\beta} \cdot \frac{i_e}{v_{be}}$
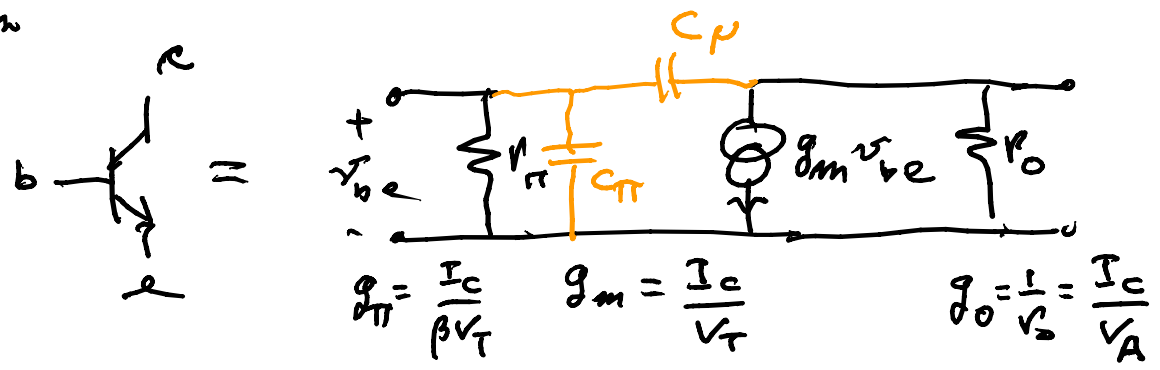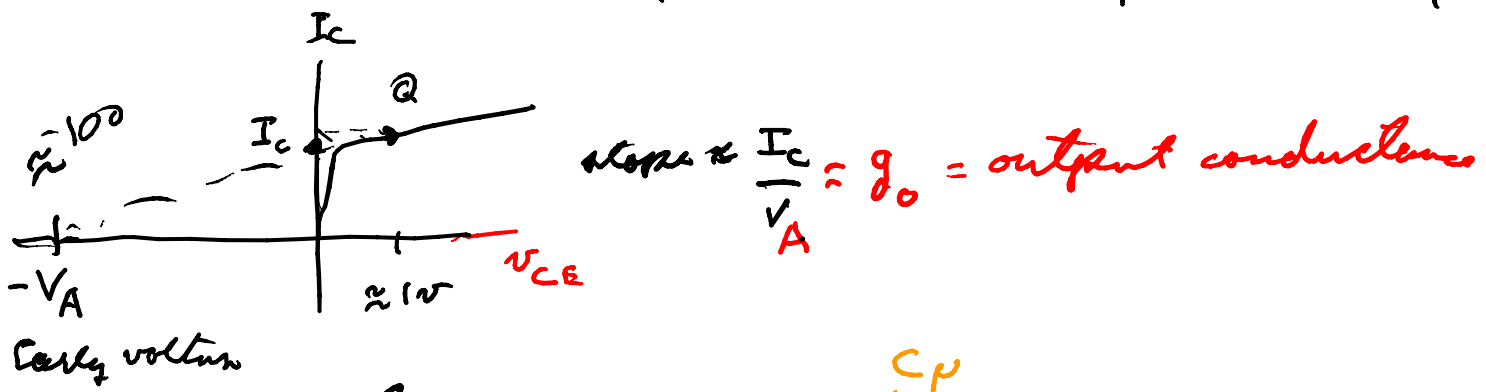
$$= \frac{1}{\beta} \cdot \frac{I_c}{v_T} = \frac{g_m}{\beta} \Rightarrow g_m = \frac{I_c}{v_T} ; g_{\pi} = \frac{1}{\beta} \frac{I_c}{v_T}$$



$\Rightarrow$  importance of  $I_c = Q$  pt. collector current

$\pi$ -equivalent p. 708