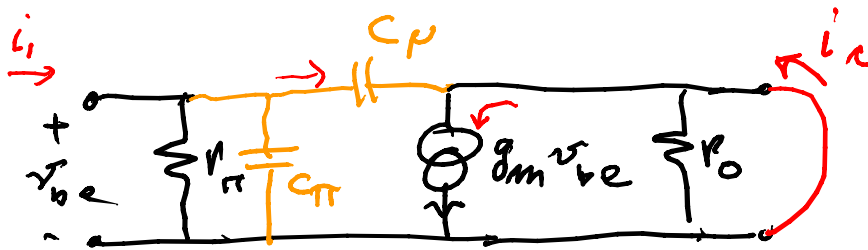


short circuit current gain of the intrinsic transistor



$$i_{cap} = C \frac{dv_c}{dt}$$

$$= AC v_c$$

$$y(\omega) = AC$$

$$i_o = g_m v_{be} - AC_{\mu} v_{be} = (g_m - AC_{\mu}) v_{be}$$

$$i_i = (g_{\pi} + AC_{\pi} + AC_{\mu}) v_{be}$$

$$\frac{i_o}{i_i} = \frac{g_m - AC_{\mu}}{g_{\pi} + A(C_{\pi} + C_{\mu})} \approx \frac{g_m}{g_{\pi} (1 + A \frac{C_{\pi}}{g_{\pi}})} = \frac{\beta}{(1 + A \frac{C_{\pi}}{g_{\pi}})}$$

@  $A=0 \equiv DC$      $\left. \frac{i_o}{i_b} \right|_{@DC} = \beta$  ;  $v = j\omega \Rightarrow \frac{i_o}{i_b} = \frac{\beta_0}{1 + j\omega \frac{C_{\pi}}{g_{\pi}}}$

act  $A = j\omega$

find at which  $\omega = \omega_T$

$$\left| \frac{i_o}{i_b}(j\omega_T) \right| = 1 \Rightarrow \beta_0 \approx \left| 1 + j\omega_T \frac{C_{\pi}}{g_{\pi}} \right| = \sqrt{1 + \left( \omega_T \frac{C_{\pi}}{g_{\pi}} \right)^2}$$


$$\frac{\beta_0^2}{(C_{\pi}/g_{\pi})^2} = \omega_T^2 \Rightarrow f_T = \frac{1}{2\pi} \cdot \frac{\beta_0}{C_{\pi}/g_{\pi}} = \text{transition frequency}$$

$$\Rightarrow \beta \rightarrow 1$$

Differential pairs  
BJT p. 613, Fig. 8.15


MOS p. 595, Fig. 8.5

op-amp p. 1003  
741

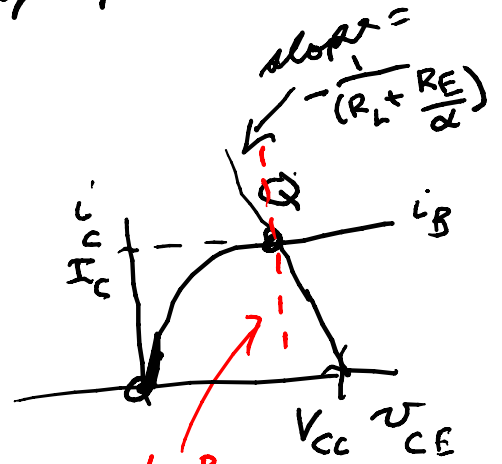

when  $R_E$  is bypassed

Biasing of BJT

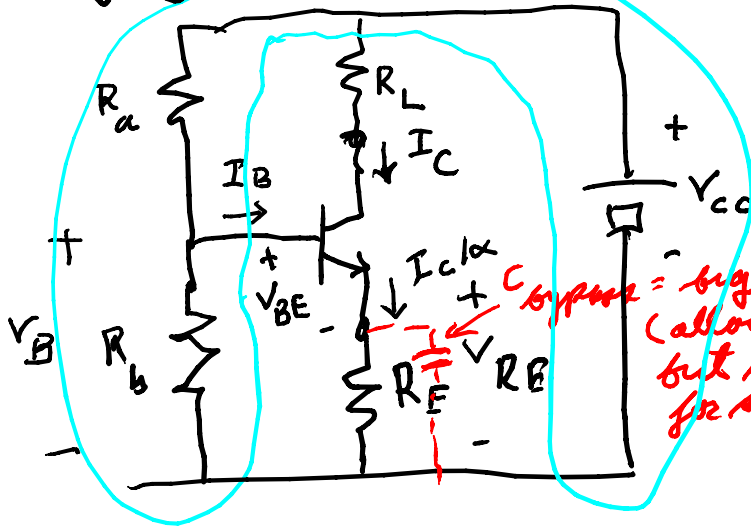



$R_E$  bypass = big (allows DC but shorts for signal)

if  $I_C \uparrow$  then due to  $R_E$ ;  $I_{BE} \downarrow$  & then  $I_C \downarrow$  due to feedback decreasing  $V_{BE}$   
(note  $I_C = \beta I_B$ )


assume  $V_{BE} = 0.7V$   
 $= V_B - V_{RE}$

$R_E$  prevents thermal runaway

by Thevenin's equivalent

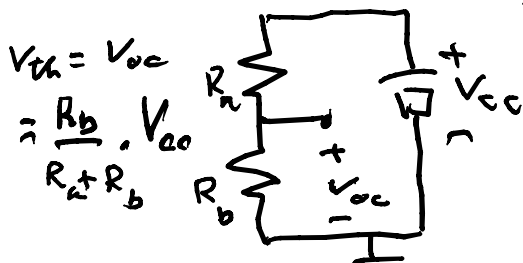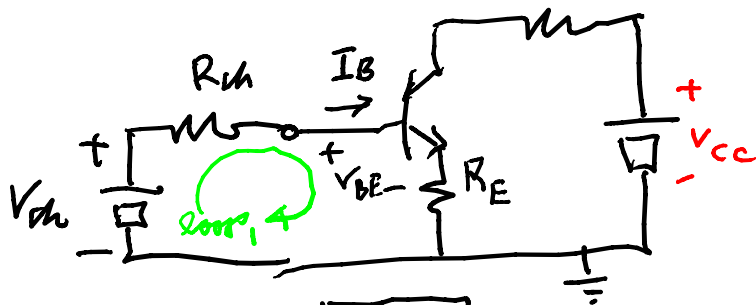

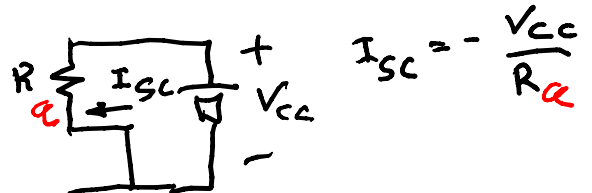$R_{th} = -\frac{V_{oc}}{I_{sc}} = -\frac{(\frac{R_b}{R_a + R_b}) \times V_{cc}}{-V_{cc}/R_a}$



$$= \frac{R_a R_b}{R_a + R_b}$$

by KVL:  $0 = -V_{th} + R_{th} I_B + V_{BE} + R_E \frac{I_C}{\alpha}$ ,  $I_C = \beta I_B$

Loop 1

$$0 = -\frac{R_b}{R_a + R_b} V_{CC} + \frac{R_a R_b}{R_a + R_b} \frac{I_C}{\beta} + V_{BE} + R_E \frac{I_C}{\alpha}$$

$$0 = -\frac{V_{CC}}{1 + \frac{R_a}{R_b}} + \left( \frac{1/\beta}{\frac{1}{R_b} + \frac{1}{R_a}} + \frac{R_E}{\alpha} \right) I_C + V_{BE}$$

design  $R_a$  &  $R_b$  given  $I_C$ ,  $\beta = \frac{\alpha}{1-\alpha}$ ,  $V_{BE}$  &  $V_{CC}$  &  $R_E$

choose 1 of  $R_a$  or  $R_b$  & check the other is  $> 0$