

$$\text{Ex: } g_m = \frac{I_C}{V_T}$$

$$V_T = 26 \times 10^{-3} \text{ V}$$

$$\text{choose } I_C = 2.6 \text{ mA}$$

$$g_m = \frac{2.6 \times 10^{-3}}{26 \times 10^{-3}} = \frac{1}{10} \text{ S}$$

$$g_o = I_C / V_A$$

$$g_{\pi} = \frac{I_C}{\beta V_T} = \frac{g_m}{\beta}, \text{ if } V_A = 130 = \text{Early voltage}$$

$$g_o = \frac{2.6 \times 10^{-3}}{1.3 \times 10^2} = 2 \times 10^{-5} \text{ S}$$

$$\text{if } \beta = 100$$

$$g_{\pi} = \frac{1}{10^3} = 10^{-3} \text{ S}$$

$$r_o = \frac{1}{g_o} = \frac{1}{2} \times 10^5 \Omega = 5 \times 10^4 \Omega = 50 \text{ k}\Omega$$

$$r_{\pi} = \frac{1}{g_{\pi}} = 10^3 \Omega = 1 \text{ k}\Omega$$

$$I_B = \frac{I_C}{\beta} = \frac{2.6 \times 10^{-3}}{102} = 26 \times 10^{-6} \text{ A}; \quad R_E = 1 \text{ k}\Omega \text{ (choose)}$$

$$V_{RE} = R_E \left(\frac{I_C}{\alpha} \right) \approx R_E I_C = 10 \times 2.6 \times 10^{-3} = 2.6 \text{ V}$$

$$\alpha = \frac{\beta}{\beta + 1} \text{ from } \beta = \frac{\alpha}{1 - \alpha}$$

$$V_{R_b} = V_{BE} + V_{RE} = 0.7 + 2.6 = 3.3 \text{ V}$$

$$I_{R_b} = \frac{V_{R_b}}{R_b} = \frac{3.3}{R_b}; \quad I_{R_a} = I_B + I_{R_b} \text{ by KCL @ Base}$$

$$= 26 \times 10^{-6} + \frac{3.3}{R_b} = \frac{V_{CC} - V_{R_b}}{R_a}$$

$$\text{Choose } V_{CC} = 9 \text{ V (battery)} \Rightarrow I_{R_a} = \frac{9 - 3.3}{R_a} = \frac{5.7}{R_a}$$

$$= 26 \times 10^{-6} + \frac{3.3}{R_b} = \frac{5.7}{R_a}$$


$$\text{Choose } R_a = \text{large} = 1 \text{ M}\Omega \Rightarrow 26 \times 10^{-6} + \frac{3.3}{R_b} = 5.7 \times 10^{-6}$$

then $\frac{3.3}{R_b} = (5.7 - 2.6) \times 10^{-6} < 0 \Rightarrow$ can't do with $R_a = 1M\Omega$

\therefore choose R_a smaller $\Rightarrow R_a = 100k\Omega = 10^5 \Omega$

$$\frac{5.7}{10^5} = 57 \times 10^{-6} = 26 \times 10^{-6} + \frac{3.3}{R_b} \Rightarrow \frac{3.3}{R_b} = 31 \times 10^{-6}$$

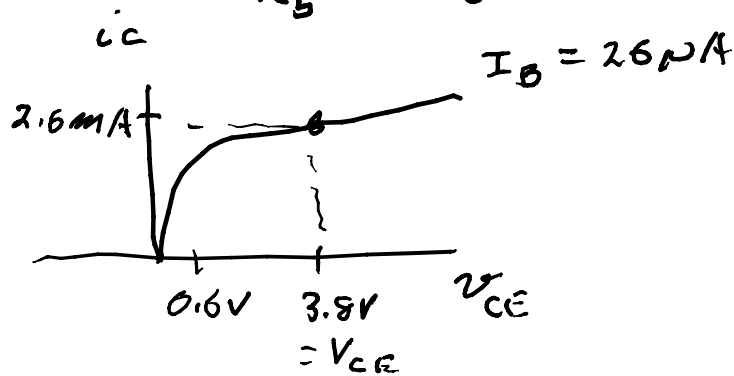or $R_b = \frac{3.3}{3.1} \times 10^5 \Omega$



Choose R_c such that


$$A_v |_{ideal} = -g_m R_c \Rightarrow R_c = \frac{100}{g_m} = 1000 = 1k$$

and $I_c = 2.6mA$, $V_{R_c} = R_c I_c = 2.6 \times 10^{-3} \times 10^3 = 2.6V$

KVL:

$$V_{CE} = V_{CC} - V_{R_c} - V_{R_E} \approx 9 - 2 \times 2.6 = 9 - 5.2 = 3.8V$$

Now use it as an amplifier, AC couple

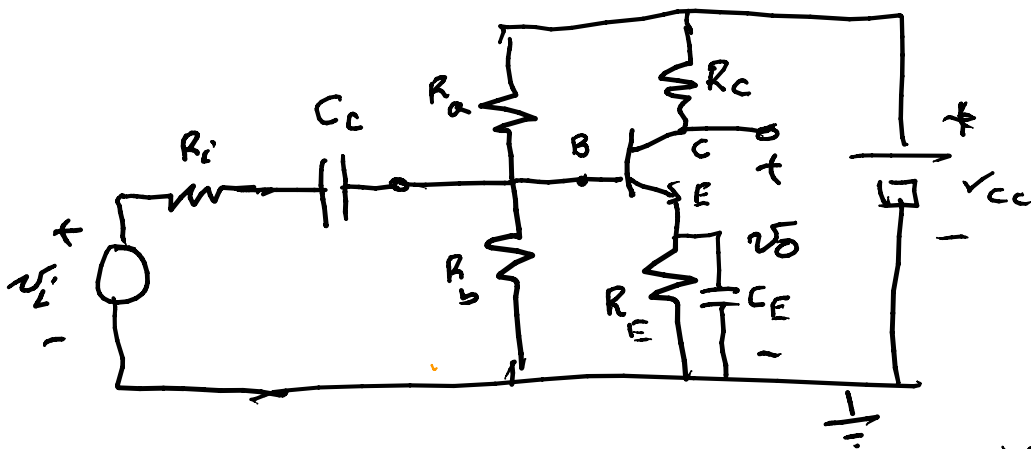

C_c & C_E
large

$$i = C \frac{dv}{dt}$$


if $v = v e^{at}$

$$i = C a v e^{at}$$


if $a = j\omega$

for small signals, use

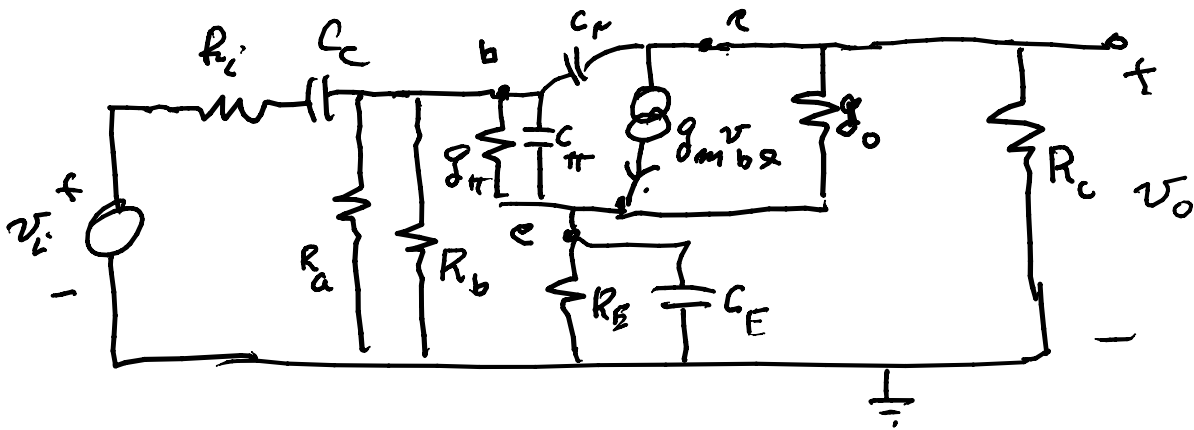small signal equivalent circuit for the transistor



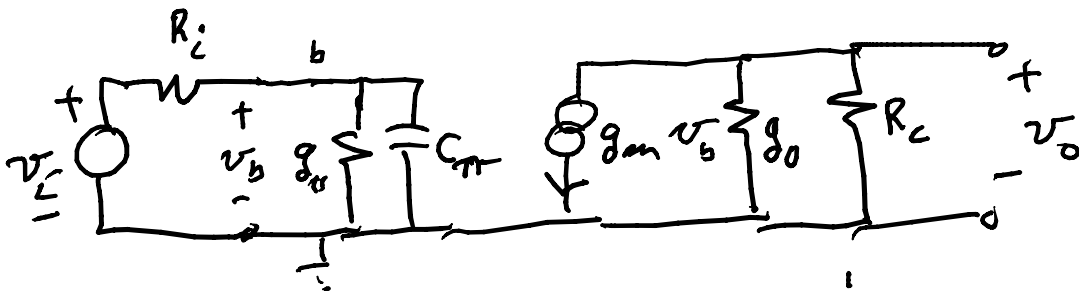approximate by ($C_E = C_C = C_P = 0$, $R_a = R_b = \infty$, R_E bypassed $= 0$)




$$A_i = \frac{v_o}{v_i}; \quad v_b = v_i \cdot \frac{\frac{1}{g_{\pi} + sC_{\pi}}}{R_i + \frac{1}{g_{\pi} + sC_{\pi}}} = \frac{1}{(1 + R_i g_{\pi}) + s R_i C_{\pi}} \cdot v_i$$

$$v_o = -g_m v_b \left(\frac{R_o R_C}{R_o + R_C} \right) = \frac{-g_m \left(\frac{R_o R_C}{R_o + R_C} \right)}{(1 + R_i g_{\pi}) + s R_i C_{\pi}} \cdot v_i$$

$$A_v = \frac{-g_m \left(\frac{R_o R_C}{R_o + R_C} \right)}{(1 + R_i g_{\pi}) + s R_i C_{\pi}}; \quad A_v(j\omega) = \frac{-g_m \left(\frac{R_o R_C}{R_o + R_C} \right)}{(1 + R_i g_{\pi}) + j\omega R_i C_{\pi}}$$
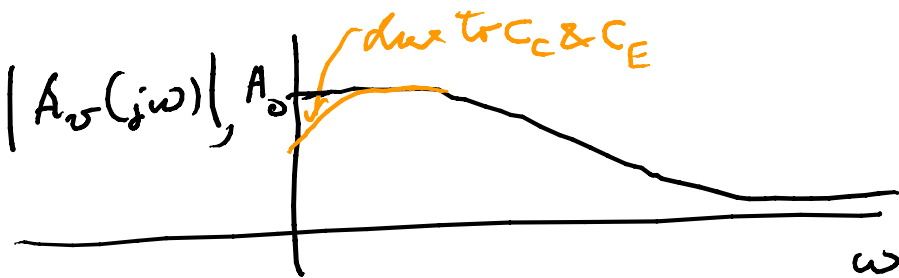
$$= \frac{-A_o}{1 + j\omega \frac{R_i C_{\pi}}{1 + R_i g_{\pi}}}$$



gives a low-pass characteristic also

$$[(1 + R_i g_{\pi}) + s R_i C_{\pi}] v_o = -g_m \left(\frac{R_o R_C}{R_o + R_C} \right) \cdot v_i$$

which is the differential equation

$$R_i C_{\pi} \frac{dv_o}{dt} + (1 + R_i g_{\pi}) v_o(t) = -g_m \left(\frac{R_o R_c}{R_o + R_c} \right) v_i(t)$$