

$$R_i C_{\pi} \frac{dv_o}{dt} + (1 + R_i g_{\pi}) v_o(t) = -g_m \left(\frac{V_o R_c}{V_o + R_c} \right) v_i(t)$$

If $v_i(t) = v_i e^{at}$ then $v_o(t) = V_o e^{at}$ results if

$$R_i C_{\pi} a V_o e^{at} + (1 + R_i g_{\pi}) V_o e^{at} = -g_m \left(\frac{V_o R_c}{V_o + R_c} \right) v_i e^{at}$$

as $e^{at} \neq 0$ for all $t \Rightarrow$ can cancel


$$\frac{V_o}{v_i} = \frac{-g_m (V_o R_c / (V_o + R_c))}{R_i C_{\pi} a + (1 + R_i g_{\pi})}$$

this is a function of complex variable

has a pole at

$$A = - \frac{(1 + R_i g_{\pi})}{R_i C_{\pi}}$$

$$s = \sigma + j\omega$$

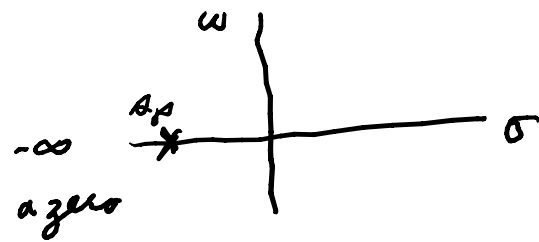

For more physical circuits look at

$$v_o(t) = V_o e^{at} 1(t)$$

$$1(t) = \text{unit step} = \begin{cases} 0 & \text{for } t < 0 \\ 1 & \text{for } t > 0 \end{cases}$$

$$\delta(t) = k 1(t)/at$$

on the left

$$R_i C_{\pi} V_o a e^{at} 1(t) + R_i C_{\pi} V_o e^{at} \underbrace{\delta(t)}_{\delta(t)} + (1 + R_i g_{\pi}) V_o e^{at} 1(t) = -g_m \left(\frac{V_o R_c}{V_o + R_c} \right) v_i(t)$$


cancel by choosing $a = A_p = -(1 + R_i g_{\pi}) / (R_i C_{\pi})$

$$R_i C_{\pi} V_o \delta(t) = -g_m \frac{V_o R_c}{V_o + R_c} v_i(t) \Rightarrow v_i(t) = \frac{\delta(t) \cdot R_i C_{\pi} V_o}{-g_m \left(\frac{V_o R_c}{V_o + R_c} \right)}$$

\Rightarrow implies $V_o e^{-\frac{(1 + R_i g_{\pi})}{R_i C_{\pi}} t} 1(t)$ is the


impulse response if $V_o = -g_m \left(\frac{V_o R_c}{V_o + R_c} \right) / (R_i C_{\pi})$

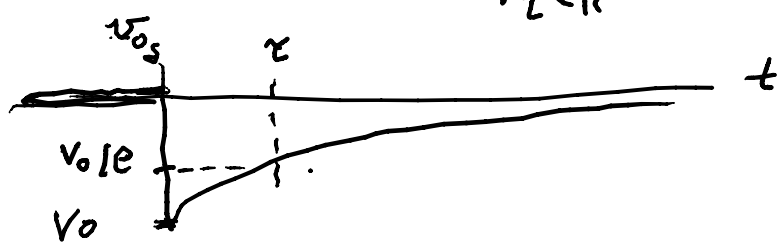∴ the impulse response is $v_{o5}(t) = -g_m \frac{(r_o R_c / (r_o + R_c))}{R_i C_{\pi}} e^{-\frac{(1 + R_i g_m)}{R_i C_{\pi}} t} \mathbb{1}(t)$




$$\tau = \frac{R_i C_{\pi}}{1 + R_i g_m} = \text{time constant}$$

Next topic: differential pairs

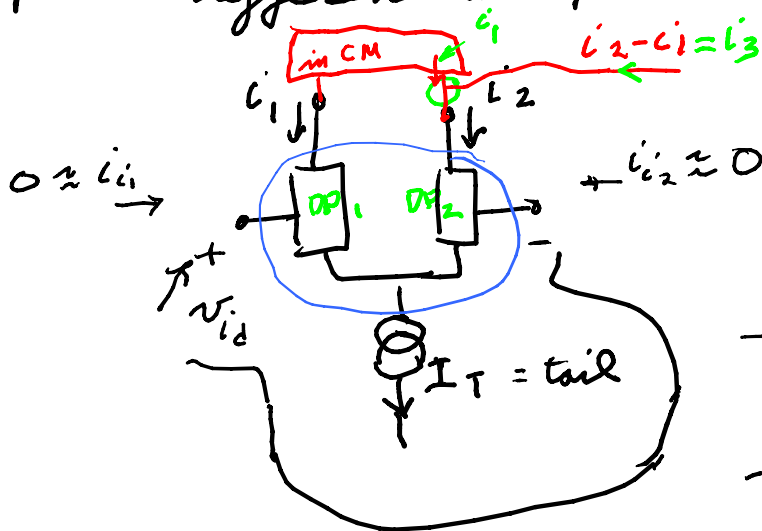

KCL: $0 = i_1 - i_2 + i_3$


$$I_T = i_1 + i_2$$

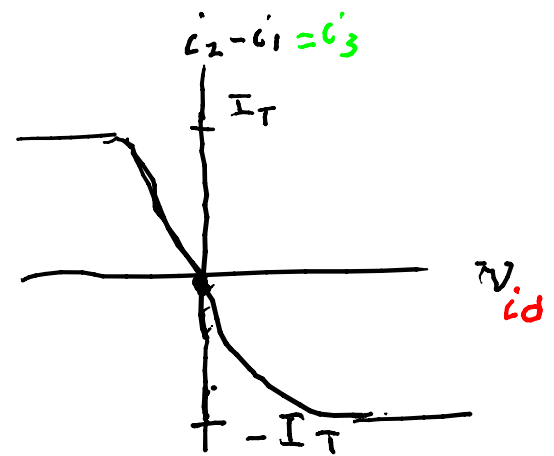

if DP's are BJT then

$$i_2 - i_1 = -I_T \tanh\left(\frac{v_{id}}{2V_T}\right)$$

To make

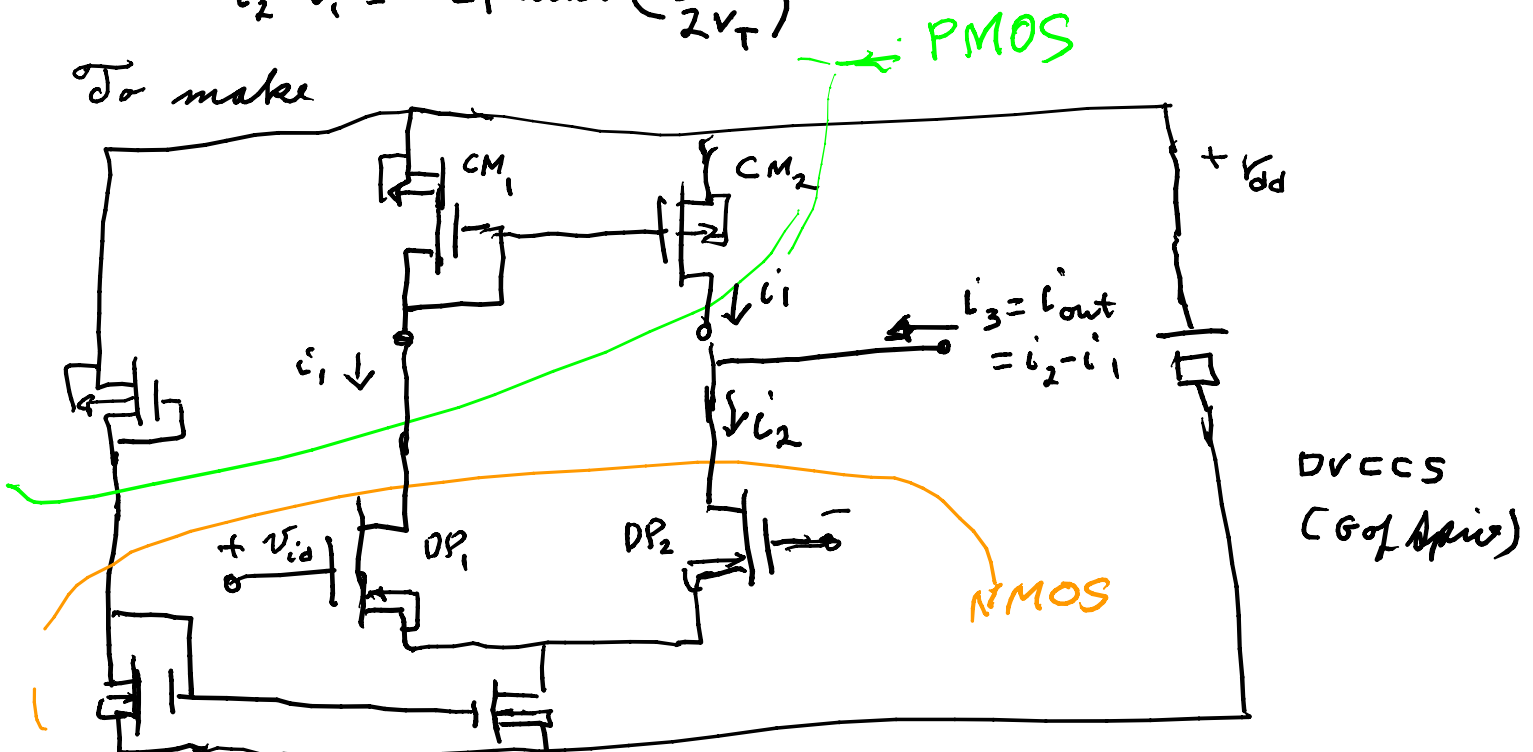

DVCCS
(G of Apis)

To put symmetric loads on DP_1 & DP_2

