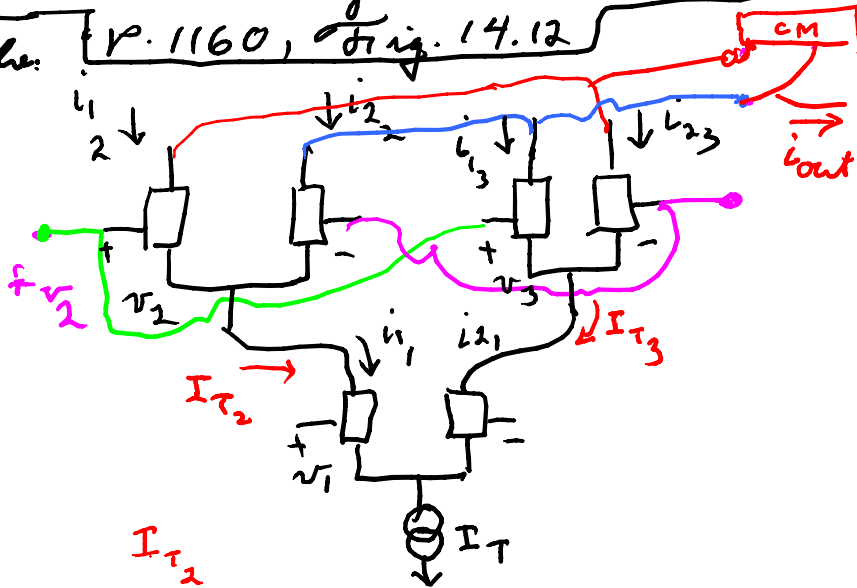


Transmission gate pulse response

multiple:

P. 1160, Fig. 14.12



any diff pair

$$i_1 = I_T f(v)$$

$$i_2 = (I_T - i_1) \text{ by KCL}$$

$$i_{1_2} = i_1 f(v_2), \quad i_{2_2} = i_1 - i_{1_2} = I_T f(v_1) - I_T f(v_1) f(v_2) \\ = I_T f(v_1) f(v_2) \quad = I_T f(v_1) (1 - f(v_2))$$

$$i_{1_3} = i_{2_1} f(v_3), \quad i_{2_3} = i_{2_1} - i_{1_3} = i_{2_1} - i_{2_1} f(v_3) \\ = (I_T - i_{1_1}) f(v_3) \quad = i_{2_1} (1 - f(v_3)) \\ = I_T (1 - f(v_1)) f(v_3) \quad = I_T (1 - f(v_1)) (1 - f(v_3))$$

$$(i_{1_2} - i_{2_2}) - (i_{1_3} - i_{2_3}) = \underbrace{(i_{1_2} + i_{2_3})}_{\text{normal } i_{out_2}} - \underbrace{(i_{2_2} + i_{1_3})}_{i_{out_3}}$$

$$i_{1_2} + i_{2_3} = I_T f(v_1) f(v_2) + I_T (1 - f(v_1)) (1 - f(v_3))$$

$$i_{2_2} + i_{1_3} = I_T f(v_1) (1 - f(v_2)) + I_T (1 - f(v_1)) f(v_3)$$

$$\text{difference} = I_T \{ f(v_1) f(v_2) + 1 - f(v_1) - f(v_2) + f(v_1) f(v_3) \}$$

$$- [f(v_1) - f(v_1) f(v_2) + f(v_3) - f(v_1) f(v_3)] \}$$

Set $v_3 = v_2$

$$I_{out} = (i_{1,2} + i_{2,3}) - (i_{2,2} + i_{1,3}) = I_2 [2f(v_1) - 1] [2f(v_2) - 1]$$


but $i_1 = \frac{I_T}{1 + e^{-v/V_T}} \Rightarrow f(v) = \frac{1}{1 + e^{-v/V_T}} = 2f(v) - 1 = \tanh\left(\frac{v}{2V_T}\right)$

$$i_0 = I_T \tanh\left(\frac{v_1}{2V_T}\right) \cdot \tanh\left(\frac{v_2}{2V_T}\right) \approx I_T \cdot \frac{v_1}{2V_T} \cdot \frac{v_2}{2V_T} \text{ for small } v_1, v_2$$

\therefore this connection gives a multiplies (analog) for small signals = Gilbert multiplies

($f(v) = \tanh v/2V_T$ for BJT)

here assume in saturation for MOS

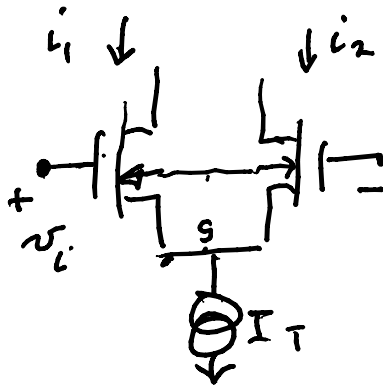

$$i_0 = k (v_{GS} - V_{th})^2$$

$$i_1 = k (v_+ - v_s - V_{th})^2 \quad \text{--- 1)}$$

$$i_2 = k (v_- - v_s - V_{th})^2 \quad \text{2)}$$

$$i_1 + i_2 = I_T \quad \text{3)}$$

and from 1) & 2)

$$v_+ - v_s - V_{th} = \sqrt{i_1/k}$$

$$v_- - v_s - V_{th} = \sqrt{i_2/k}$$

$$v_{id} = v_i = v_+ - v_- = \sqrt{i_1/k} - \sqrt{i_2/k}$$

square $v_i^2 = \frac{i_1}{k} + \frac{i_2}{k} - \frac{2}{k} \sqrt{i_1 i_2}$

$$\Rightarrow -\sqrt{i_1 i_2} = \frac{k}{2} v_i^2 - \frac{(i_1 + i_2)}{2} = \frac{k}{2} v_i^2 - \frac{I_T}{2}$$

$$i_1 i_2 = \left(\frac{k}{2} v_i^2 - \frac{I_T}{2} \right)^2$$

$$i_2 = I_T - i_1 \Rightarrow i_1 I_T - i_1^2 = \left(\frac{k}{2} v_i^2 - \frac{I_T}{2} \right)^2$$

$$i_1^2 - I_T i_1 + \left(\frac{k}{2} v_i^2 - \frac{I_T}{2} \right)^2 = 0$$

$$i_1 = \frac{I_T}{2} \pm \frac{1}{2} \sqrt{I_T^2 - 4 \left(\frac{k}{2} v_i^2 - \frac{I_T}{2} \right)^2} = \frac{1}{2} \left\{ I_T \pm \sqrt{4 \cdot \frac{k}{2} v_i^2 \cdot \frac{I_T}{2} - k^2 v_i^4} \right\}$$