

$$i_1 = \frac{1}{2} \left\{ I_T \pm \sqrt{2k v_i^2 I_T - k^2 v_i^4} \right\} = \frac{I_T}{2} \left\{ 1 \pm \sqrt{\frac{2k}{I_T} v_i} \sqrt{1 - \frac{1}{4} \left(\frac{\sqrt{2k} v_i}{I_T} \right)^2} \right\}$$

$$i_2 = I_T - i_1 ; \quad i_0 = i_1 - i_2 = 2i_1 - I_T \quad ; \quad \text{as } i_1 \uparrow \text{ if } v_i \uparrow \text{ more + in } i_1$$


$$= I_T \sqrt{\frac{2k}{I_T} v_i} \sqrt{1 - \frac{1}{4} \left(\frac{\sqrt{2k} v_i}{I_T} \right)^2}$$

Body effect

p. 324, Eq. (5.107)

$$V_{th} = V_{TO} + \text{GAMMA} (\sqrt{\text{PHI} + V_{SB}} - \sqrt{\text{PHI}})$$
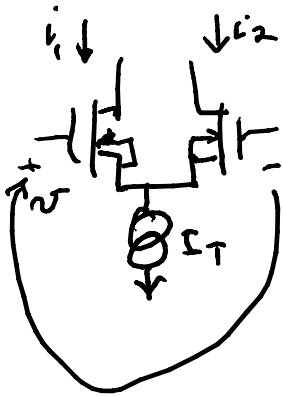
$$\text{PHI} = 2\phi_s, \quad \text{GAMMA} = \delta$$



$$i_0 = i_1 - i_2 = i_1 - (I_T - i_1) = 2i_1 - I_T$$

$$i_1 + i_2 = I_T \quad i_0 = I_T \sqrt{\frac{2k}{I_T} v} \sqrt{1 - \frac{1}{4} \left(\frac{\sqrt{2k} v}{I_T} \right)^2}$$

$$R = \frac{k_p \cdot W}{2 \cdot L}$$

$$i_0(x) = I_T x \sqrt{1 - \frac{1}{4} x^2}$$

$$x = \sqrt{\frac{2k}{I_T} v}$$



$$\frac{di_0}{dx} = I_T \left\{ \sqrt{1 - \frac{1}{4} x^2} + x \frac{1}{\sqrt{1 - \frac{1}{4} x^2}} \cdot \frac{1}{2} \left(-\frac{1}{4} 2x \right) \right\}$$


$$= 0 = I_T \left\{ \frac{1 - \frac{1}{4} x^2 - \frac{1}{4} x^2}{\sqrt{1 - \frac{1}{4} x^2}} \right\} \Rightarrow 0 = 1 - \frac{1}{2} x^2$$

$$i_{0, \text{max}} \text{ is at } x = \pm \sqrt{2}, \quad x_{\text{min}} = x_{\text{max}} \Rightarrow i_0 = I_T \sqrt{2} \cdot \sqrt{1 - \frac{1}{4} (\sqrt{2})^2} = I_T \frac{\sqrt{2}}{\sqrt{2}} = I_T$$

$$i_0 = i_1 - i_2$$


$$i_0 = I_T \begin{cases} \frac{\sqrt{2k}}{I_T} v \sqrt{1 - \frac{1}{4} \left(\frac{\sqrt{2k}}{I_T} v \right)^2} \\ 1 \\ -1 \end{cases} \quad \text{if } \sqrt{\frac{I_T}{k}} < v$$
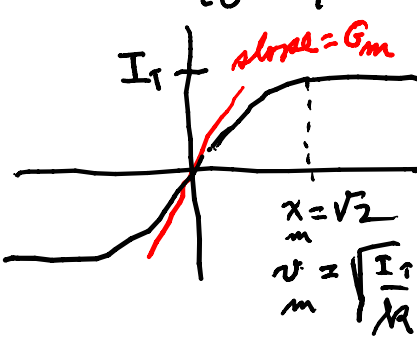
$$-\sqrt{\frac{I_T}{k}} < v < \sqrt{\frac{I_T}{k}}$$



$$x = \sqrt{\frac{2k}{I_T} v}$$


$$\left. \frac{di_0}{dv} \right|_{v=0} = G_m \Big|_{v=0} = \frac{I_T \left(1 - \frac{x^2}{2} \right)}{\sqrt{1 - \frac{1}{4} x^2}} \cdot \sqrt{\frac{2k}{I_T}} \Big|_{x=0} = \sqrt{2k I_T}$$

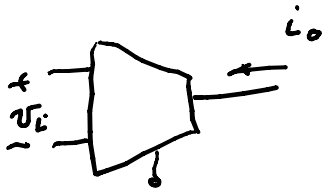




OTA = operational transconductance amplifier

DVCCS

$$\frac{d i_o}{d v_i} \approx G_m$$

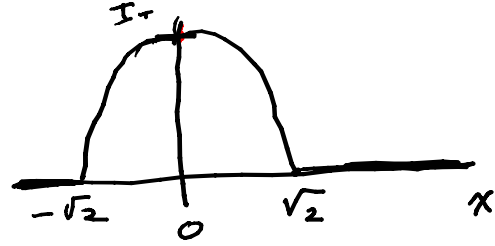


Transmission Gate = pass transistor

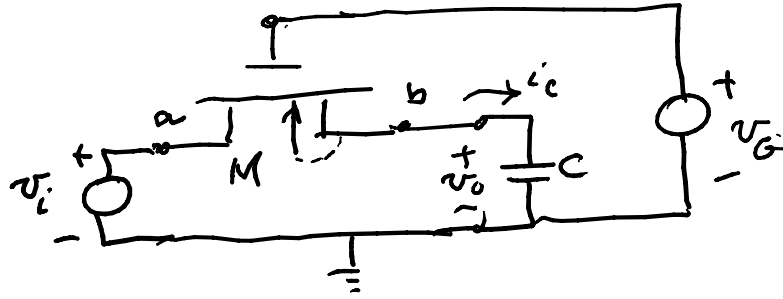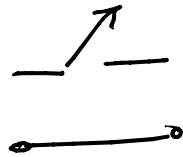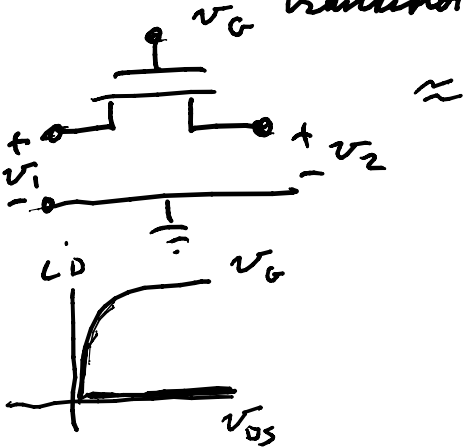

$$a = S \text{ if } v_i < v_0$$

$$a = D \text{ if } v_i > v_0$$

if $v_0 = 0 @ t = 0$ & v_i is a step 

and $v_0 = \max > 0$; $v_0 = v_i$

$\Rightarrow a = \text{Drain}$ & $b = \text{Source}$

$$i_c = C \frac{d v_0}{d t} = I_D = \frac{K P W}{2 L} (v_{GS} - V_{th})^2$$

as M is in saturation $v_{GS} = v_i - v_0$

$$v_{DS} = v_i - v_0$$

$$v_{DS} > v_{GS} - V_{th}$$

$$C \frac{d v_0}{d t} = K (v_i - v_0 - V_{th})^2; \quad K = \frac{K P W}{2 L}$$

(assume $V_{th} = \text{const.} = V_{T0}$)

$$= \frac{C d(v_i - V_{th} - v_0)}{d t} = -C \frac{d v_0}{d t} = C \frac{d x}{d t}$$

$$= -K x^2$$

$$\left[\frac{d x}{d t} = -\frac{K}{C} x^2 \right] \text{ Riccati eq.}$$

$$x = v_i - V_{th} - v_0$$

$$\frac{d x}{d t} = -\frac{d v_0}{d t}$$

$$x(0) = v_i - V_{T0}$$

$$\frac{dx}{x^2} = -\frac{k}{c} dt$$

$$\int_{x(0)}^{x(t)} \frac{dx}{x^2} = \int_0^t -\frac{k}{c} dt$$

$$= -\frac{1}{x} \Big|_{x(0)}^{x(t)} = -\frac{k}{c} t \Big|_0^t = -\frac{k}{c} t$$

$$= -\frac{1}{x(t)} + \frac{1}{x(0)} = -\frac{k}{c} t$$

$$\frac{1}{x} = \frac{k}{c} t + \frac{1}{x(0)} \Rightarrow x = \frac{1}{\frac{k}{c} t + \frac{1}{x(0)}}$$

$$x(t) = v_i - v_{oh} - v_o = \frac{1}{\frac{k}{c} t + \frac{1}{v_i - v_{to}}}$$

$$v_o(t) = v_i - v_{oh} - \frac{1}{\frac{k}{c} t + \frac{1}{v_i - v_{to}}}$$

note $v_o(0) = 0$ as desired

