

Exam questions, preliminary
 inverters MOS sizing
 compare BJT & MOS biasing; saturation, etc.
 MOS equivalent circuit
 $\frac{v_o}{v_i}(s)$ transfer function
 poles & zeroes

741 op amp, p. 1003, F. 12.13

ring oscillator, p. 1239, F. 15.28


floating gate, p. 1243, F. 15.31

Hysteresis, p. 1359, F. 17.20


Comparator to sense Δv_B


$v_o = V_+$ if $\Delta v_B > 0$ (a 1 in memory)

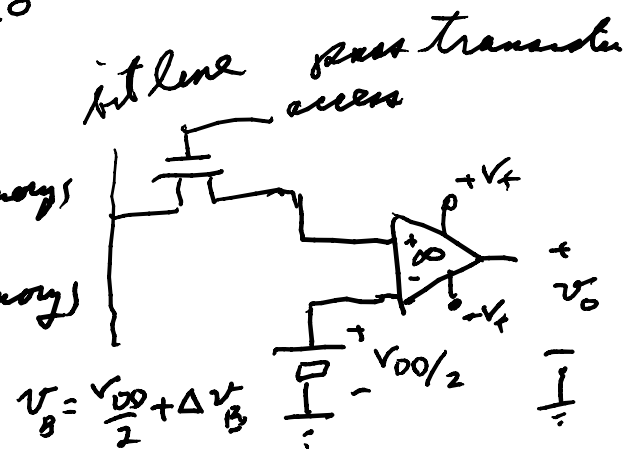$v_o = -V_+$ if $\Delta v_B < 0$ (a 0 in memory)




for the comparator use an op-amp

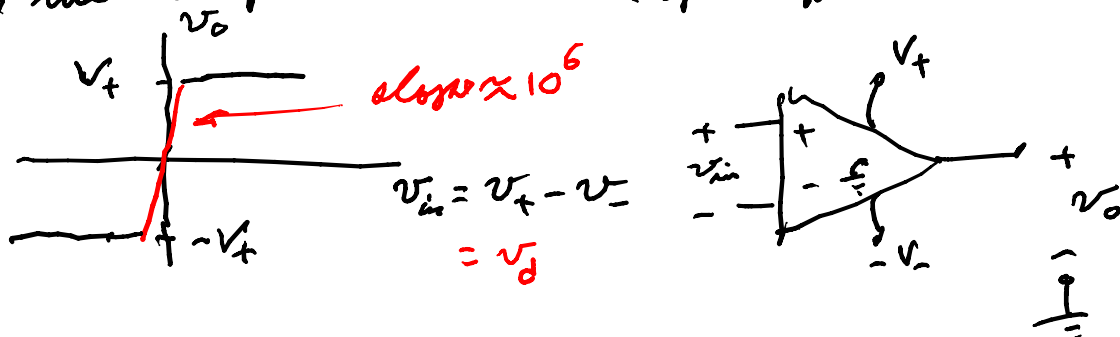

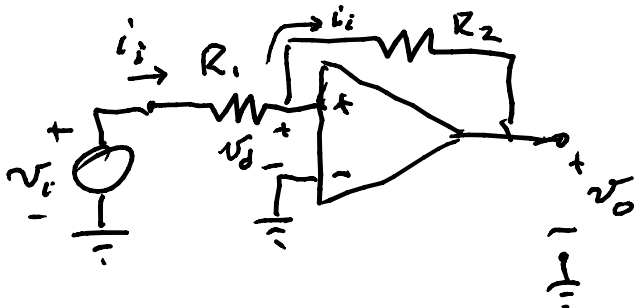

ideal op-amp linear mode

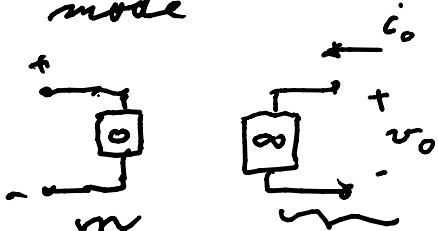

anullator
 $i_i = 0, v_i = 0$

norator
 $i_o = \text{arbitrary}$
 $v_o = \text{'' ''}$
 (independent of i_o)

$$(v_i - v_d) = R_1 \cdot i_i$$

$$(v_d - v_o) = R_2 \cdot i_i$$

if linear $v_d = 0$ by virtual ground at op-amp input


$$i_i = G_1 v_i, -v_o = R_2 G_1 v_i \Rightarrow \frac{v_o}{v_i} = -\frac{R_2}{R_1}$$

$G_1 = 1/R_1$

irrespective of input of op-amp at + or -

for an actual op-amp we get saturation actually get hysteresis


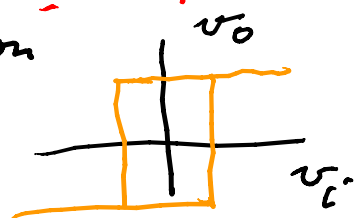
solve for v_o w $v_d = v_{in}$ with v_i as a parameter




$$G_1 (v_i - v_d) = G_2 (v_d - v_o) \Rightarrow G_2 v_o = (G_2 + G_1) v_d - G_1 v_i$$

$$v_o = \left(1 + \frac{G_1}{G_2}\right) v_d - \frac{G_1}{G_2} v_i$$


load line eq.

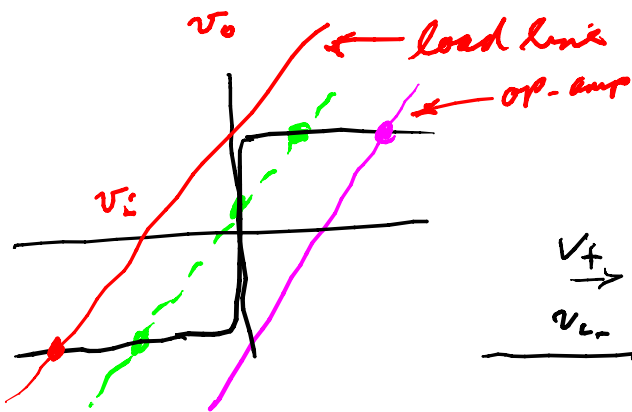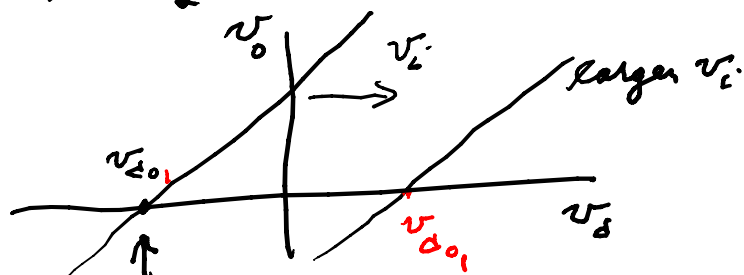
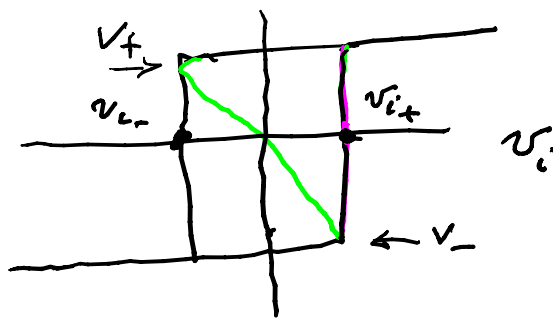
$$\left(1 + \frac{G_1}{G_2}\right) v_{d0} = + \frac{G_1}{G_2} v_i = \text{eq. for intersect of load line on } x = v_d \text{ axis}$$



to find v_{i+}

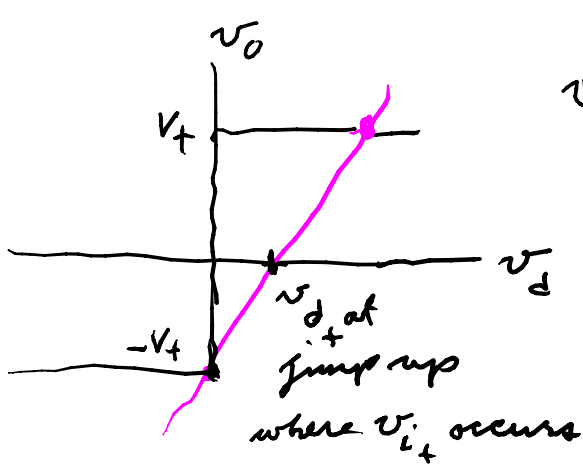


$$v_o = -v_t = \left(1 + \frac{G_1}{G_2}\right) v_{d+} - \frac{G_1}{G_2} v_{i+} \quad \text{load line}$$

$$-(-V_t) = \text{slope} = \frac{V_t}{1 + \frac{G_2}{G_1}} = \frac{dv_o}{dv_d} \Big|_{\text{load line}}$$

$$\Rightarrow v_{d+} = \frac{V_t}{\left(\frac{G_1/G_2}{1 + G_1/G_2}\right) v_{i+}} = \left(1 + \frac{G_1}{G_2}\right) v_{i+}$$
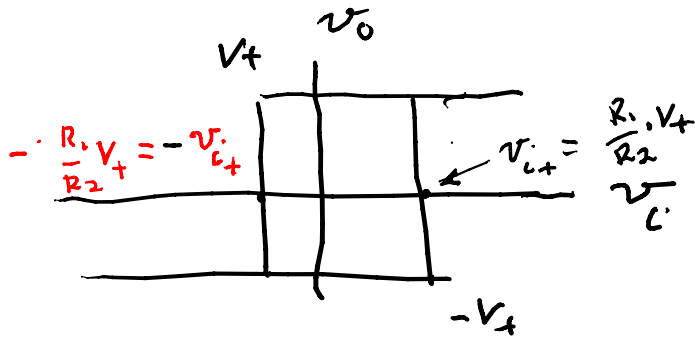
$$\Rightarrow v_{i+} = \frac{G_2}{G_1} v_t$$




text gives

$$v_{i+} = V_t \times \left(\frac{R_1}{R_2}\right)$$

(Eq. (17.30)) p. 1359

back to pass transistors

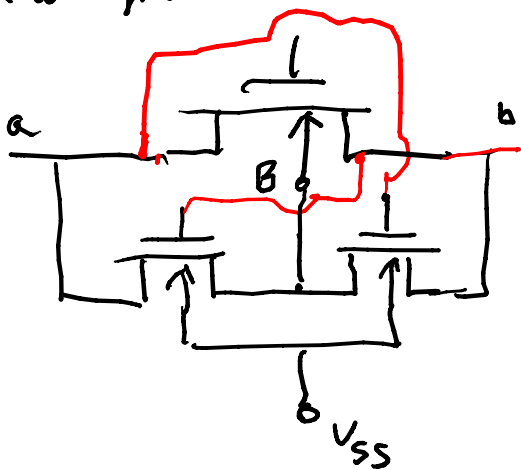

ties B to a if a = S
to b if b = S