
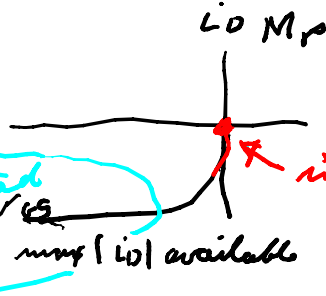
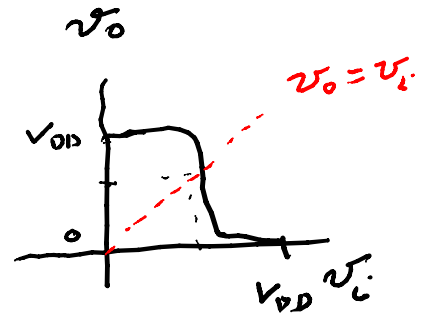


CMOS inverter

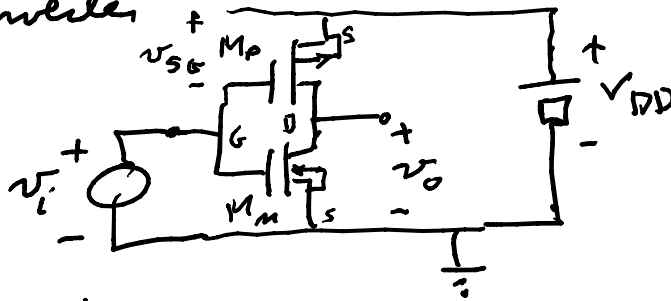

$$v_{DS} = v_o \text{ when } v_i = 0$$

implies M_p is in Ohmic = (triode) region
& M_n is cut-off

$$v_{SG} = V_{DD} \text{ when } M_n \text{ channel has } v_{GS} = 0 = v_i$$

But if $v_o = v_i$ then $v_{DS_n} = v_{GS_n} > v_{GS_n} - V_{TO_n}$ if $V_{TO} > 0$
enhancement mode MOS
 $\Rightarrow M_n$ is saturated

$$\text{then } M_p \quad v_{SG_p} = V_{DD} - v_i, \quad v_{SD_p} = V_{DD} - v_o = V_{DD} - v_i$$

$$v_{SD_p} = v_{SG_p} \geq v_{SG_p} - (-V_{TO_p}) \text{ saturation}$$



\Rightarrow at $v_o = v_i$ both M_n & M_p are in saturation

$$\Rightarrow I_{D_n} = \frac{k_p}{2} \left(\frac{W}{L}\right)_m (v_i - V_{TO_m})^2 (1 + \lambda_n v_o)$$


$$= I_{S_p} = \frac{k_p}{2} \left(\frac{W}{L}\right)_p (V_{DD} - v_i - (-V_{TO_p}))^2 (1 + \lambda_n [V_{DD} - v_o])$$

usually know all but $(W/L)_p$ & as $\frac{k_p}{2} \mu < \frac{k_p}{2} \mu$
need $(W/L)_p > (W/L)_m$

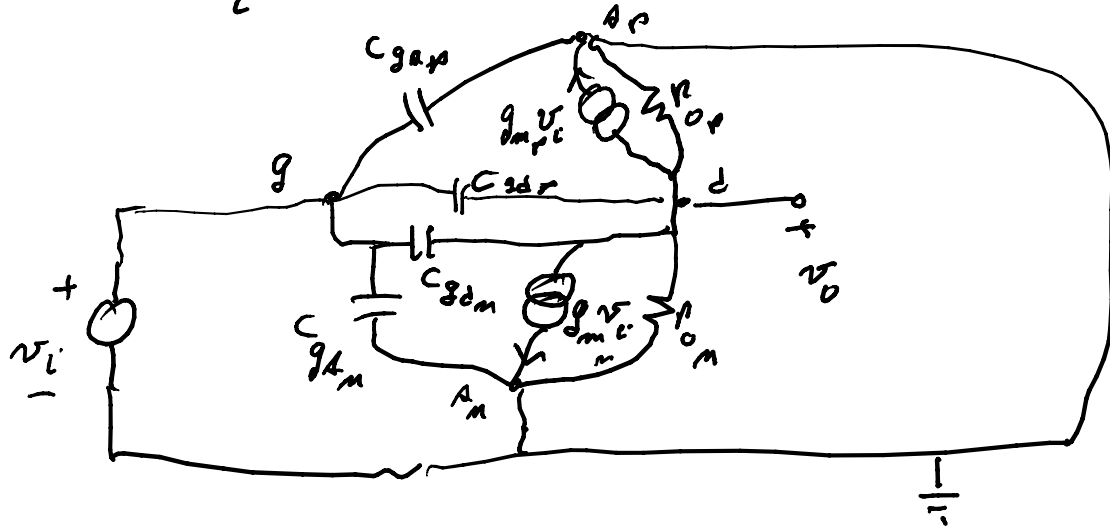
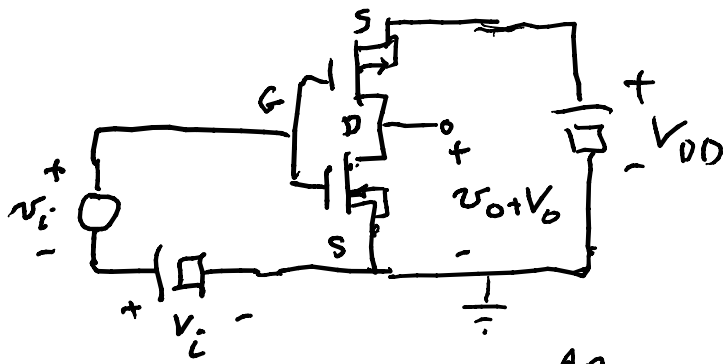
assume bias at $v_i = v_o = V_o$ & inject small signal




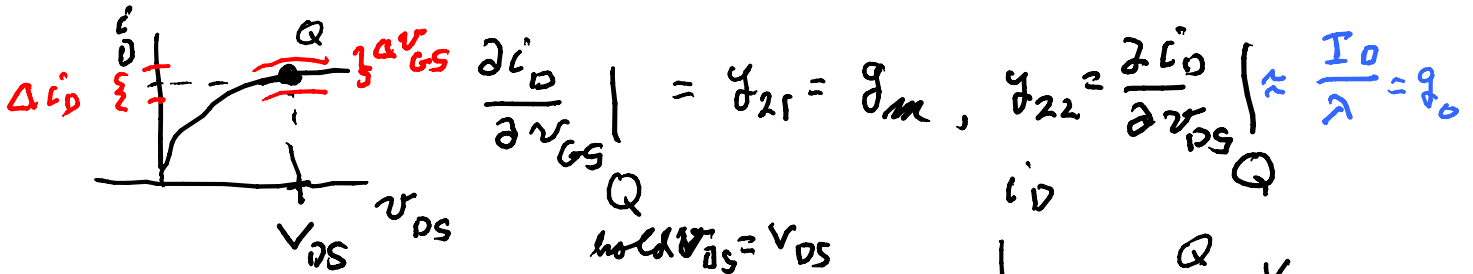
$$\begin{aligned}
 \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} &= Y \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 = v_{gs} \\ v_2 = v_{ds} \end{bmatrix} = \begin{bmatrix} i_g \\ i_d \end{bmatrix}
 \end{aligned}$$



hold $v_{GS} = v_{GS}$
 $v_{ds} = 0$


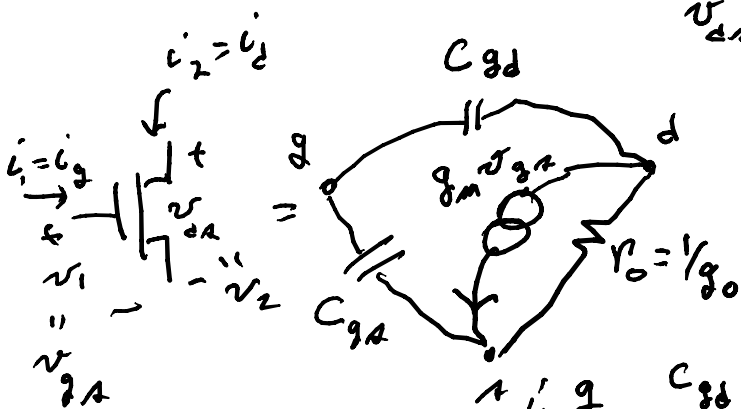
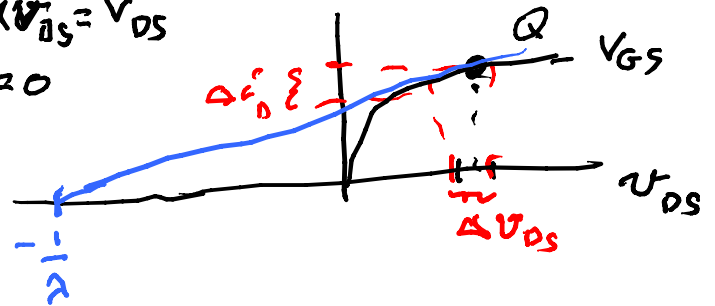

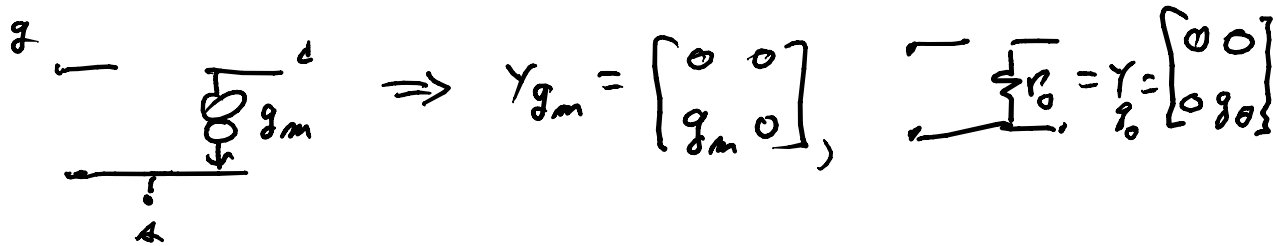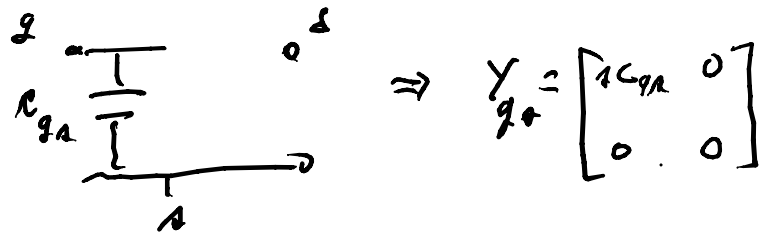
$$\Rightarrow Y \Rightarrow \Rightarrow Y_{gd} = \begin{bmatrix} sC_{gd} & -sC_{gd} \\ -sC_{gd} & sC_{gd} \end{bmatrix}, \quad i = Y v$$



$$Y = Y_{gd} + Y_{ga} + Y_{gm} + Y_{go} = \begin{bmatrix} 2C_{gd} + 2C_{ga} & -2C_{gd} \\ g_m - 2C_{gd} & g_o + 2C_{gd} \end{bmatrix}$$

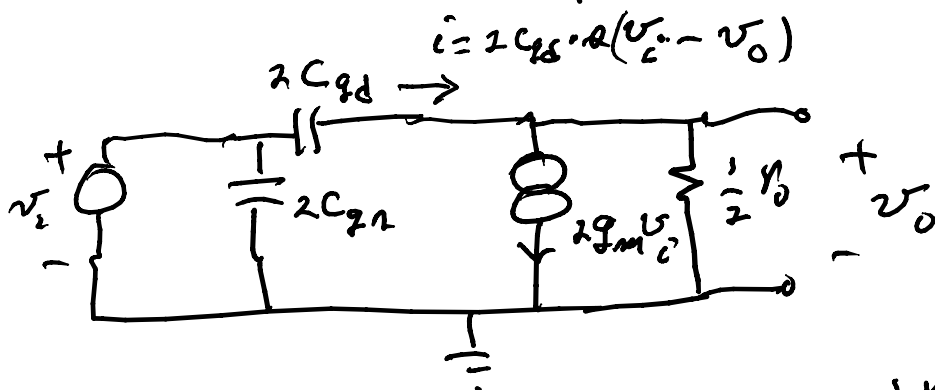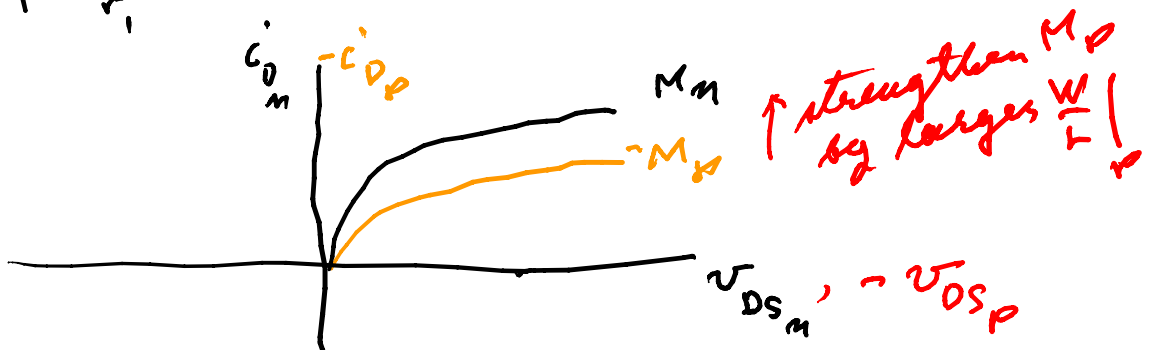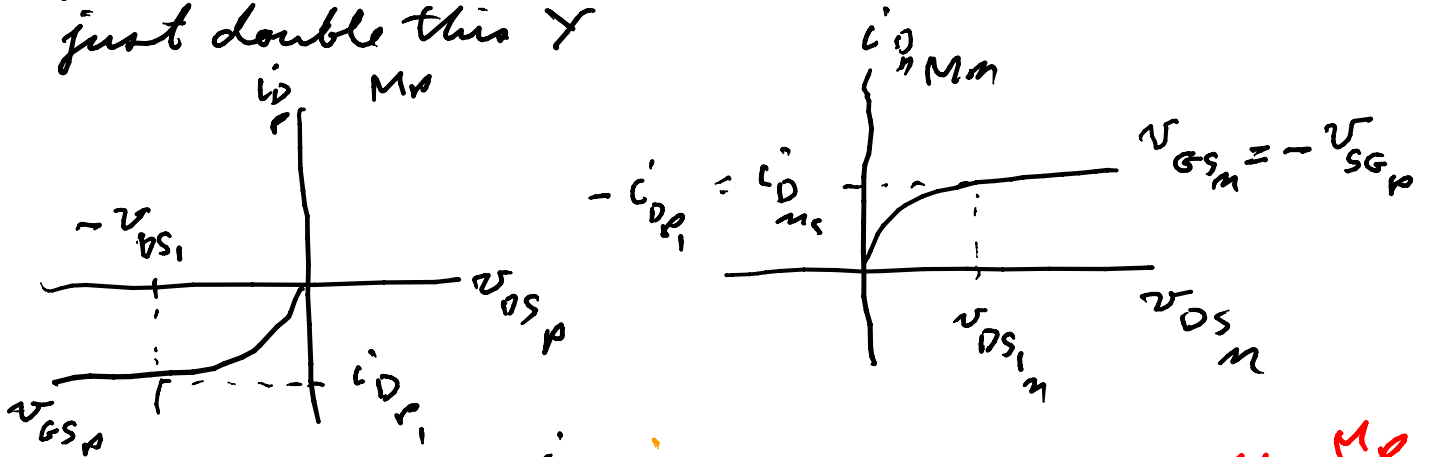if M_p is complement numerically then for the inverters just double this Y



to find v_0/v_i

$$v_0 = -2g_m \frac{1}{2} v_0 v_i + 2C_{gd} \cdot A (v_i - v_0) \frac{v_0}{2}$$

solve: $(1 + 2g_m \frac{1}{2} v_0 + 2C_{gd} \frac{v_0}{2} \cdot A) v_0 = (2C_{gd} \cdot A - 2g_m \frac{v_0}{2}) v_i$

$$\frac{v_o}{v_i} = \frac{2(C_{gd} \cdot s - g_m \frac{r_o}{2})}{2(C_{gd} \frac{r_o}{2} s + g_m \frac{r_o}{2} + \frac{1}{2})}$$

$$\text{pole @ } s = - \left(g_m \frac{r_o}{2} + \frac{1}{2} \right) / C_{gd} \frac{r_o}{2}$$

$$\text{zero @ } s = (g_m r_o / 2) / C_{gd}$$