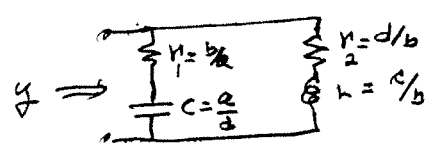


E/EE 610 Fall 2012 Final

#1, a) $2 \operatorname{Ev} y(s) = y(s) + y(-s) = \frac{as+b}{cs+d} + \frac{-as+b}{-cs+d} = \frac{(as+b)(-cs+d) + (-as+b)(cs+d)}{(cs+d)(-cs+d)}$
 $= \frac{(-aca^2 + bd + ada - bca) + (-aca^2 + bd - ada + bca)}{-c^2s^2 + d^2}$
 $= \frac{2(-aca^2 + bd)}{(d^2 - c^2s^2)} \Rightarrow \operatorname{Ev} y(s) = 0 @ -aca^2 + bd = 0$
 $\Rightarrow \text{zeros of Ev } y(s) @ s = \pm \sqrt{\frac{bd}{ac}}$ (which are real as $a, b, c, d > 0$)

b) $y(s) = \frac{as}{bs+d} + \frac{b}{cs+d} = \frac{1}{\frac{b}{a} + \frac{1}{d}s} + \frac{1}{\frac{c}{b}s + \frac{d}{b}}$



as all of R_1, R_2, C, L are > 0 this is a passive circuit which requires $y(s)$ to be PR


$\therefore y(s)$ is PR for all positive a, b, c, d .

Other means of checking: poles are in $\sigma < 0 \Rightarrow$ analytic in $\sigma > 0$
 and $G(j\omega) = \operatorname{Ev} y(j\omega) = \frac{ac\omega^2 + bd}{(d^2 + c^2\omega^2)} > 0 \forall \omega$

c) For $y(s)$ to be RC, PR, poles and zeros on $-\sigma$ axis (true for all $a, b, c, d > 0$) and alternate with highest a pole & lowest a zero. Write $y(s) = \frac{a}{c} \left(\frac{s + b/a}{s + d/c} \right)$, so need $d/c \geq b/a$ [the RC condition].

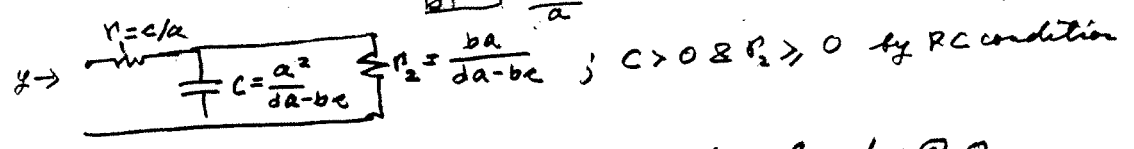
d) 1st case: remove poles of $y(s) @ \infty$ and constants of $z @ \infty$
 as no pole at ∞ , start with $z = \frac{(cs+d)(cs+d)}{(as+b)(as+b)}$

$\frac{cs+d}{as+b} \cdot \frac{cs+d}{as+b} = \frac{c/a}{cs+d} \cdot \frac{a^2}{(as+b)^2} = \frac{c/a}{cs+d} \cdot \frac{a^2}{(a^2 + 2ab/s + b^2/s^2)}$
 $\Rightarrow y(s) = \frac{1}{\frac{c}{a} + \frac{1}{\frac{a^2}{da-bc} s + \frac{ba}{da-bc}}}$



2nd case: remove constants of $y @ 0$ and poles of $z @ 0$

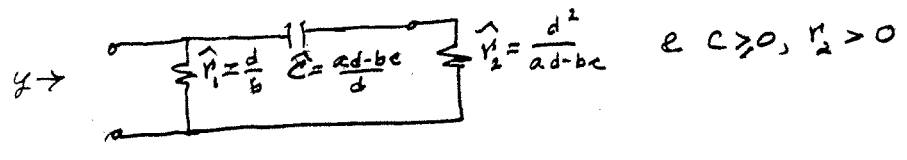$\frac{d+cs}{b+cs} \cdot \frac{b+cs}{b+cs} = \frac{b/d}{b+cs} \cdot \frac{d}{ad-bc} \cdot \frac{1}{s} = \frac{b/d}{b+cs} \cdot \frac{d}{ad-bc} \cdot \frac{1}{s}$
 $\Rightarrow y(s) = \frac{b}{d} + \frac{1}{\frac{d}{ad-bc} s + \frac{1}{ad-bc}}$




#2. The 2-port $Y(s) = \begin{bmatrix} Cs+G & -Cs-G-g \\ -Cs-G+g & Cs+G \end{bmatrix}$ & $Y = Y_{11} - \frac{Y_{12} Y_{21}}{Y_{22} + Y_L}$



$G = 1/R$

$$= \frac{\Delta Y + Y_{11} Y_L}{Y_{22} + Y_L} = \frac{g^2 + (Cs+G)Y_L}{(Cs+G) + Y_L}$$

a) $\Rightarrow Y Y_L + Y(Cs+G) = g^2 + (Cs+G)Y_L$

$$Y_L = \frac{g^2 - (Cs + \frac{1}{R})Y}{Y - (Cs + \frac{1}{R})}$$

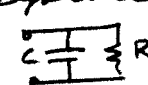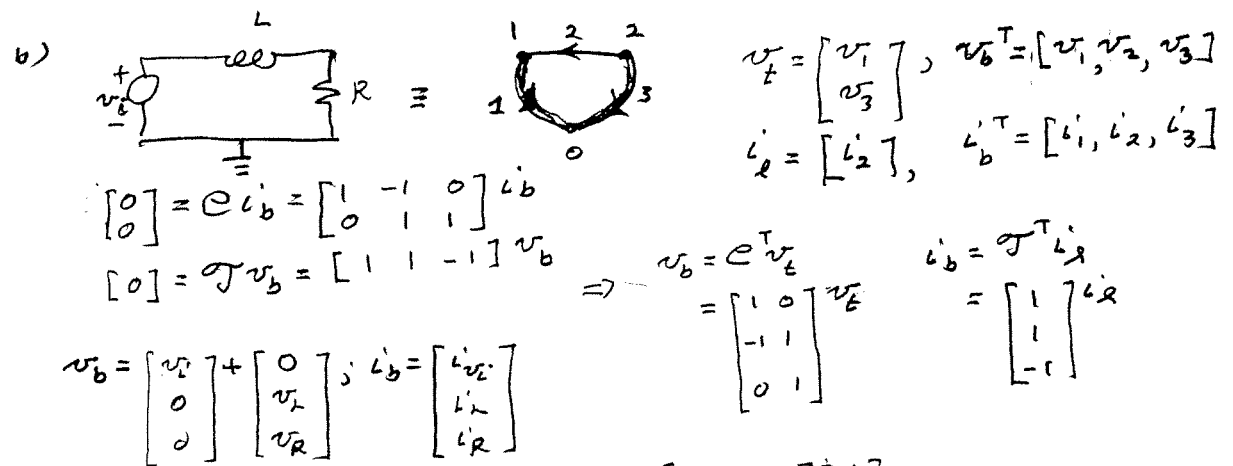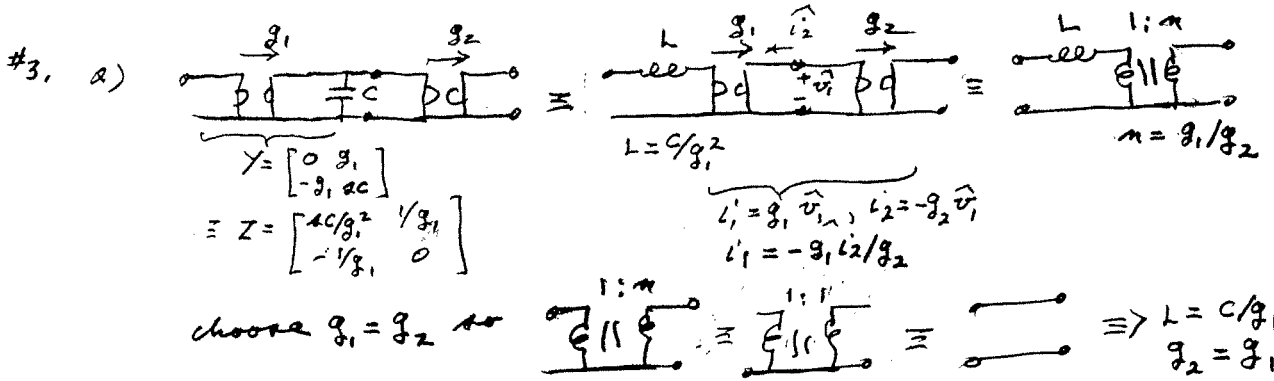b) as $Cs + \frac{1}{R} = C(s+a)$ has the same a for all C 's we can set $s+a = p \Rightarrow s = p-a$ and synthesize $\hat{Y}(p) = Y(p-a)$ (which is assumed PR) and then replace each Cp in the circuit by $Cp = C(a+a) \Rightarrow$ 



$$\begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}_b = \begin{bmatrix} v_1 = u \\ 0 \\ 0 \end{bmatrix} + \begin{bmatrix} 0 \\ v_L = \Delta L i_L = \Delta L i_2 \\ v_R = R i_R = R i_3 \end{bmatrix} = \begin{bmatrix} u \\ 0 \\ 0 \end{bmatrix} + \begin{bmatrix} 0 & 0 & 0 \\ 0 & \Delta L & 0 \\ 0 & 0 & R \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & 0 \\ -1 & 1 \\ 0 & 1 \end{bmatrix} v_L = \begin{bmatrix} u \\ 0 \\ 0 \end{bmatrix} + \begin{bmatrix} 0 & 0 & 0 \\ 0 & \Delta L & 0 \\ 0 & 0 & R \end{bmatrix} \begin{bmatrix} 1 \\ 1 \\ -1 \end{bmatrix} i_L = \begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix} u + \begin{bmatrix} 0 \\ \Delta L \\ R \end{bmatrix} i_L$$

$$\Rightarrow \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = - \begin{bmatrix} 1 & 0 \\ -1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} v_L \\ i_L \end{bmatrix} + \begin{bmatrix} 0 & 0 & 0 \\ 0 & \Delta L & 0 \\ 0 & 0 & -R \end{bmatrix} \begin{bmatrix} v_L \\ i_L \end{bmatrix} + \begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix} u$$

$$\Rightarrow \begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & -L \\ 0 & 0 & 0 \end{bmatrix} \frac{dx}{dt} = \begin{bmatrix} -1 & 0 & 0 \\ 1 & -1 & 0 \\ 0 & -1 & -R \end{bmatrix} x + \begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix} u, y = v_o = v_3 = [0 \ 1 \ 0] \begin{bmatrix} v_1 \\ v_3 \\ i_2 \end{bmatrix}$$

$$y = [0 \ 1 \ 0] x$$

Here $x_1 = u, x_2 = -R x_3, -L \dot{x}_3 = x_1 - x_2 = u + R x_3 \Rightarrow x_3 = \frac{-u}{R + L s}$

$$y = v_o = x_2 = \frac{R}{R + L s} \cdot u$$

$$\Rightarrow \frac{v_o}{v_L} = \frac{R}{R + L s}$$

(checked by voltage divider equation applied to circuit)