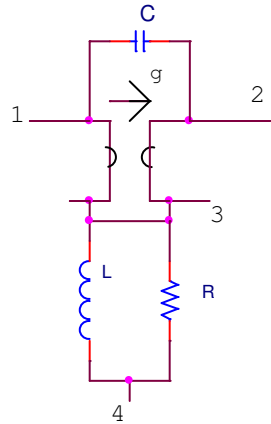


610 Fall 2012 – Homework 4

1. For the following circuit
  - a) Give the indefinite admittance matrix  $Y_{ind}(s)$ .
  - b) Ground node 4 and eliminate node 3 to give the 2-port  $Y(s)$ ; obtain  $Z(s)=Y(s)^{-1}$



2. For the result of Problem 1, evaluate the even part of  $Y(s)$  and the even part of  $Z(s)$ , compare, and discuss the even part zeros in terms of  $G=1/R$
3. Using the 2-port  $Y(s)$  of problem 1, set  $C=G=0$  and
  - a. Find the load impedance  $z_L(s)$  in terms of the input impedance  $z(s)$ .
  - b. Equate with the Richards function of the text and discuss the possibility for lossless synthesis.
4. The following 2-port circuit has the input port at nodes 1-5 and the output at nodes 2-5.
  - a. Give the transfer function  $T(s)=V_{2-5}(s)/V_{1-5}(s)$  when fed by a voltage source and having an open-circuit load.
  - b. Discuss why we know there is at least one real pole or zero.
  - c. Assume  $C4=C5=C$  and  $R1=R2=R$ , normalize  $L = R = C = gm = 1$ . Give the normalized  $T(s)$  and find the poles and zeros.
  - d. Give the unit step response and the impulse response of the normalized circuit.

