

610 Fall 2012 – Homework 6

1. Synthesize by the two Cauer and the two Foster forms the lossless admittances

$$y_1(s) = \frac{s(s^2 + 3)}{(s^2 + 1)(s^2 + 5)}$$

$$y_2(s) = \frac{(s^2 + 1)(s^2 + 5)}{s(s^2 + 3)}$$

2. Replace each L by an R in the above syntheses and give the resulting RC admittances. Compare degrees of different  $y(s)$ , including LC versus RC.

3. Set up the companion matrix form of state-variable equations for the admittance

$$y(s) = \frac{3s^2 + 2s + 1}{s^2 + 2}$$

and synthesize the resulting 3-port admittance matrix, loaded in two unit capacitors, and check by analyzing the circuit that  $y(s)$  results.

4. From Homework #5, problem 5, the following formulas hold for the lossless positive-real  $\tanh$  and  $\operatorname{coth} = \operatorname{coth}$ .

$$\tanh(s) = 2s \left[ \sum_{n=0}^{\infty} \frac{1}{(s^2 + (n + \frac{1}{2})^2 \pi^2)} \right]$$

$$\operatorname{coth}(s) = \frac{1}{s} + 2s \left[ \sum_{n=1}^{\infty} \frac{1}{(s^2 + (n\pi)^2)} \right]$$

Using these give second Foster and second Cauer type syntheses of  $y(s) = \operatorname{coth}(sl)$  [which represents a normalized shorted transmission line of length  $l$ ].

5. (conceptually challenging). Show that the following is positive-real and discuss the position and nature of its singularities (note that a limit of poles is an essential singularity and all real numbers are limits of rational numbers).

$$y(s) = \sum_{k=1}^{\infty} \sum_{m=1}^{\infty} \operatorname{coth}\left(s \frac{k}{m}\right)$$