

this has the same graph  
with  $v_1$  &  $v_2$  can be independent  
 $i_3, i_4, i_5 \quad " \quad "$

} the tree branch voltages  
can be "variables"  
& same for colless  
branch currents

write  $i_b$  = branch currents =  $\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = i_b$ ,  $v_b$  =  $\begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix} = \begin{bmatrix} v_t \\ -v_t \\ v_t \\ -v_t \\ v_t \end{bmatrix}$   
 $v_b$  = branch voltages

$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} i_b \\ i_b \\ i_b \\ i_b \\ i_b \end{bmatrix}$$




KCL:

$$\begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & | & 1 & 1 & 1 \\ 0 & 1 & | & 0 & -1 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \text{cut set equations}$$

$$0_t = C i_b$$

$$= \begin{bmatrix} 1 & 2 & | & -K \end{bmatrix} \begin{bmatrix} i_t \\ i_x \end{bmatrix} \Rightarrow i_t = K i_x \Rightarrow i_b = \begin{bmatrix} i_t \\ i_x \end{bmatrix} = \begin{bmatrix} -K \\ 1 \end{bmatrix} i_x$$

KVL: use loops

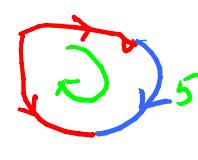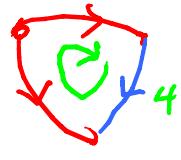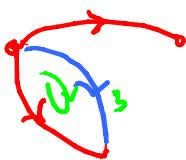

$$\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} = \left[ \begin{array}{cc|ccc} -1 & 0 & 1 & 0 & 0 \\ -1 & 1 & 0 & 1 & 0 \\ -1 & 1 & 0 & 0 & 1 \end{array} \right] \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix} \Rightarrow \underline{0}_t = \mathcal{T}v_t, \quad \mathcal{T} = \text{tie set matrix}$$

$$= \left[ \begin{array}{c|cc} K^T & 1 \\ & 1_3 \end{array} \right] \begin{bmatrix} v_t \\ v_L \end{bmatrix} \Rightarrow v_L = -K^T v_t \Rightarrow \begin{bmatrix} v_t \\ v_L \end{bmatrix} = \begin{bmatrix} 1_t \\ -K^T \end{bmatrix} v_t$$

$$v_b = e^T v_t, \quad \underline{0}_t = e^T i_b$$

$$i_b = \mathcal{T}^T i_L; \quad \underline{0}_L = \mathcal{T} v_b$$

note if know  $K$ , know both  
 $e \in \mathcal{T}$  so  $KVL \Leftrightarrow KCL$



$$\Rightarrow \text{Power in from outside} = 0 = \sum_{i=1}^b v_b i_b = v_b^T i_b = v_b^T \mathcal{T} i_L = v_t^T e^T \mathcal{T} i_L$$

$$\Rightarrow v_b^T \mathcal{T} = \underline{0}_L$$

$$\Rightarrow e^T \mathcal{T}^T = \underline{0}_{t,L}$$


$$\left[ \begin{array}{c|cc} 1 & -K \\ \hline & 1_L \end{array} \right] \left[ \begin{array}{c} Q \\ \hline 1_L \end{array} \right] \Rightarrow Q = K \Rightarrow \mathcal{T}^T = \left[ \begin{array}{c} Q \\ \hline 1_L \end{array} \right]$$

$$\begin{aligned} \mathcal{T} &= [Q^T \quad 1_L] \\ &= [-K^T; \quad 1_L] \end{aligned}$$

for laws of components use

$$Y_{6 \times 6} = \begin{bmatrix} G_i & 0 & 0 & 0 & 0 \\ 0 & AC_P & 0 & 0 & 0 \\ 0 & 0 & G_T + AC_H & 0 & 0 \\ G_m & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & G_L \end{bmatrix}$$

$$i_f = \frac{1}{G_L} R_i$$

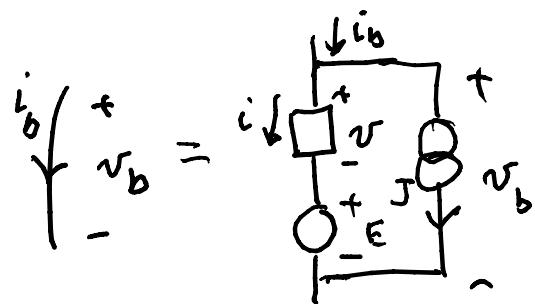

$$v_b = v + \xi \quad i = Y_{bxb} v$$

$$i_b = i + J$$

$$i = i_b - J = Y_{bxb} \cdot v = Y_{bxb} (v_b - E) \Rightarrow$$

$$i_b = Y_{bxb} \times v_b + (J - Y_{bxb} E)$$

$$i_b = \mathcal{C}^T i_L, \quad 0 = \mathcal{C} i_b = 0 = \mathcal{C} Y_{bxb} \mathcal{C}^T \cdot v_L + \mathcal{C} (J - Y_{bxb} E)$$

$$\Rightarrow (\mathcal{C} Y_{bxb} \mathcal{C}^T - \mathcal{C} J) = \mathcal{C} Y_{bxb} \mathcal{C}^T \cdot v_L$$

*t equations  
for t unknowns  
(v\_L)*

$$\Rightarrow v_L = [\mathcal{C} Y_{bxb} \mathcal{C}^T]^{-1} \underbrace{(\mathcal{C} Y_{bxb} \mathcal{C}^T - \mathcal{C} J)}$$

*Norton's equivalent current  
sources feeding tree branches*

$$\left[ \begin{array}{c|cc} 1 & 0 \\ 0 & 1 \end{array} \right] \left[ \begin{array}{c|cc} 1 & 1 & i \\ 0 & 0 & -1 - 1 \end{array} \right] \left[ \begin{array}{ccccc} G_i & 0 & 0 & 0 & 0 \\ 0 & \alpha C_P & 0 & 0 & 0 \\ 0 & 0 & g_{\pi} + \alpha C_{\pi} & 0 & 0 \\ g_m & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & G_L \end{array} \right] \left[ \begin{array}{c|cc} 1 & 0 \\ 0 & 1 \\ \vdots & \vdots \\ 1 & 0 \\ \vdots & \vdots \\ 1 & -1 \end{array} \right] = \mathcal{C} Y_{bxb} \mathcal{C}^T$$

$$= \left[ \begin{array}{ccccc} G_i + g_m & 0 & g_{\pi} + \alpha C_{\pi} & 0 & G_L \\ -g_m & \alpha C_P & 0 & 0 & -G_L \end{array} \right] \left[ \begin{array}{c|cc} 1 & 0 \\ 0 & 1 \\ \vdots & \vdots \\ 1 & 0 \\ \vdots & \vdots \\ 1 & -1 \end{array} \right]$$

$$= \left[ \begin{array}{cc} G_i + g_m + g_{\pi} + \alpha C_{\pi} + G_L & -G_L \\ -g_m - G_L & \alpha C_{\pi} + G_L \end{array} \right]$$