

Richards' function, p. 361




$$R(a) = \frac{kz(a) - az(k)}{kz(k) - az(a)} \Rightarrow \frac{1}{R(a)} = G(a) = \frac{kz(k) - az(a)}{kz(a) - az(k)}$$

$$G(k) = \frac{kz(k) - kz(k)}{kz(k) - kz(k)} = \frac{0}{0} \Rightarrow a=k \text{ factors numerator \& denominator if } y(a) \text{ is rational in } a$$

$$G(-k) = \frac{kz(k) - (-k)z(-k)}{kz(-k) - (-k)z(k)} = \frac{kz(k) + kz(-k)}{kz(-k) + kz(k)} = \frac{k(z(k) + z(-k))}{k(z(k) + z(-k))}$$

$$= \frac{0}{0} \text{ if } y(k) = -y(-k) \Rightarrow \text{if } \exists y(a) = \frac{1}{2}(y(a) + y(-a)) \text{ has a zero at } a=k$$

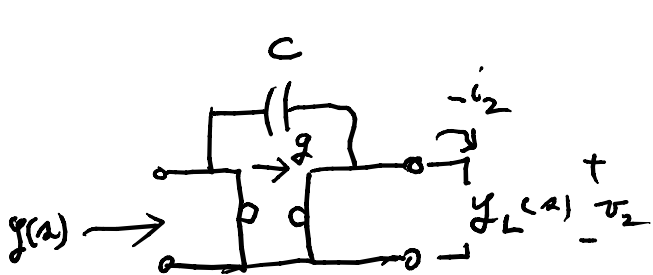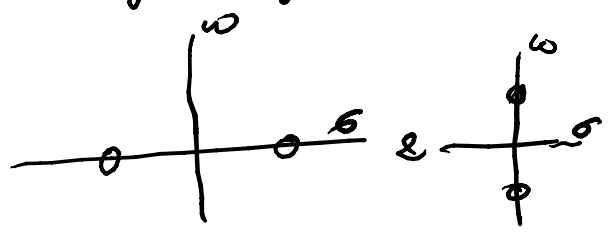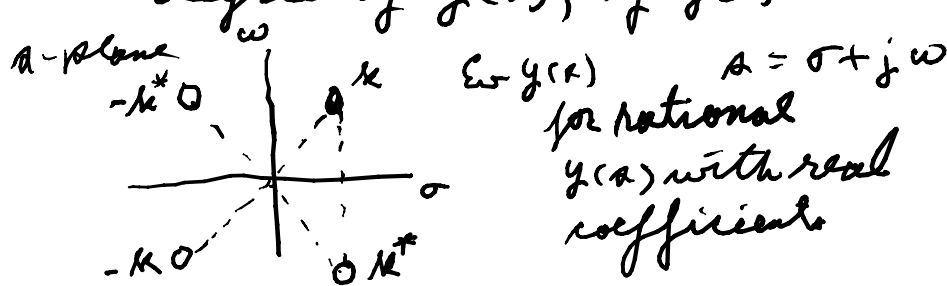allows degree of $G(a)$ to go down by 1 from the degree of $y(a)$, if $y(a)$ is a ratio of polynomials



$$Y = \begin{bmatrix} ca & -ca-g \\ -ca+g & ca \end{bmatrix} ; \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} ca & -ca-g \\ -ca+g & ca \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$\Rightarrow (-y_L - ca)v_2 = (-ca + g)v_1$$

$$i_1 = y \cdot v_1 = \frac{ca(-ca-g)(-ca+g)}{-y_L - ca} v_1$$

$$y(a) = \frac{y_{11} + y_{12} \frac{1}{-y_L - y_{22}} \times y_{21}}{1} = \frac{-y_L y_{11} - y_{11} y_2 + y_{12} y_2}{-y_L - y_{22}}$$

$$= \frac{(y_L y_{11} + \Delta y)}{(y + y_{22})}$$

$$= (ac y_L + g^2) / (y_L + ac) \Rightarrow y \cdot y_L + y \cdot ac = ac y_L + g^2$$

$$(y - ac) y_L = g^2 - ac \cdot y$$

$$y_L(a) = \frac{g^2 - ac \cdot y(a)}{y(a) - ac}$$

$$= g^2 \left(\frac{1 - \frac{ac}{g} \cdot \frac{y(a)}{g}}{y(a) - ac} \right)$$

$$\frac{y_L(a)}{g} = \frac{1 - \frac{ac}{g} \cdot \frac{y(a)}{g}}{\frac{y(a)}{g} - \frac{ac}{g}}$$


compare $\frac{ky(k) - ay(a)}{ky(a) - ay(k)}$

$$ky(k) \left[1 - \frac{a}{k} \cdot \frac{y(a)}{y(k)} \right]$$

$$ky(k) \left[\frac{y(a)}{y(k)} - \frac{a}{k} \right]$$

$$\Rightarrow \frac{1 - \frac{a}{k} \cdot \frac{y(a)}{y(k)}}{\frac{y(a)}{y(k)} - \frac{a}{k}}$$

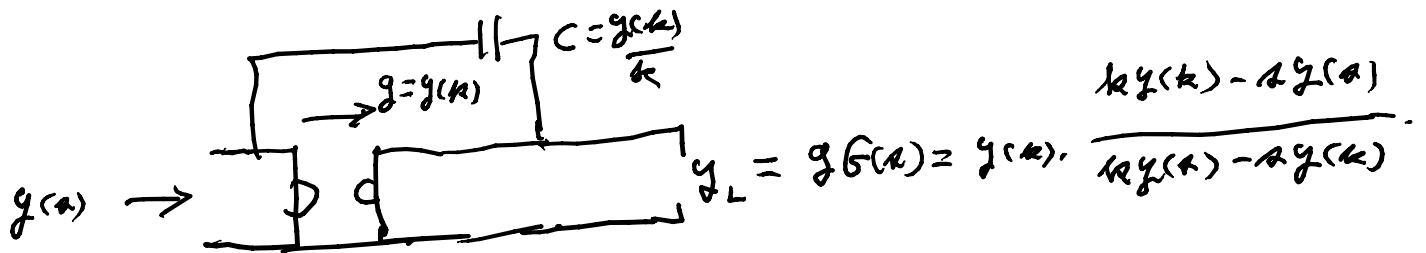take $\Rightarrow k = \frac{g}{c}, \quad g = y(k)$
 $\Rightarrow c = \frac{g}{k} = \frac{y(k)}{k}$



allows synthesis if k is real

look at lossless circuits:

$P(t) \Rightarrow$ average power in sinusoidal steady state

$$P(\omega) = 0 \text{ if lossless } \operatorname{Re}(V^{*T} I) = 0 = \operatorname{Re}[V_1^* I_1 + V_2^* I_2 \dots V_n^* I_n]$$

$$\operatorname{Re} x = \frac{1}{2} (x + x^*) = \frac{1}{2} (x + x^{*T}) \quad j^* = -\sqrt{-1} = -j$$

$$\operatorname{Re} V^{*T} I = \frac{1}{2} (V^{*T} I + I^{*T} V) = 0 \quad \text{if } I = Y(j\omega) V$$

$$= \frac{1}{2} (V^{*T} Y(j\omega) V + V^{*T} Y_{C(j\omega)}^{*T} V) = \frac{1}{2} V^{*T} [Y(j\omega) + Y_{C(j\omega)}^{*T}] V$$

$$\frac{1}{2} [Y(j\omega) + Y(j\omega)^T] = O_{n \times n}$$

$$= \frac{1}{2} [Y(j\omega) + Y(-j\omega)] = O_{n \times n} \quad \text{if entries in } Y(s) \text{ are rational with real coefficients}$$

for scalars $y(s)$ rational real coefficients



$$\frac{1}{2} (y(j\omega) + y(-j\omega)) = 0 \quad \text{for all } \omega$$

$$y(s) + y(-s) \equiv 0 \quad \text{for a lossless } y(s)$$

since it is 0 on a dense set, waxis.


$$y(s) = -y(-s) \Rightarrow \text{Ev } y(s) \equiv 0 \quad \therefore \text{for the Richards' function}$$

can't be if the circuit can choose any k we want for $y(s)$ is stable $\frac{k_0}{s - s_0} \Rightarrow e^{s_0 t}$

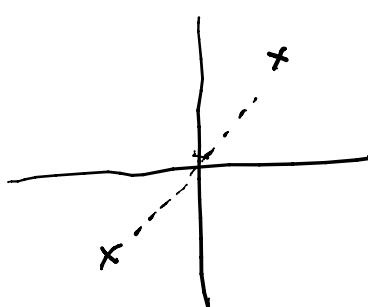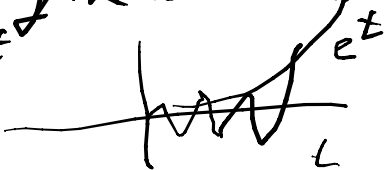all poles are on $j\omega$ axis

Let $z(s) = \frac{1}{y(s)}$ satisfies $P(\omega) = 0 \Rightarrow$ poles of $z(s)$ are on the $j\omega$ axis. \Rightarrow zeros of $y(s)$ are on $j\omega$ axis

see p. 342 no double poles $\rightarrow \frac{k_0 s}{(s - s_0)^2} \rightarrow$ 

$$y(s) = \frac{\prod_k (s - j\omega_k)(s - j\omega_k^*)}{\prod_k (s - p_k)(s - p_k^*)}$$

$$= \sum_k \frac{K_k}{s - j\omega_k} + \frac{K_k^*}{s + j\omega_k} +$$

need real residues $\Rightarrow K_k = K_k^*$

$$= \sum \frac{2K_k s}{s^2 + \omega_k^2} + K_\infty s$$

is passive if $K_k > 0$

poles & zeros will alternate

Ex: $y(s) = \frac{2s}{s^2 + 1} + \frac{3s}{s^2 + 2} + \frac{1}{s} + 5s = \frac{a_6 s^6 + a_4 s^4 + a_2 s^2 + a_0}{s(b_4 s^4 + b_2 s^2 + b_0)}$

$$= \frac{\text{Ev polynomial}}{\text{od polynomial}}$$