
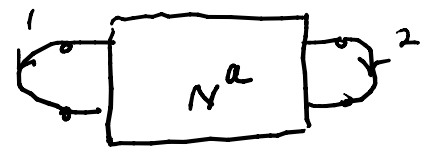

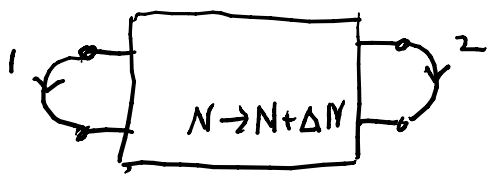
$$\frac{\partial T(x)}{\partial x} / \frac{T(x)}{x} = S_x = \text{sensitivity of } T \text{ with respect to } x$$



$N^a = \text{adjoint}$
same graph as N

$$v_b = \begin{bmatrix} v_1 \\ v_2 \\ \vdots \\ v \end{bmatrix}$$

$$i_b = \begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i \end{bmatrix}$$

assume $Y_N = Y$ exists
as does $Y_{N^a} = Y^a$

Have i_b, v_b, i_b^a, v_b^a

$$i_b^T v_b^a - i_b^a T v_b = 0$$

$$i_1 \cdot v_1^a - i_1^a v_1 + i_2 \cdot v_2^a - i_2^a v_2 + v^T Y^T v^a - v^a T Y^a T v$$

Make a change in N, Δ ; but don't change in N^a

$$\Delta i_1 \cdot v_1^a - i_1^a \Delta v_1 + \Delta i_2 \cdot v_2^a - i_2^a \Delta v_2 + (\Delta v^T Y^T v^a - v^a T Y^a T \Delta v) + v^T \Delta Y^T v^a = 0$$

If interested in $\frac{v_2}{v_1} = T(x)$ then fix v_1 & see how v_2 changes, look at Δv_2 (as change something in N)

⇒ $\Delta v_1 = 0$; as want Δv_2 , isolate it by $i_2^a = 1$

set $v_1^a = 0 \Rightarrow \Delta i_1 v_1^a = 0$; force $\Delta i_2 = 0$ by open circuit on port 2 of N



force

$$(\Delta v^T Y^T v^a - v^a T Y^a T \Delta v) = 0 = \Delta v^T Y^T v^a - \Delta v^T Y^a v^a$$

$$= \Delta v^T (Y^T - Y^a) v^a \Rightarrow Y^T - Y^a = 0_{(b-2) \times (b-2)}$$

↑ since Y 's exist, holds for all v^a & v

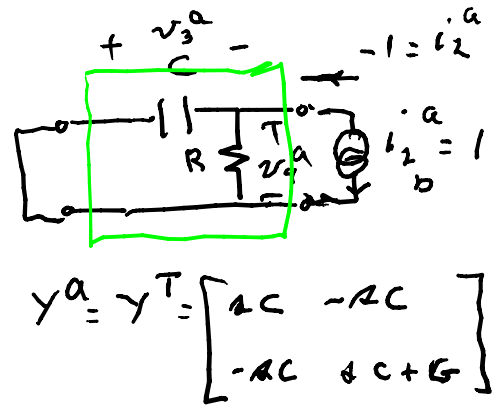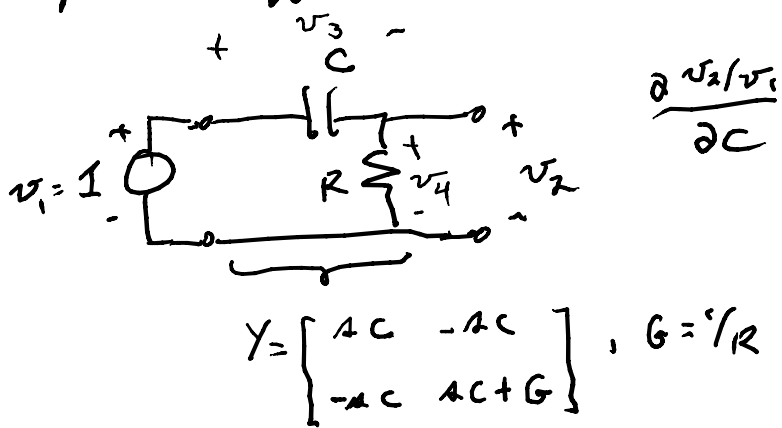\Rightarrow derive $Y^a = Y^T = \text{transpose } Y \text{ of original}$
 \therefore just analyze the circuits to get $\frac{\Delta v_2 / \Delta x}{v_1=1} = \frac{\Delta TCA}{\Delta x}$, $x = \text{component}$



if change C ; $\Delta Y = \begin{bmatrix} \Delta C & -\Delta C \\ -\Delta C & \Delta C \end{bmatrix} = \Delta C \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix}$

know $-\Delta v_2 = -v^T \Delta Y v_a = -\Delta C [v_3 \ v_4] \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix} \begin{bmatrix} v_3^a \\ v_4^a \end{bmatrix}$


for N; $v_4 = \frac{R}{R + \frac{1}{\Delta C}} \cdot v_1$, $v_3 = \frac{1/\Delta C}{R + \frac{1}{\Delta C}} \cdot v_1$; $v_3^a = -v_4^a$
 $v_1 = 1$ $v_4^a = \frac{1}{G + \Delta C} \cdot (-1)$

$$-\Delta v_2 = -\Delta C \left[\frac{R\Delta C}{1 + R\Delta C}, \frac{1}{1 + R\Delta C} \right] \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix} \begin{bmatrix} \frac{1}{G + \Delta C} \\ \frac{1}{G + \Delta C} \end{bmatrix}$$

$$= -\Delta C \frac{1}{1 + R\Delta C} \cdot \frac{1}{G + \Delta C} \begin{bmatrix} R\Delta C - 1 & -R\Delta C + 1 \end{bmatrix} \begin{bmatrix} 1 \\ -1 \end{bmatrix} =$$

$$= -\frac{2(R\Delta C - 1)}{(1 + R\Delta C)(G + \Delta C)} (\Delta C)$$
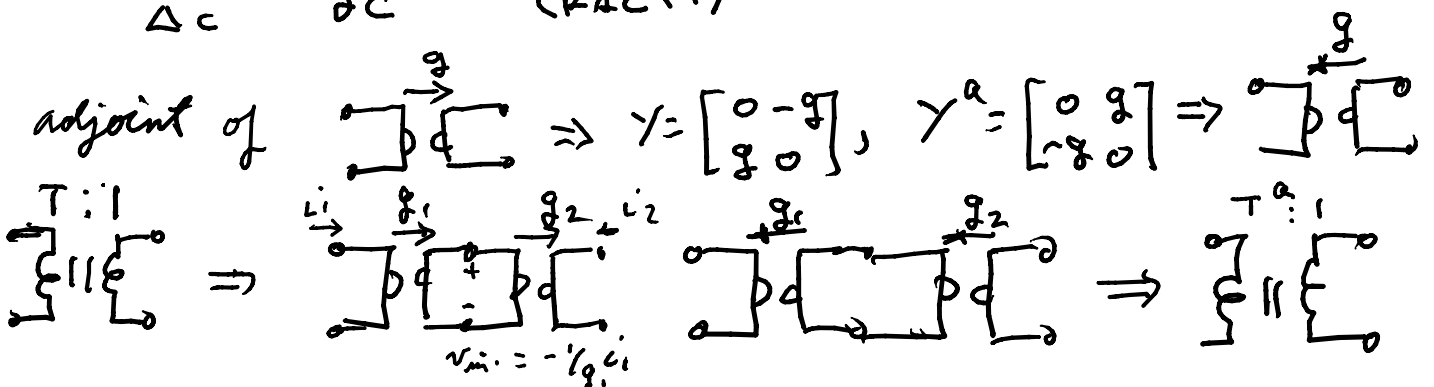
$$\Rightarrow \frac{\Delta v_2}{\Delta C} = \frac{\partial v_2}{\partial C} = \frac{2\Delta(R\Delta C - 1) \cdot R}{(R\Delta C + 1)^2} = \frac{\partial (v_2/v_1)}{\partial C}$$




$$v_2 = v_{mid} = -\frac{1}{g_1} i_1$$

$$i_2 = g_2 \cdot v_{mid}$$



$$-\frac{i_1}{g_1} = \frac{i_2}{g_2} = -\frac{g_2 i_1}{g_1} = i_2$$

$$v_2 = \frac{g_2}{g_1} v_1 \Rightarrow T = \frac{g_2}{g_1}$$

$$T^a = T = g_2/g_1$$

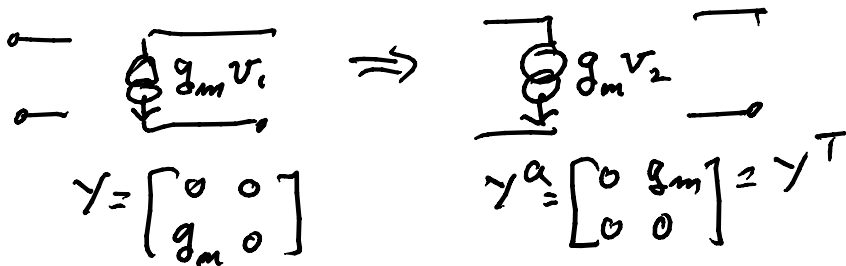

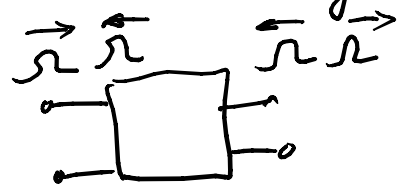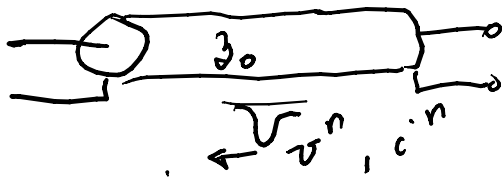scattering matrix \Rightarrow waves; incident & reflected



$$\begin{aligned} 2v &\triangleq v^i + v^n & \Rightarrow & 2v^i = 2v + 2Z_0 i & \Rightarrow & 2v^i = v + Z_0 i \\ 2Z_0 i &\triangleq v^i - v^n & \Rightarrow & 2v^n = 2v - 2Z_0 i & \Rightarrow & 2v^n = v - Z_0 i \end{aligned}$$

normally $Z_0 = 50 \Omega \Rightarrow$ normalize to 1 \Rightarrow

like direct & quadrature axis voltages of power systems.

Define scattering matrix by $v^n = S v^i$

$$\text{but } v^i = (1_2 + \gamma)v, \quad v^n = (1_2 - \gamma)v$$

$$\Rightarrow v = (1_2 + \gamma)^{-1} v^i \Rightarrow v^n = (1_2 - \gamma)(1_2 + \gamma)^{-1} v^i$$

$$S = (1_2 - \gamma)(1_2 + \gamma)^{-1}$$

$$\left[\begin{array}{c} \boxed{1} \\ \boxed{C} \end{array} \right] \quad \gamma = 2C \quad S = (1 - \gamma)/(1 + \gamma) = \frac{1 - 2C}{1 + 2C} ; \text{ here } \bar{S}^T(-A) = S(-A)$$

look at $v^T i = \frac{1}{2}(v^i + v^n)^T (\frac{1}{2}[v^i - v^n])$

general property of lossless circuit