

scattering matrix, p. 177


$$2v^i = v + z_0 i$$

$$2v^n = v - z_0 i$$

normalize z_0 to 1 for a 2-port

$$2v^i = v + i$$

$$2v^n = v - i$$

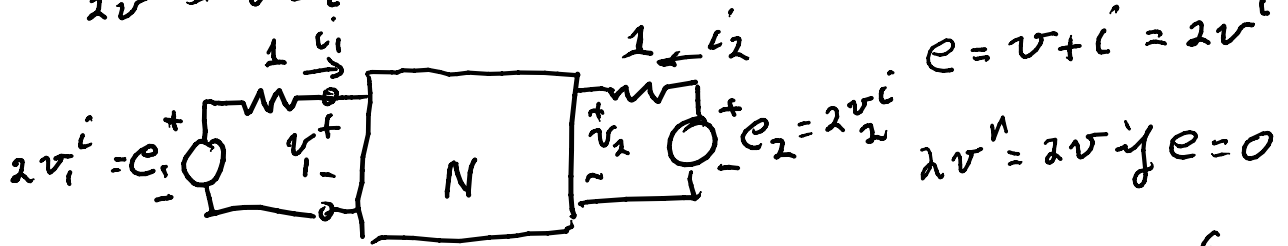

$$e = v + i = 2v^i$$

$$2v^n = 2v \text{ if } e = 0$$

$$E_1 = 2V_1^i; E_2 = 0 \Rightarrow V_2 = V_2^n = \frac{V_2}{E_1} = \frac{V_2^n}{2V_1^i} \Big|_{V_2^i = 0} = \frac{S_{21}}{2} \quad \begin{matrix} S_{21} = \\ \text{transmission} \\ \text{coefficient} \end{matrix}$$

$$V^n = S V^i$$


gives physical meaning of S_{21} as a voltage transfer ratio

$$S_{11} = \frac{V_1^n}{V_1^i} \Big|_{V_2^i = 0} = \text{reflection coefficient at port 1 when terminate at port 2 in } z_0 = 1$$

$$i = \frac{1}{2} \cdot 2v^i = v^i$$

If $z_{11} = 1$, other $z_{ij} = 0 \Rightarrow$
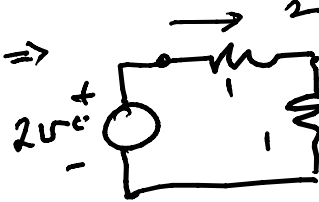
$$S_{11} = \frac{v_1^n}{v_1^i} = \frac{v - v}{v + v} = 0$$



$$V^n = S(\omega) V^i \Rightarrow \omega = j\omega \Rightarrow \text{Laplace transforms} = \text{Fourier transforms}$$

Passive case $E(t) = \int_{-\infty}^t p(\tau) d\tau \geq 0 \Rightarrow$ also if $t \rightarrow \infty$

$$E(\infty) = \int_{-\infty}^{\infty} v^T(\tau) i(\tau) d\tau \geq 0$$

$$v = v^i + v^n, \quad i = v^i - v^n$$

$$v^T i = (v^i + v^n)^T (v^i - v^n) = v^{iT} \cdot v^i - v^{nT} \cdot v^n + \underbrace{v^{nT} \cdot v^i - v^{iT} \cdot v^n}_{\text{sum} = 0}$$

$$\mathcal{E}(\infty) = \int_{-\infty}^{\infty} [v^{iT}(t) \cdot v^i(t) - v^{nT}(t) \cdot v^n(t)] dt \geq 0 \text{ for passive}$$

$\int_{-\infty}^{\infty} v_i^i(t) v_i^i(t) dt$ is one component to look at

Parseval theorem

$$\int_{-\infty}^{\infty} f(t) g(t) dt = \int_{-\infty}^{\infty} \mathcal{F}^*[f(t)] \mathcal{F}[g(t)] df$$

$$\mathcal{F}[f] = \int_{-\infty}^{\infty} f(t) e^{-j2\pi ft} dt, \quad g(t) = \mathcal{F}^{-1}[\mathcal{F}[g]] = \int_{-\infty}^{\infty} \mathcal{F}[g] e^{+j2\pi ft} df$$

$$\Rightarrow \int_{-\infty}^{\infty} v_i^i(t) v_i^i(t) dt = \int_{-\infty}^{\infty} V_i^{i*}(j\omega) V_i^i(j\omega) d\omega \quad \omega = 2\pi f$$

$$\int_{-\infty}^{\infty} v(t) df = \int_{-\infty}^{\infty} [v^{iT}(t) \cdot v^i(t) - v^{nT}(t) \cdot v^n(t)] dt = \int_{-\infty}^{\infty} [V^{iT*} V^i - V^{nT*} V^n] \frac{d\omega}{2\pi} > 0 \Rightarrow \int_{-\infty}^{\infty} v^{iT} v^i > \int_{-\infty}^{\infty} v^{nT} v^n$$

$$\Rightarrow \int_{-\infty}^{\infty} [V^{iT*} V^i - V^{nT*} S(j\omega) S(j\omega) V^i] df \geq 0$$

$$= \int_{-\infty}^{\infty} V^{iT*} [I_2 - S^{T*}(j\omega) S(j\omega)] V^i df \geq 0$$

implies that $I_2 - S^{T*}(j\omega) S(j\omega)$ is a positive semidefinite

$\Rightarrow S(s)$ has no poles on $s = j\omega$

If $\mathcal{E}(\infty) = 0 \Rightarrow$ a lossless circuit $\Rightarrow I_2 = S^{T*}(j\omega) S(j\omega)$

$$\Rightarrow \text{lossless } S^{-1}(j\omega) = S^{T*}(j\omega)$$

If $S(j\omega)$ is rational in $j\omega$ with real coefficients (a real circuit) then $S^*(j\omega) = S(-j\omega)$

now replace $j\omega$ by $s = j\omega, \Rightarrow \omega = s/j$

\Rightarrow lossless $\Rightarrow \frac{1}{2} = S^T(-s)S(s)$ for all s ; this analytically continues S from $j\omega$ axis to whole s -plane

Ex: $S(s)$ for a capacitor; $Y(s) = sC$ $\frac{1}{s}C$



We have $v^n = S(s)v^i$

$$\left[\frac{v - v^i}{2} \right] = S(s) \left[\frac{v + v^i}{2} \right]$$

$$\frac{v - Y \cdot v}{2} = S(s) \left[\frac{v + Y \cdot v}{2} \right]$$

$$S(s) = \frac{1 - Y}{1 + Y} = \frac{1 - sC}{1 + sC}$$
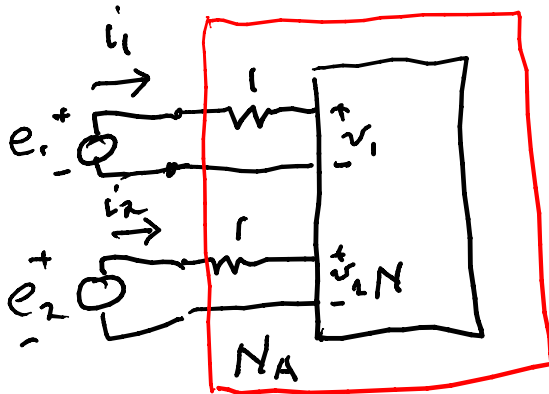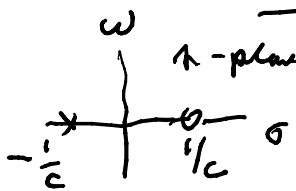
$$S(-s) = \frac{1 - (-s)C}{1 + (-s)C} = \frac{1 + sC}{1 - sC} = 1/S(s)$$



$N_A = \text{augmented } N$

$$i = Y_A \cdot e; \quad i = v - v_1, \quad e = 2v^i$$

$$(v^i - v^n) = Y_A \cdot 2v^i \Rightarrow (1_2 - 2Y_A)v^i = v^n$$

$S = 1_2 - 2Y_A \Rightarrow$ gives a nice way to find S

Here $\int v^i(t)v^i(t) dt \geq 0$ if finite \Rightarrow call v^i square integrable, it is in $L^2 = L^2$, Lebesgue integrable

if we apply $v^i \in L^2_b$

then $v^n \in L^2_b$


as $v = v^i + v^n \Rightarrow v \in L^2_b$, & $i \in L^2_b$ if N is passive

finite energy in v^i gives finite energy in v^n & v, i

Here for N passive, $S(s)$ is bounded real

if rational we call it BR: no poles in $\sigma > 0$
& $\frac{1}{2} - S^T(-s)S(s) \geq 0$
 $s = j\omega$

& only real coefficients

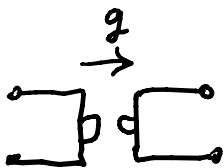Ex:  ; $Y = \begin{bmatrix} 0 & -g \\ g & 0 \end{bmatrix}$, $S = (I_2 - Y)(I_2 + Y)^{-1}$

$$S = \begin{bmatrix} 1+g & \\ -g & 1 \end{bmatrix} \begin{bmatrix} 1 & -g \\ g & 1 \end{bmatrix}^{-1}$$

$$\begin{bmatrix} 1 & -g \\ g & 1 \end{bmatrix}^{-1} = \frac{1}{1+g^2} \begin{bmatrix} 1 & (-1)^{2+1}(-g) \\ (-1)^{1+2}(g) & 1 \end{bmatrix}$$

$$= \frac{1}{1+g^2} \begin{bmatrix} 1 & g \\ -g & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1+g & \\ -g & 1 \end{bmatrix}^2 \times \frac{1}{1+g^2}$$

$$= \frac{1}{1+g^2} \begin{bmatrix} 1-g^2 & 2g \\ -2g & 1-g^2 \end{bmatrix} \quad \begin{bmatrix} 1 & g \\ -g & 1 \end{bmatrix} \begin{bmatrix} 1 & g \\ -g & 1 \end{bmatrix}^2 = \begin{bmatrix} 1-g^2 & 2g \\ -2g & 1-g^2 \end{bmatrix}$$

Note $S = (I_2 - Y)(I_2 + Y)^{-1} \stackrel{?}{=} (I_2 + Y)^{-1}(I_2 - Y)$

$(I_2 + Y)(I_2 - Y) = I_2 - Y^2 = (I_2 - Y)(I_2 + Y)$

If $Y = Y^T$ then $S = S^T$ since $S^T = (I_2 + Y^T)^{-1}(I_2 - Y^T)$
 $= (I_2 + Y)^{-1}(I_2 - Y) = S$