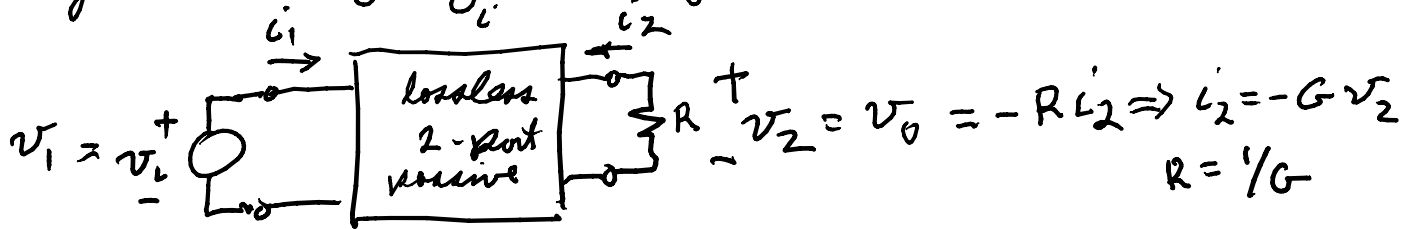


Synthesis of $\frac{v_o(s)}{v_i(s)}$ by terminated 2-port



$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$i_2 = -G v_2 = y_{21} v_1 + y_{22} v_2 \Rightarrow -(G + y_{22}) v_2 = y_{21} v_1$$

$$\frac{v_2}{v_1} = \frac{-y_{21}}{G + y_{22}} = \frac{-y_{21}}{1 + y_{22}} \quad \text{if normalize } G = 1$$

\therefore design $y_{22} = PR$ lossless = $\frac{n_{22}(s)}{d_{22}}$; n & d polynomial

as poles of y_{21} will need to be in poles of y_{22} then finite zeros all in y_{21}

$$\begin{aligned} \text{Ex: } \frac{v_o}{v_i} &= \frac{k}{s^3 + 3s^2 + 3s + 1} = \frac{k}{(s^3 + 3s) + (3s^2 + 1)} = \\ &= \frac{k(3s^2 + 1)}{\left(\frac{s^3 + 3s}{3s^2 + 1}\right) + 1} = \frac{k/(s^3 + 3s)}{1 + \left(\frac{3s^2 + 1}{s^3 + 3s}\right)} \end{aligned} \quad \text{have 2 possible } y_{22}$$

$$y_{22,1} = \frac{s^3 + 3s}{3s^2 + 1}, \quad y_{22,2} = \frac{3s^2 + 1}{s^3 + 3s}$$

$$\int \frac{1}{s} \Rightarrow \text{open @ } s = \infty$$

$$\int s \Rightarrow \text{short @ } s = \infty$$



gives zeros of transmission at $s = \infty$


1st Lauer

\therefore desire a 1st Lauer synthesis of Y_{22}


$$Y_{22} = \frac{s^3 + 3s}{3s^2 + 1}$$

$$\begin{array}{r} 3s^2 + 1 \overline{) s^3 + 3s} \\ \underline{3s^2} \\ s \\ \underline{3s} \\ 1 \\ \underline{3s} \\ \end{array}$$


$$\frac{9}{8}s = L_1$$

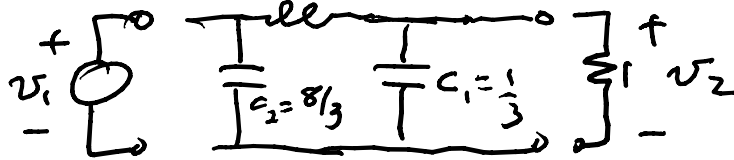
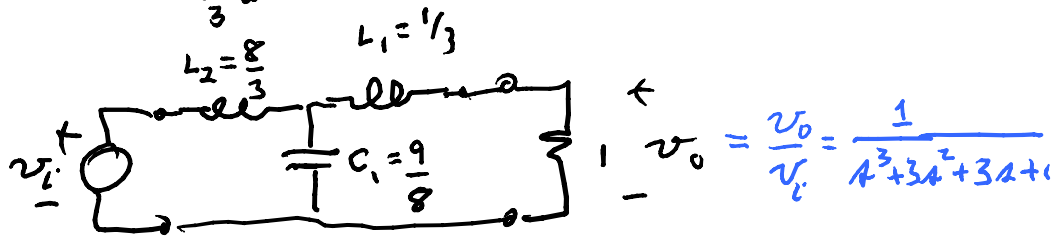
$$Y_{22} = \frac{3s^2 + 1}{s^3 + 3s} = \frac{1}{\frac{1}{3}s + \frac{1}{\frac{9}{8}s + \frac{1}{\frac{8}{3}s}}}}$$


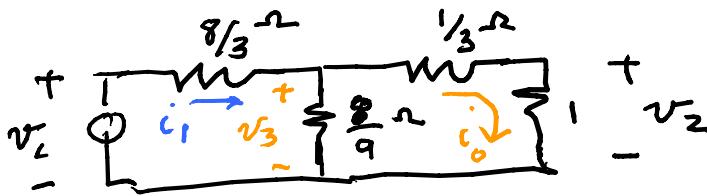
$$\frac{v_o}{v_i} = \frac{k}{s^3 + 3s^2 + 3s + 1} \quad @ \quad s=1 = \frac{v_o}{v_i} = \frac{k}{8}$$




assume $v_o = 1V$, $i_o = 1A \Rightarrow v_3 = 1 + \frac{1}{3} = \frac{4}{3}V$

$$i_1 = \frac{9}{8} \cdot \frac{4}{3} + 1 = \frac{3}{2} + 1 = \frac{5}{2} \Rightarrow v_i = \frac{8}{3} \cdot i_1 + v_3$$

$$v_i = \frac{8}{3} \cdot \frac{5}{2} + \frac{4}{3} = \frac{20}{3} + \frac{4}{3} = \frac{24}{3} \text{ for } v_o = 1$$
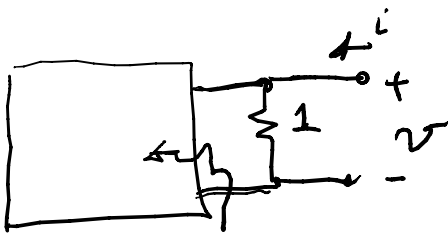
$$\therefore \text{for } \frac{v_2}{v_1} = \frac{1}{24/3} = \frac{3}{24} = \frac{1}{8} = \frac{k}{8} \Rightarrow k=1$$



PR $y(s)$
that's lossless

$$i = (1+y) \cdot v \Rightarrow v = \frac{i}{1+y}$$

\Rightarrow natural response for $i=0$
is due to zeros of $1+y$
means all zeros of $1+y$ are in
the open left half plane
of $1+y$

$$1 + \frac{n}{d} = \frac{d+n}{d} \Rightarrow \text{zeros are}$$

zeros of $n+d$ of y

\therefore if y is PR lossless

then for $y = \frac{n}{d}$ we have $P(s) = n(s) + d(s)$ is a

Hurwitz polynomial \Leftrightarrow no zeros
in $\sigma > 0$

\Rightarrow gives a nice test for

Hurwitz polynomials $P(s) = E \cdot P(s) + O \cdot d(s)$

$$y = 1 + \frac{O \cdot P}{E \cdot P} \text{ or } 1 + \frac{E \cdot P}{O \cdot P}$$

$$P(s) = s^5 + 4s^4 + 3s^3 + 2s^2 + s + 1$$

$$(s^5 + 3s^3 + s) + (4s^4 + 2s^2 + 1)$$

$$\frac{s^5 + 3s^3 + s}{4s^4 + 2s^2 + 1} = y(s)$$

$$4s^4 + 2s^2 + 1 \overline{) s^5 + 3s^3 + s}$$

$$\begin{array}{r} \frac{1}{4}s \\ \hline 4s^4 + 2s^2 + 1 \overline{) s^5 + 3s^3 + s} \\ \underline{s^5 + \frac{1}{2}s^3 + \frac{1}{4}s} \\ \frac{5}{2}s^3 + \frac{3}{4}s \end{array}$$

$$\frac{5}{2}s^3 + \frac{3}{4}s \overline{) 4s^4 + 2s^2 + 1}$$

$$\underline{4s^4 + \frac{6}{5}s^2}$$

$$\frac{25}{8}s + 1$$

$$\frac{4}{5}s^2 + 1 \overline{) \frac{5}{2}s^3 + \frac{3}{4}s}$$


$$\underline{\frac{5}{2}s^3 + \frac{25}{8}s}$$

$$-\frac{1}{2}s \overline{) \sqrt{4/5 s^2 + 1}}$$

The Couner synthesis is not passive

$$= -\frac{32}{5} s + \frac{1}{-\frac{1}{8}s^2}$$


$L_1 = 8/5$ $L_2 = -32/5$

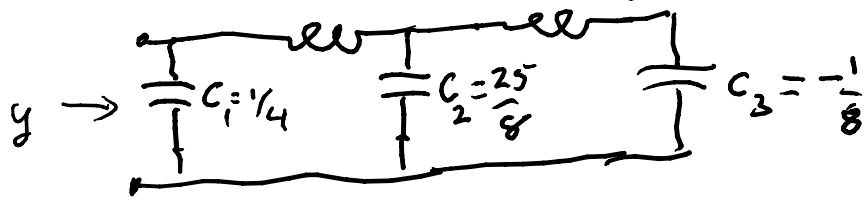

--- check that can use one of the two y_{22} 's \Rightarrow $\frac{od}{Ev}$ or $\frac{Ev}{od}$


$\frac{\sqrt{2}}{v_1}$ all zeroes of transmission @ $\infty = \frac{R}{A^n + \dots}$

n is even

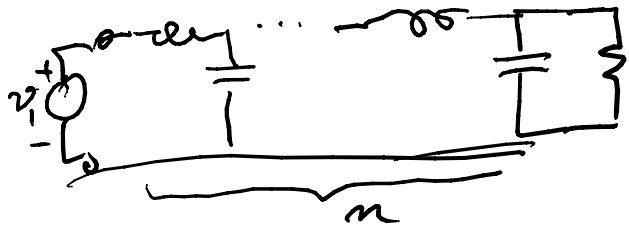


$y_{22} = \frac{Ev}{od} P \Rightarrow$ pole @ ∞ works

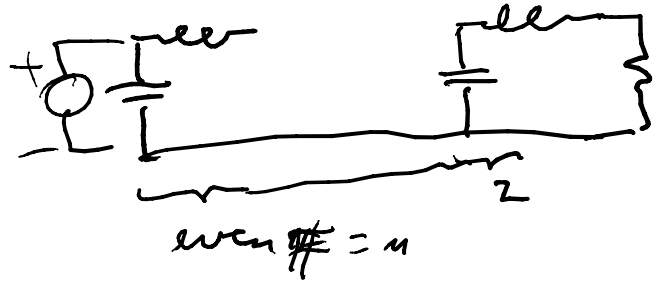$y_{22} = \frac{od}{Ev} P \Rightarrow 0$ @ ∞



doesn't work


n is odd

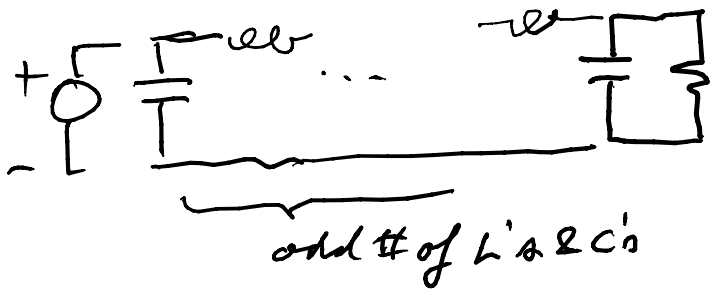

$y_{22} = \frac{od}{Ev} P$ pole @ ∞

doesn't work

$y_{22} = \frac{Ev}{od} P$ out @ ∞

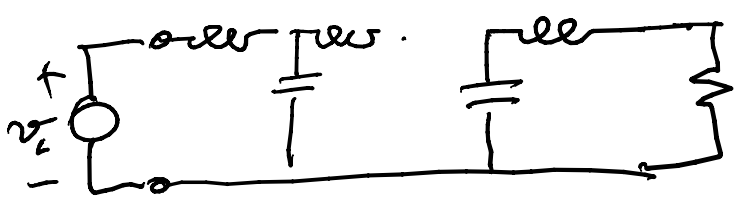

works

$\delta(\frac{\sqrt{2}}{v_1}) = n$

these work for low-pass $v_{oh}(s)$, terminated in R