

$$\underbrace{\begin{matrix} v_1 & v_2 \\ i_1 & i_2 \end{matrix}}_{\text{Transforms}} \quad i_2 = -i_N = -y_N v_2 = -y_N v_2$$

$$i_1 = -T i_2 = -T(-y_N v_2) = T y_N T^T v_1$$

$$\begin{aligned} v_2 &= T^T v_1 \\ i_1 &= T i_2 \end{aligned}$$

$$y_{in} = T y_N T^T$$

$$i = y v; \quad i = i_1 + i_2 = \text{sum 1st row + 2nd row of } T y_N T^T \\ = (\text{sum of all entries in } T y_N T^T) \cdot v$$

$$\begin{aligned} T y_N T^T &= \begin{bmatrix} t_{11} & t_{12} \\ t_{21} & t_{22} \end{bmatrix} \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} t_{11} & t_{21} \\ t_{12} & t_{22} \end{bmatrix} \\ &= \begin{bmatrix} t_{11} y_{11} + t_{12} y_{21} & t_{11} y_{12} + t_{12} y_{22} \\ t_{21} y_{11} + t_{22} y_{21} & t_{21} y_{12} + t_{22} y_{22} \end{bmatrix} \begin{bmatrix} t_{11} & t_{21} \\ t_{12} & t_{22} \end{bmatrix} \end{aligned}$$


$$\Rightarrow y = t_{11}^2 y_{11} + t_{11} t_{12} y_{21} + t_{11} t_{12} y_{12} + t_{12}^2 y_{22} \\ + t_{11} t_{21} y_{11} + t_{12} t_{21} y_{21} + t_{11} t_{22} y_{12} + t_{12} t_{22} y_{22} \\ + \dots$$

PR if
N is passive


but if there is a pole in y_{21} , not in y_{11} & y_{22}
then this is dominated by the terms like $t_{11} t_{12}$
 \therefore we can choose this to have a negative residue
 \Rightarrow that y is not PR

Partial pole removal for zeros of $\frac{v_2}{v_1}$ not at 0 or ∞ but on $j\omega$ axis:

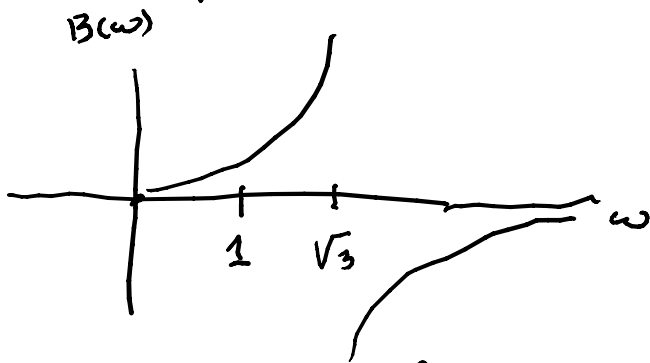
$$\frac{v_2}{v_1} = \frac{k(a^2+1)}{a^2+3a+3} = \frac{k \left(\frac{a^2+1}{a^2+3} \right)}{1 + \frac{3a}{a^2+3}} = -\frac{y_{21}}{1+y_{22}}$$



$$\frac{a^2+3}{3a} = \frac{1}{y_{22}}$$

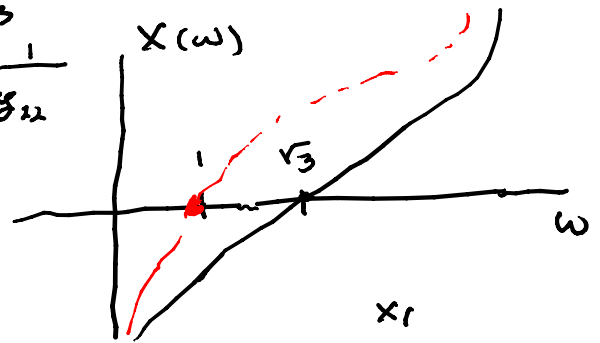

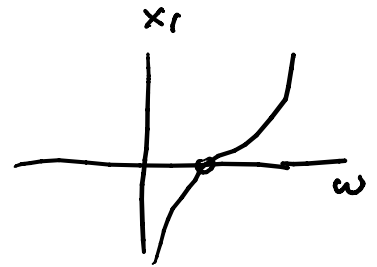
$$\frac{1}{y_{22}} = \frac{a^2+3}{3a} = \frac{a^2+1}{3a} + \frac{2}{3a} = \frac{1}{a} + \frac{1}{3}a$$



need a series arm

or a shunt arm

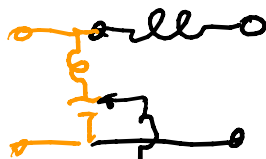



$$y_{22} = \frac{3a}{a^2+3}$$

$$z_1 = \frac{a^2+1}{3a} = \frac{1}{3}a + \frac{1}{3a}$$

\therefore need to write

$$\frac{v_2}{v_1} = \frac{k \left(\frac{a^2+1}{3a} \right)}{1 + \frac{a^2+3}{3a}} \Rightarrow y_{22} = \frac{a^2+3}{3a} = \frac{a^2+1}{3a} + \frac{2}{3a}$$

$$c_1 = 1/3$$

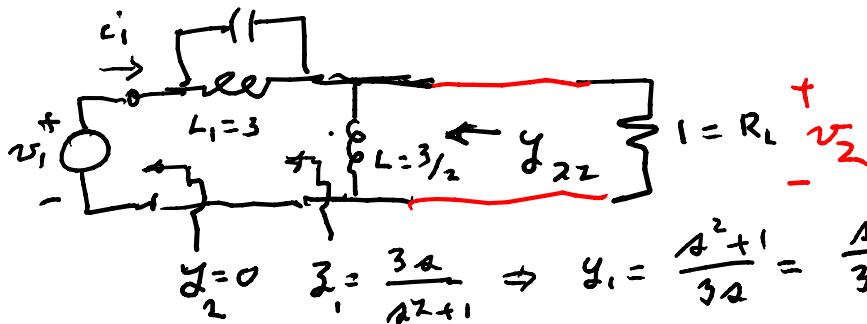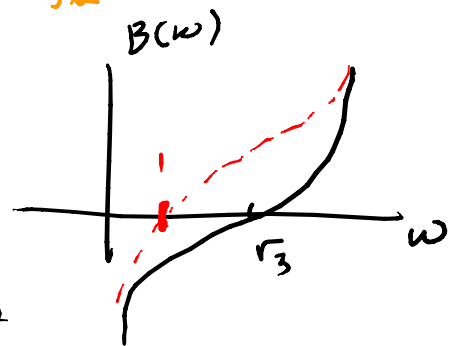

$$y_2 = 0 \quad z_1 = \frac{3a}{a^2+1} \Rightarrow y_1 = \frac{a^2+1}{3a} = \frac{1}{3} + \frac{1}{3a}$$

To find k :

$$v_2 = \left(\frac{1}{1 + \frac{1}{3a}} \right) L_1; \quad L_1 = \left(\frac{1}{3}a + \frac{1}{3a} \right) (v_1 - v_2) = \frac{a^2+1}{3a} (v_1 - v_2)$$

$$v_2 = \left(\frac{3a/2}{1 + \frac{3a}{2}} \right) \frac{a^2+1}{3a} (v_1 - v_2)$$


$$\left(1 + \frac{3R/2 \cdot R^2 + 1}{(1 + 3/2 R) \cdot 3R}\right) v_2 = \frac{3R/2 (R^2 + 1)}{(1 + 3/2 R) \cdot 3R} v_1$$

$$\frac{v_2}{v_1} = \frac{\frac{1}{2} (R^2 + 1) / (1 + \frac{3}{2} R)}{1 + \frac{\frac{1}{2} (R^2 + 1)}{(1 + \frac{3}{2} R)}} = \frac{\frac{1}{2} (R^2 + 1)}{1 + \frac{3}{2} R + \frac{1}{2} R^2 + \frac{1}{2}} = \frac{R^2 + 1}{3 + 3R + R^2}$$

$\Rightarrow k=1$ and synthesized the desired $\frac{v_2}{v_1}$

How to make a negative capacitor:

Use a negative impedance converter: NIC

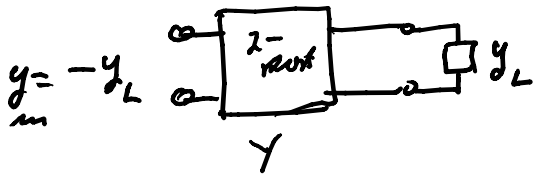

$$y_{in} = y_{11} - \frac{y_{21} y_{12}}{y_{22} + y_L} = \frac{\Delta y + y_{11} y_L}{y_{22} + y_L}$$

can not get an NIC out of a 2-port with an admittance

Chain matrix, Y

$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = Y \begin{bmatrix} v_2 \\ -i_2 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} v_2 \\ -i_2 \end{bmatrix}$$

several types of NIC $i_2 = -y v_2$

a) $v_1 = v_2$
 $i_1 = i_2$ $\Rightarrow i_1 = -y v_1$


$$Y = \begin{bmatrix} 1 & 0 \\ 0 & -1 \end{bmatrix} \text{ current inverting}$$

b) $v_1 = -v_2$
 $i_1 = -i_2$
 $i_1 = y_{in} v_1 = -y_{in} v_2 = -\frac{1}{y_L} y_{in} (-i_2)$
 $v_2 = -\frac{1}{y_L} i_2$

$$Y = \begin{bmatrix} -1 & 0 \\ 0 & 1 \end{bmatrix} \text{ voltage inverting NIC}$$

if $y_{in} = -y_L \Rightarrow i_1 = -i_2$

for the I NIC can make in 2 ways

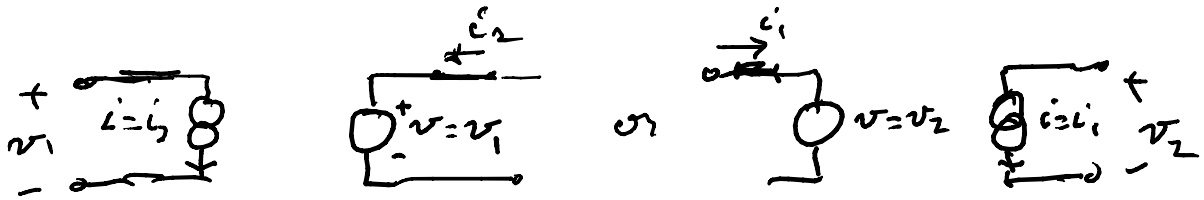

can use 2 forms for V NIC also