

*1. a) If voltage @ C not good $> |V_{T0}|$ & $< V_{DD} - |V_{T0}|$ both transistors would be ohmic; assume it is the case

$$I_{Dn} = \frac{K_P W}{2 L} \left\{ (V_{DD} - |V_{T0}|) V_C - \frac{1}{2} V_C^2 \right\} = I_{Sp} = \frac{K_P W}{2 L} \left\{ (V_{DD} - 0 - |V_{T0}|)(V_{DD} - V_C) - \frac{1}{2} (V_{DD} - V_C)^2 \right\}$$

$$\Rightarrow V_{DD} V_C - V_C^2 - \frac{1}{2} V_C^2 = V_{DD}^2 - V_{DD} V_C - V_{DD} + V_C - \frac{1}{2} V_{DD}^2 + \frac{1}{2} V_{DD} V_C - \frac{1}{2} V_C^2 \Rightarrow \text{solve for } V_C$$

$$\Rightarrow 0 = \frac{1}{2} V_{DD}^2 - V_{DD} - (V_{DD} - 2) V_C \Rightarrow$$

$$V_C = \frac{V_{DD}(\frac{1}{2} V_{DD} - 1)}{V_{DD} - 2} = \frac{9(4.5 - 1)}{7} = \underline{4.5V = V_C}$$

since $4.5 = V_C = V_{DSn} < V_{GSn} - |V_{T0n}| = 8$ M_n is ohmic
 & $4.5 = V_{DB} - V_C = V_{SDp} < V_{GSp} - |V_{T0p}| = V_{DD} - 0 - 1 = 8$, M_p is ohmic
 so the assumption is valid & $V_C = V_{DD}/2$ [not a good logic device]


b) By symmetry $V_C = V_{DD}/2$ when $A=1, B=0$,
 For the other 2 cases the circuit is an inverter, so
 $A=0=B \Rightarrow C=1$; $A=1=B \Rightarrow C=0$

#2. For the given circuit, $V_{GS} = 0$, so the law is

$$I = I_S (1 - e^{-V/V_T})$$

a) $g = I_S (-1) (-1/V_T) e^{-V/V_T} = \frac{I_S}{V_T} \cdot e^{-V/V_T} = g$

b) $R = \frac{1}{g} \Big|_{V=V_2} = \frac{0.026}{10^{-18}} \cdot e^{\frac{1}{2 \times 0.026}} = 0.026 \times 10^{18} \times 2.248 \times 10^8$
 $= 5.895 \times 10^{24} \Omega \Rightarrow$ a very large small signal R
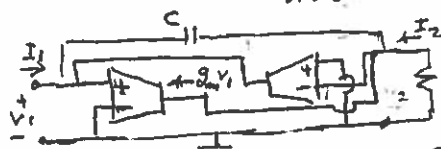
#3. a)  ; $\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ -GV_2 \end{bmatrix} = \begin{bmatrix} ca & -ca + gm \\ -ca - gm & ca \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$

from second row $-GV_2 - caV_2 = (-ca - gm)V_1 \Rightarrow \frac{V_2}{V_1} = \frac{ca + gm}{ca + G} = \frac{a + gm/c}{a + G/c}$

b) zero: $a_0 = -gm/c$, pole: $a_p = -G/c$

#4. $I_C = \beta I_B = 2 \times 10^2 \times 10^{-5} = 2 \times 10^{-3} A = I_S = \frac{K_P W}{2 L} (V_{SG} - |V_{T0}|)^2 \Rightarrow V_{SG} = |V_{T0}| + \frac{2L}{K_P} I_S$
 assume M_{out} in saturation $\Rightarrow I_{S_{out}} = 2 \left(\frac{W}{L}\right)_{min} \cdot I_C = 2 \times 1 \times 2 \times 10^{-3} A$
 $\Rightarrow V_{R_L} = 1 \times 4 \times 10^{-3} V = 4 mV$

(check assumption: $V_{SG_{min}} - |V_{T0}| = \frac{2(\frac{1}{2})}{K_P} I_S = \frac{2 \times 10^{-3}}{3 \times 10^{-4}} = 6.67V < V_{DD} - V_{R_L} = 8.996$

i. $V_{R_L} = 4 mV$