
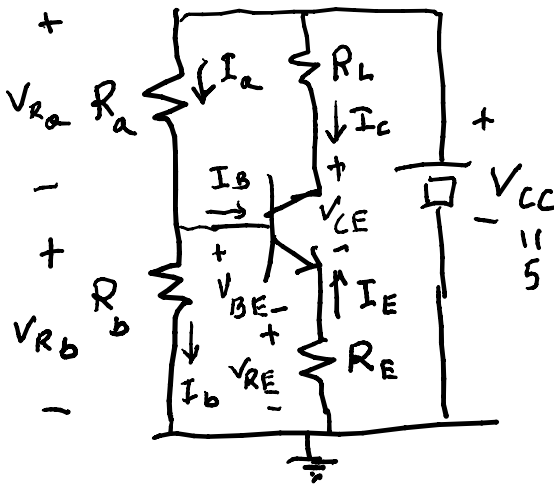


Biasing the 2N2222

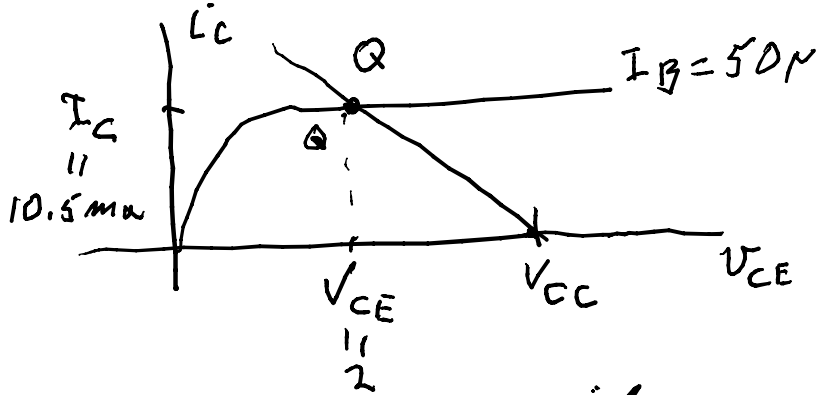

$$-I_E = I_C / \alpha$$

$$\beta = \text{given}$$

$$\alpha = \frac{\beta}{1 + \beta} = \frac{256}{257} = 0.996$$

$$\beta = \beta_f = 256$$

$$-I_E = \frac{10.5 \times 10^{-3}}{0.996} = 10.54 \text{ mA}$$

assume  $V_{BE} = 0.7$ ,  $R_E = 50 \Omega \Rightarrow V_{RE} = R_E (-I_E) = 50 \times 10.54 \text{ mV}$   
 $\approx \frac{100}{2} \times 10.54 \times 10^{-3} = 0.527 \text{ V}$

$$V_{R_b} = V_{BE} + V_{RE} = 1.227 \text{ V}$$

$$\Rightarrow V_{R_a} = V_{CC} - V_{R_b} = 5 - 1.227 = 3.773$$

$$I_B = 50 \text{ nA} \Rightarrow I_a = I_B + I_b \Rightarrow R_a I_a = R_a (I_B + I_b) = 3.773$$

$$R_b I_b = 1.227$$

$$R_a I_B + \frac{1.227}{R_b} \times R_a = 3.773 \Rightarrow \text{solve for } R_a$$


$$R_a \left( I_B + \frac{1.227}{R_b} \right) = 3.773 \Rightarrow R_a = \frac{3.773}{50 \times 10^{-6} + \frac{1.227}{R_b}}$$

choose  $R_b$  in MEG Ohm range,  $R_b = 1 \text{ MEG} = 10^6 \Omega$


$$\Rightarrow R_a = \frac{3.773}{51.227} \times 10^6 = 0.659 \times 10^6 = 659 \text{ K} \Omega$$

also know  $R_L$ :  $V_{RL} = R_L I_C = V_{CC} - V_{RE} - V_{CE} = 5 - 0.527 - 2 = 2.473 \text{ volt}$
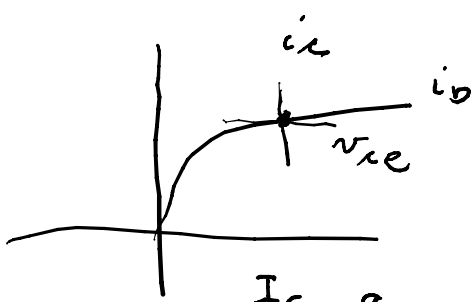
$$R_L = \frac{2.473}{10.5 \times 10^{-3}} = 0.236 \times 10^3 = 236 \Omega$$




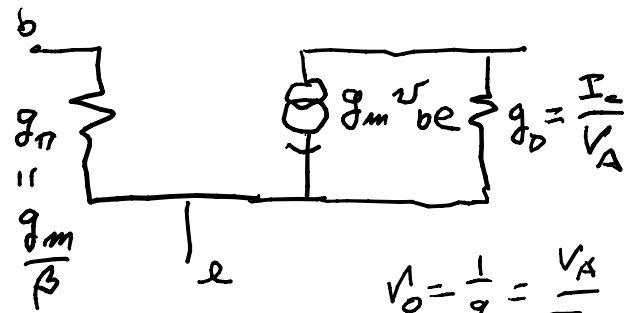
$$\frac{I_C}{V_T} = g_m = \frac{10.5 \text{ mA}}{26 \text{ mV}} = 0.404 \text{ V}^{-1}$$



$$r_{\pi} = \frac{1}{g_{\pi}} = 633 \Omega$$

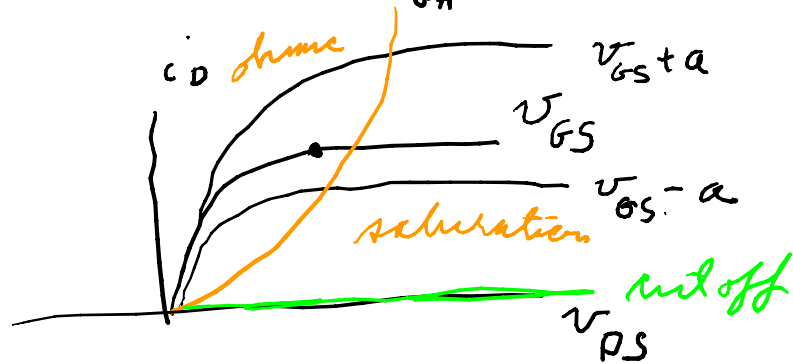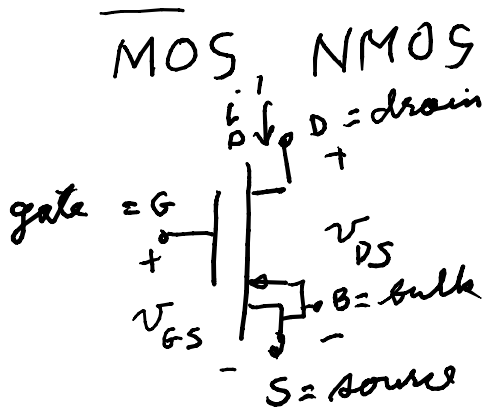
$$V_o = \frac{1}{g_o} = \frac{V_A}{I_C} = \frac{74.03}{10.5 \times 10^{-3}} = 7.05 \text{ k}\Omega$$




$$i_D = \begin{cases} 0 & v_{GS} \leq V_{T0} \text{ (cut off)} \\ \frac{K_P}{2} \times \frac{W}{L} (v_{GS} - V_{T0})^2 (1 + \lambda v_{DS}) & v_{GS} - V_{T0} \leq v_{DS} \text{ (saturation)} \\ \frac{K_P}{2} \times \frac{W}{L} \left[ (v_{GS} - V_{T0}) v_{DS} - \frac{1}{2} v_{DS}^2 \right] (1 + \lambda v_{DS}) & v_{DS} \leq v_{GS} - V_{T0} \text{ (ohmic triode)} \end{cases}$$

$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_Q = 2 \times \frac{K_P}{2} \times \frac{W}{L} (v_{GS} - V_{T0}) (1 + \lambda v_{DS}) \Big|_Q = 2 \frac{I_D}{(V_{GS} - V_{T0})}$$

(overdrive)

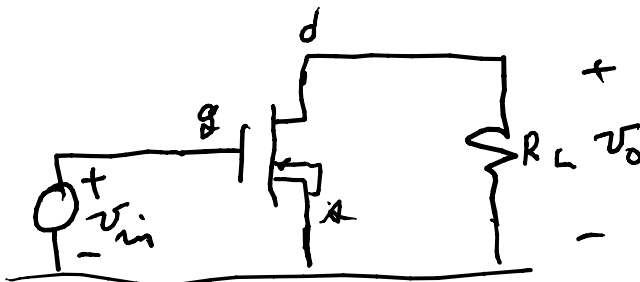

$$\frac{v_o}{v_{in}} = -g_m R_L$$

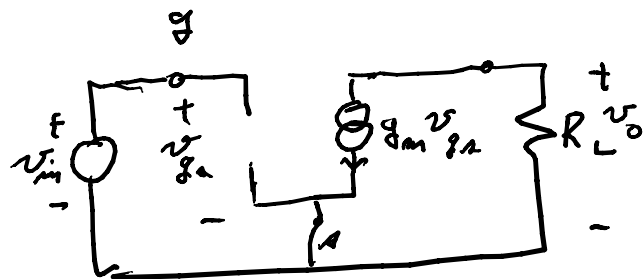

$$v_o = (-g_m v_{in}) R_L$$