
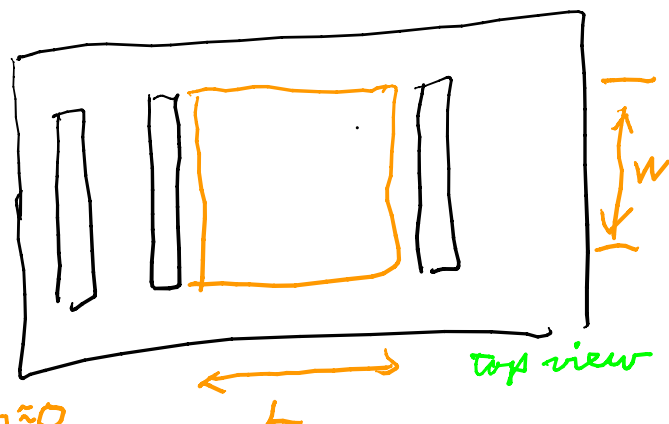
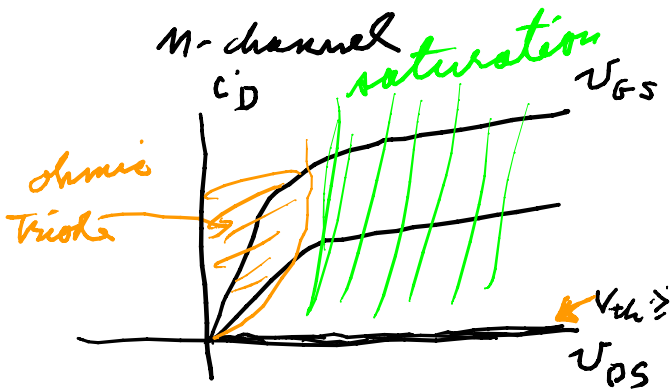
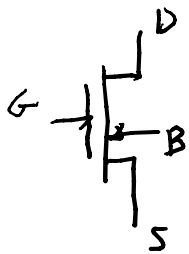


MOS, p. 253 = picture

pp. 354-355 eq

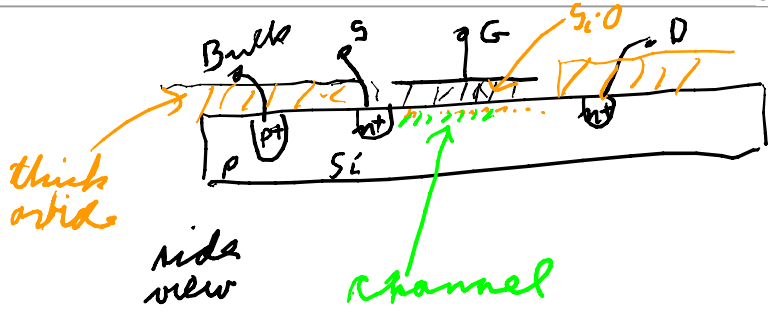


$V_{th} = \text{threshold voltage} = V_{T0}$
if $v_{DS} = 0$

$$i_D = \frac{k_p \cdot W}{2 \cdot L} \times \begin{cases} 0 & \text{if } v_{GS} \leq V_{th} \text{ cutoff} \\ (v_{GS} - V_{th})^2 (1 + \lambda v_{DS}) & \text{if } v_{GS} \geq V_{th}, v_{GS} - V_{th} \leq v_{DS} \text{ saturation} \\ [2(v_{GS} - V_{th})v_{DS} - v_{DS}^2] (1 + \lambda v_{DS}) & \text{if } v_{GS} \geq V_{th}, v_{GS} - V_{th} \geq v_{DS} \end{cases}$$

here $V_{th} = V_{T0} + \gamma \left(\sqrt{-v_{BS} + 2\phi_f} - \sqrt{2\phi_f} \right)$
(p. 324)


$2 \phi_f \approx 2/3$ for NMOS
 $\approx 3/4$ for PMOS
 $[v_{BS} \rightarrow v_{SB_p}]$

Equivalent small signal circuit

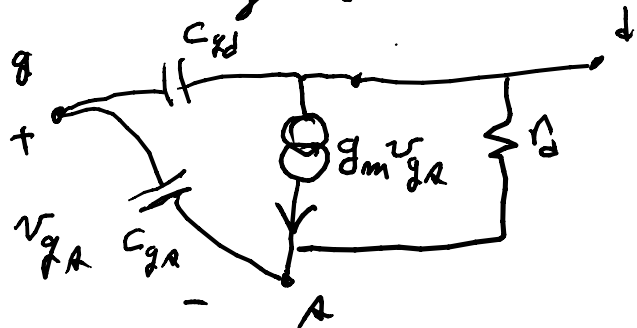

i_D are proportional to W/L



For PMOS

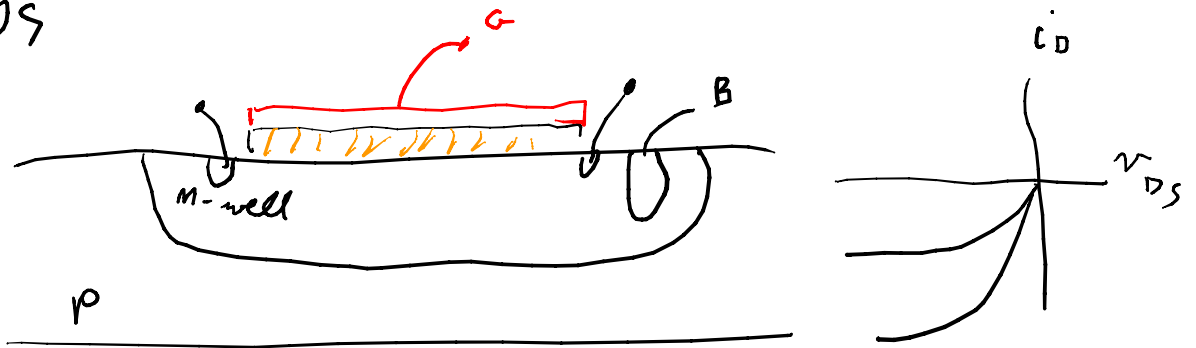

Interested in g_m & g_d ; in saturation region

$$g_m = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_Q = \frac{2I_D}{(V_{GS} - V_{th})} \quad , \quad g_d = \left. \frac{\partial I_D}{\partial v_{DS}} \right|_Q = \frac{\lambda I_D}{1 + \lambda v_{DS}} \approx \lambda I_D$$

Current Mirrors

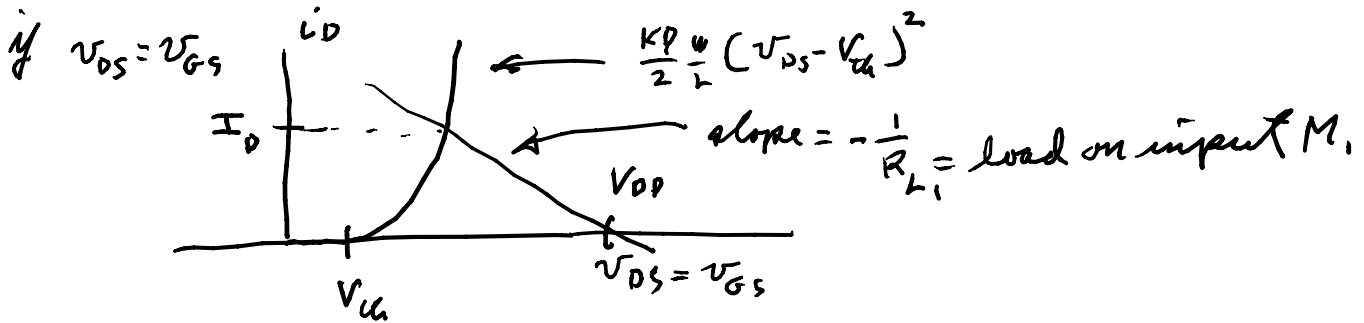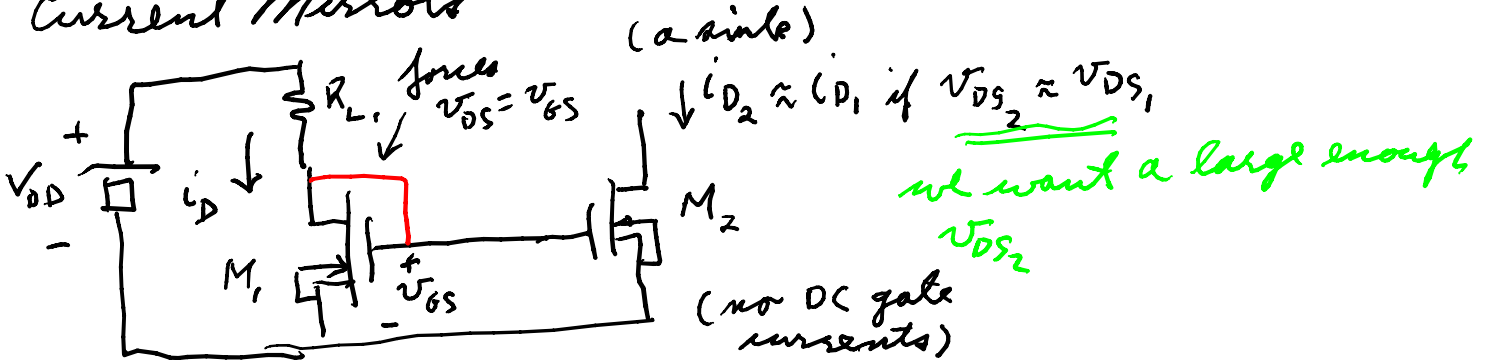

(see NA 741 op amp, p. 1003 for its BJT realization; many current mirrors, differential pairs & a power output).

source current, use PMOS

